


# Lecture 5

## EE 421 / CS 425

# Digital System Design

Fall 2024

Shahid Masud

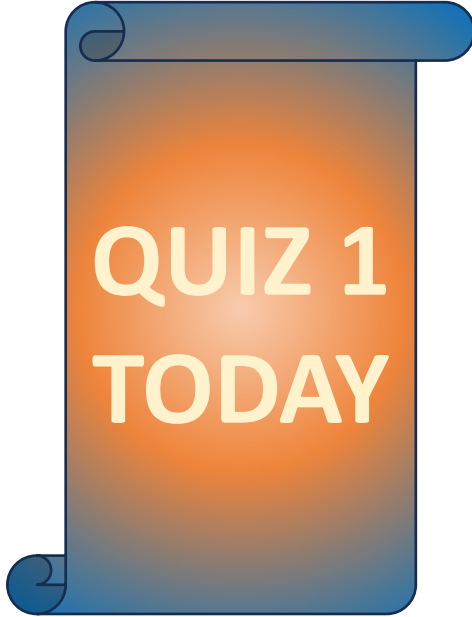

QUIZ 1  
TODAY



# Topics

- Pulse Circuits
- Timing Related Effects in Combinational Circuits
- Glitches
- Hazards
- Identify and Remove Glitches and Hazards (May do in next lecture)
- QUIZ 1 Today

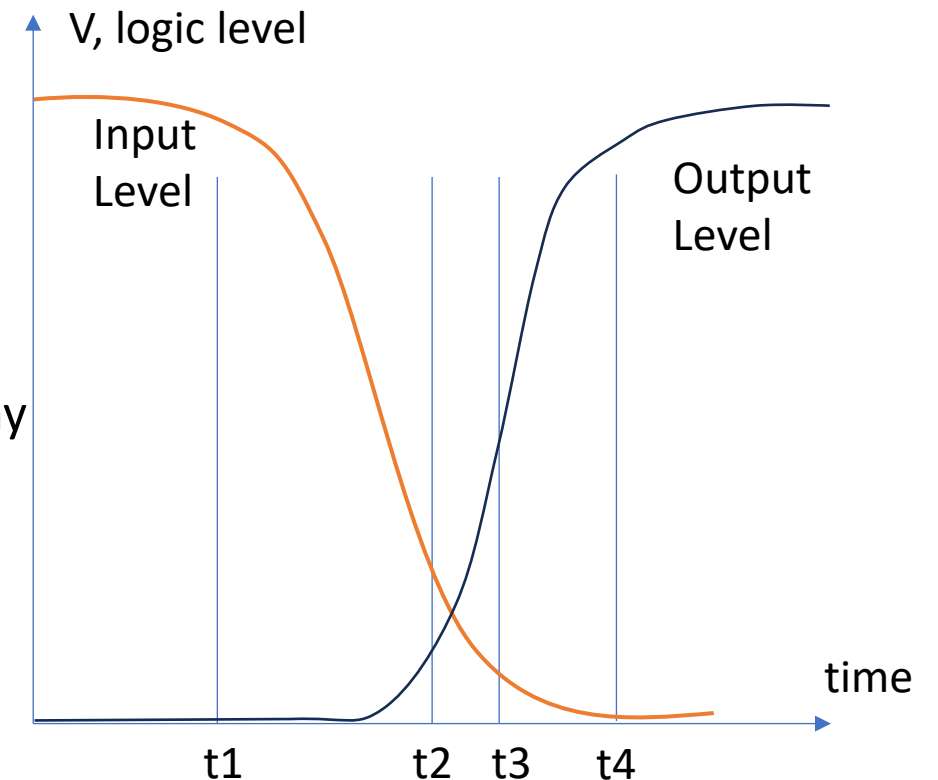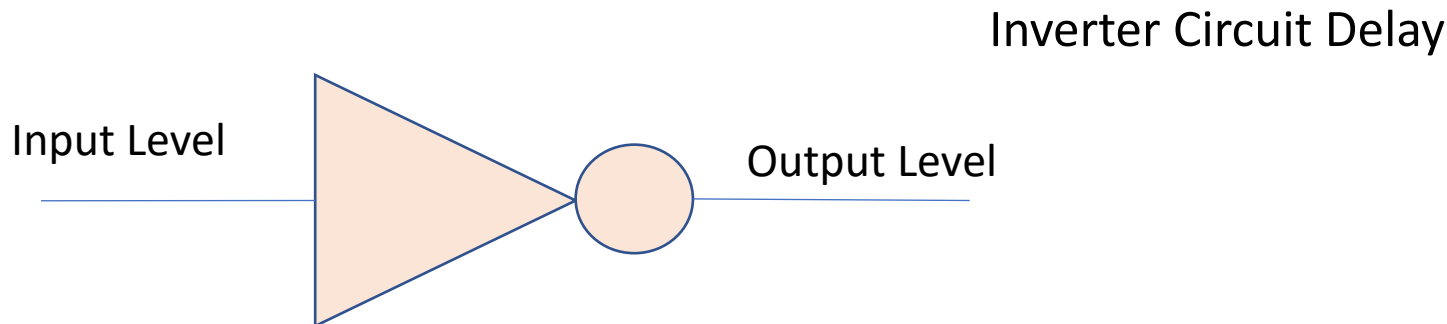
# Timing Waveforms

Every physical circuit has some processing delay; once the input has settled, **the correct output appears after some time.**


Propagation delay from a gate is defined by:  
 $t_{plh}$  = time delay in output going from low to high  
 $t_{phl}$  = time delay in output going from high to low



# A simple pulse circuit

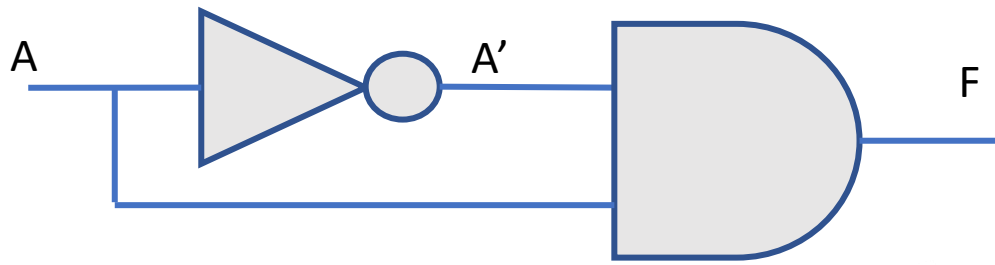


Each gate has Propagation Delay

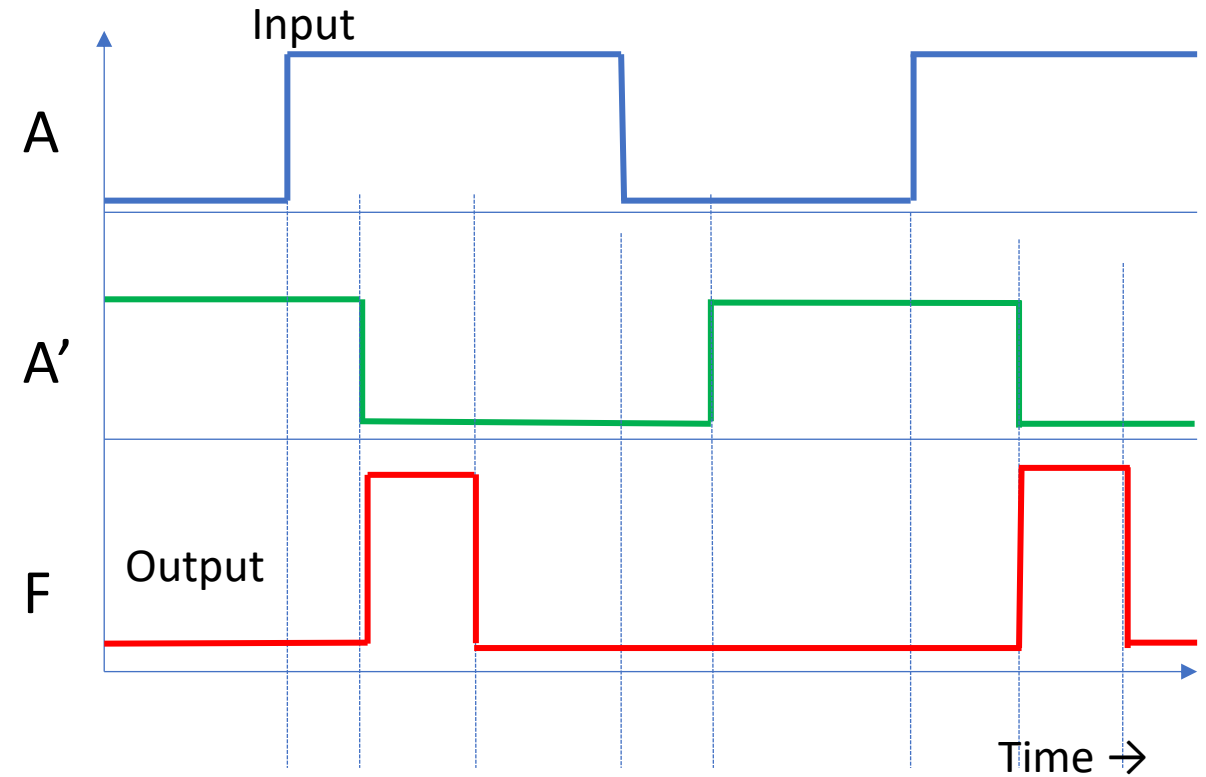


Question: What will be the Output if there are two inverters in series?

Question: What will be the Output if there are three inverters in series?
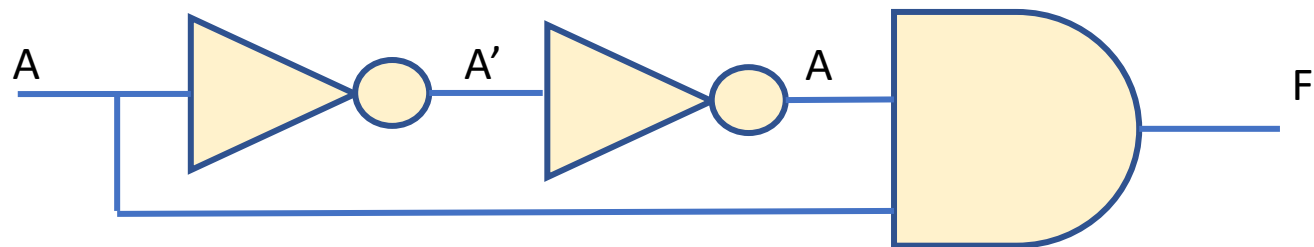
# Two and Three Inverters in simple pulse circuit




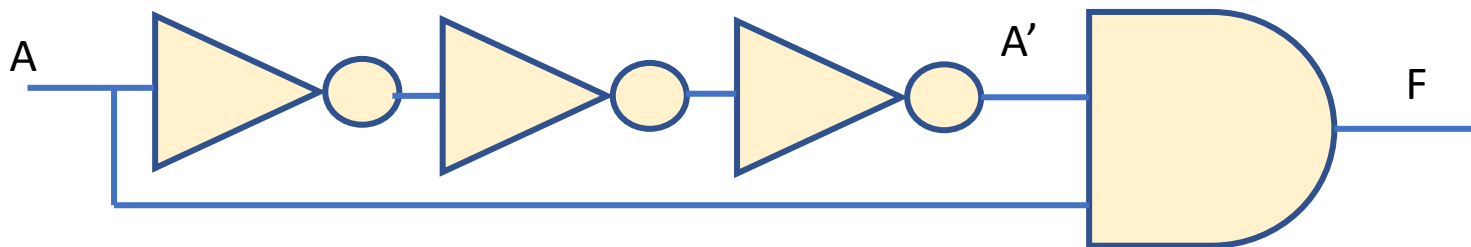For even number of Inverters:  
Check input  $A$  transitions from 0 to 1 and from 1 to 0  
Pulse behaviour is not observed  
(Hint: Check whether  $F$  is like  $A$ ?)



For Odd number of Inverters:  
At 0 to 1 transitions at  $A$ , a pulse will appear at  $F$ . The pulse width is proportional to number of inverters as their propagation delay adds up

# A Pulse Shaper Circuit

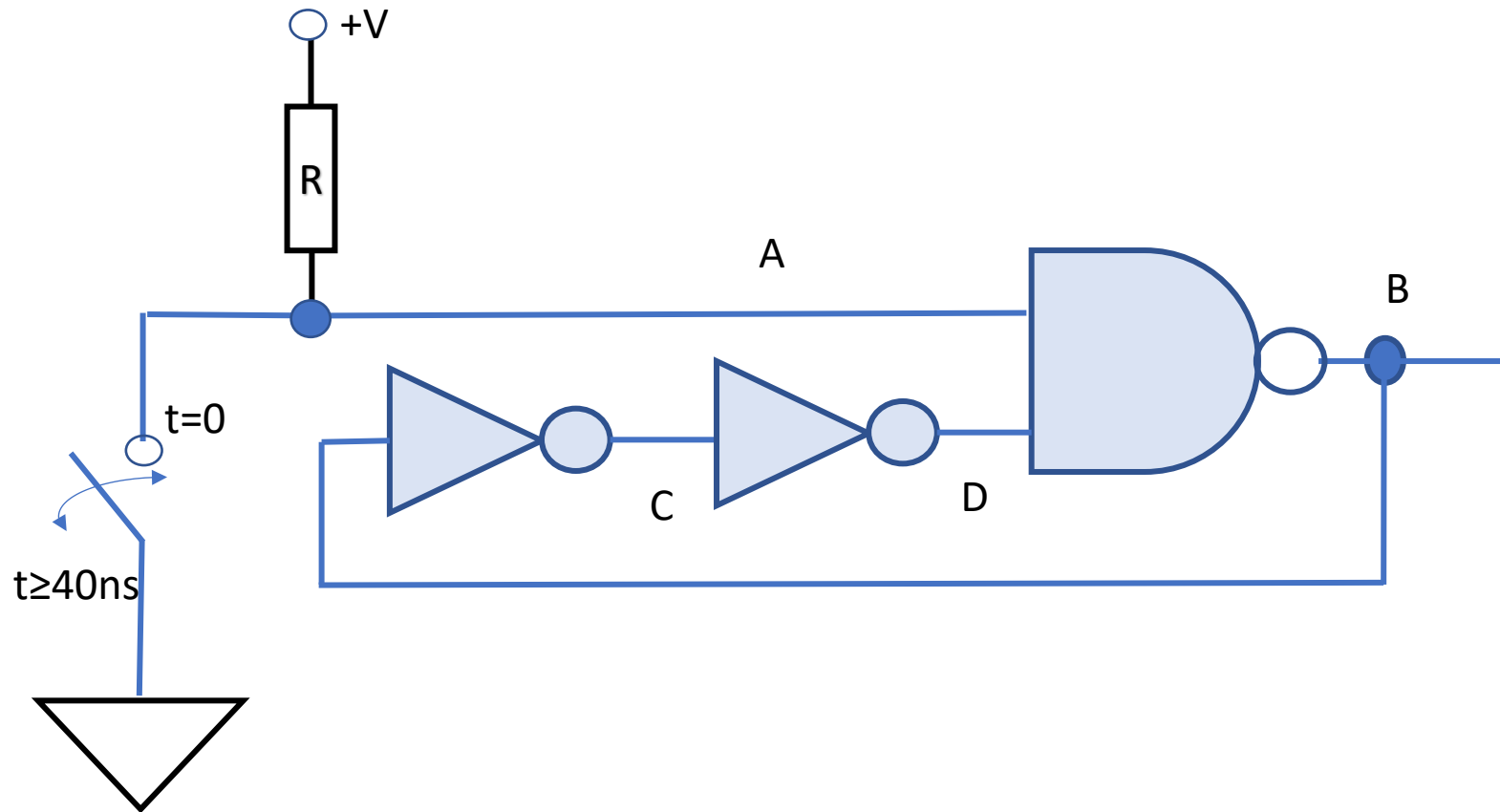

## Case 1:

Assume propagation delay of gates as  $10\text{ns}$

Switch is closed at  $t=0\text{ns}$ , thus:

$A$  goes to '0' at time  $t=0\text{ns}$

$B$  goes to '1' at time  $t=10\text{ns}$


$C$  goes to '0' at time  $t=20\text{ns}$

$D$  goes to '1' at time  $t=30\text{ns}$

Since  $D='1'$ ,  $A='0'$ , hence:

**Output  $B='0'$  always for  $A='0'$  in steady state**

# Pulse Shaper Circuit – Case 2

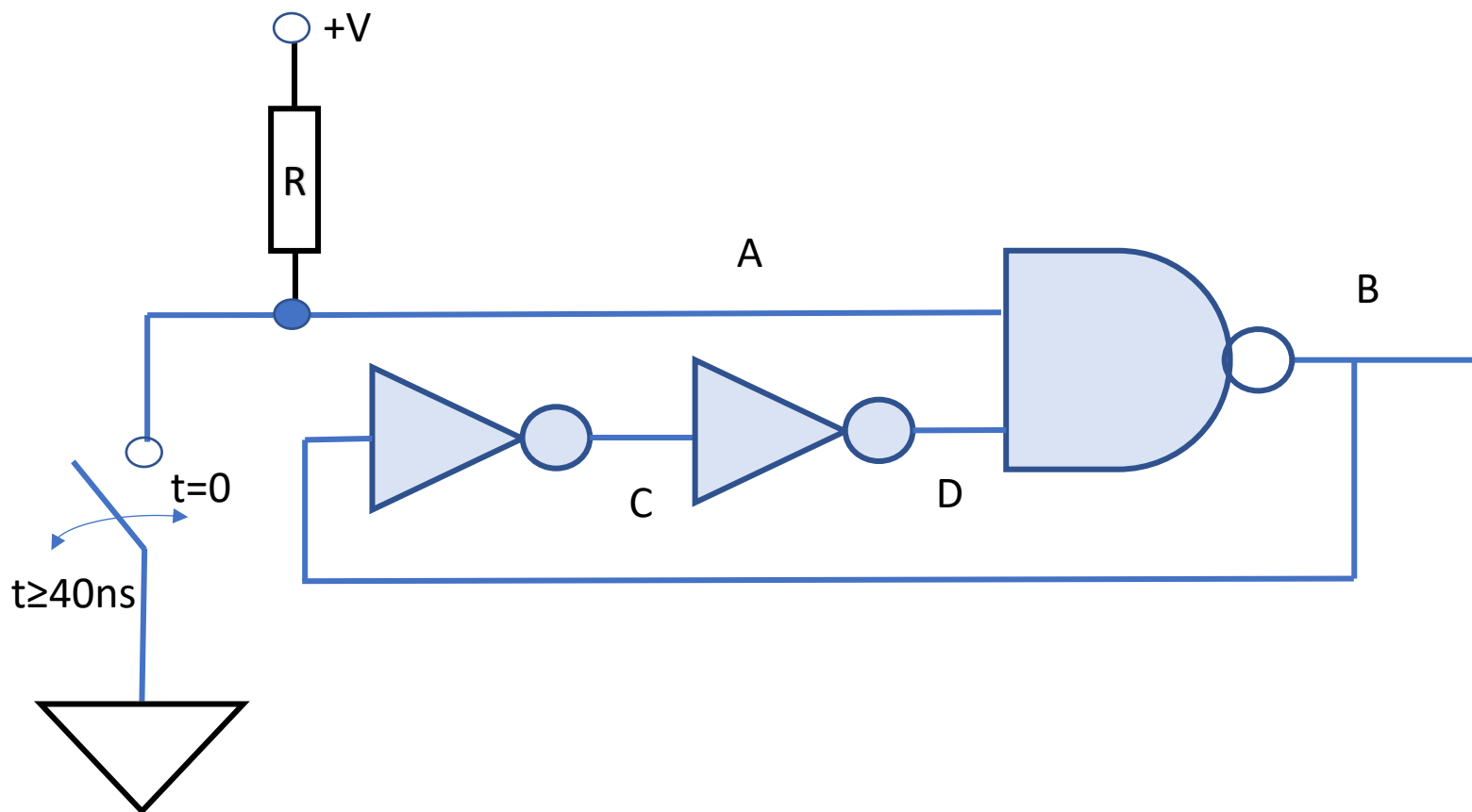

## Case 2:

Assume propagation delay of gates as 10ns

Output B was in steady state = '0' while Switch was closed at t=0

Now Switch is opened at t=40ns

So A goes to '1' at t=40ns

B goes to '0' after 10ns at t=50ns

C goes to '1' at t = 60ns

D goes to '0' at t = 70ns

Now D='0' and A='1', hence B='1' at t=80ns

C goes to '0' at t=90ns

D goes to '1' at t=100ns

Since A = '1' and D='1' so B='0' at t=110ns

Time Period of this oscillator is determined by propagation delay of gates

Same behavior can be obtained from a NOR gate circuit with some changes

The cycle will start repeating automatically

We get an **OSCILLATOR**

# Glitches and Hazards

**Glitch:** An Unwanted Pulse at the Output of a Combinational Logic Circuit. Glitch is dependent upon Inputs and how the circuit is configured


**Hazard:** A Combinational Logic Circuit with a potential to produce Glitches is called a Hazard.

## Possible Reasons:

1. Using Un-Stable Input Signals
2. Not Considering Propagation Delays in high-speed designs
3. Using Asynchronous Inputs




# Kinds of Hazards

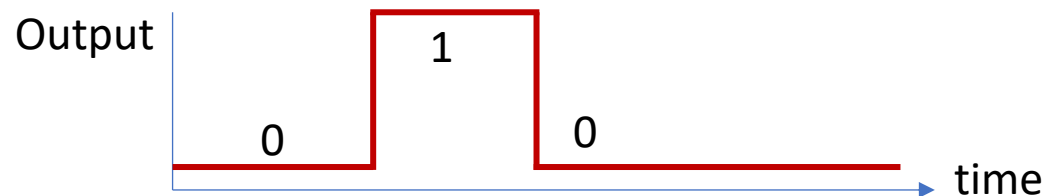


Input Changes cause output to change from '0' to '1' to '0'

**STATIC ZERO HAZARD**

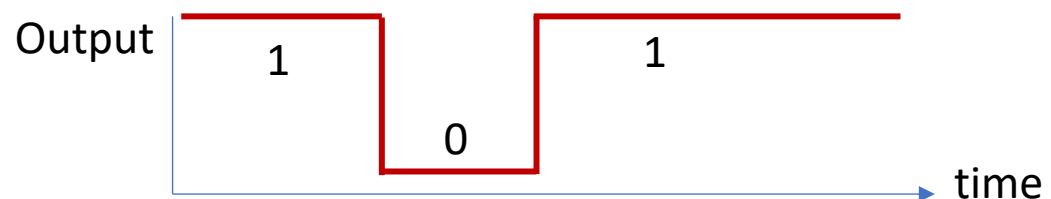

Input Changes cause output to change from '1' to '0' to '1'



**STATIC ONE HAZARD**

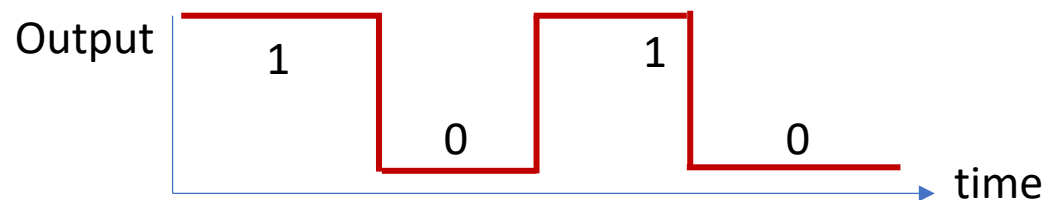

Input Changes cause two or more changes from '1' to '0' to '1' to '0', Or changes from '0' to '1' to '0' to '1'



**DYNAMIC HAZARD**

# Circuit with Static 1 Hazard

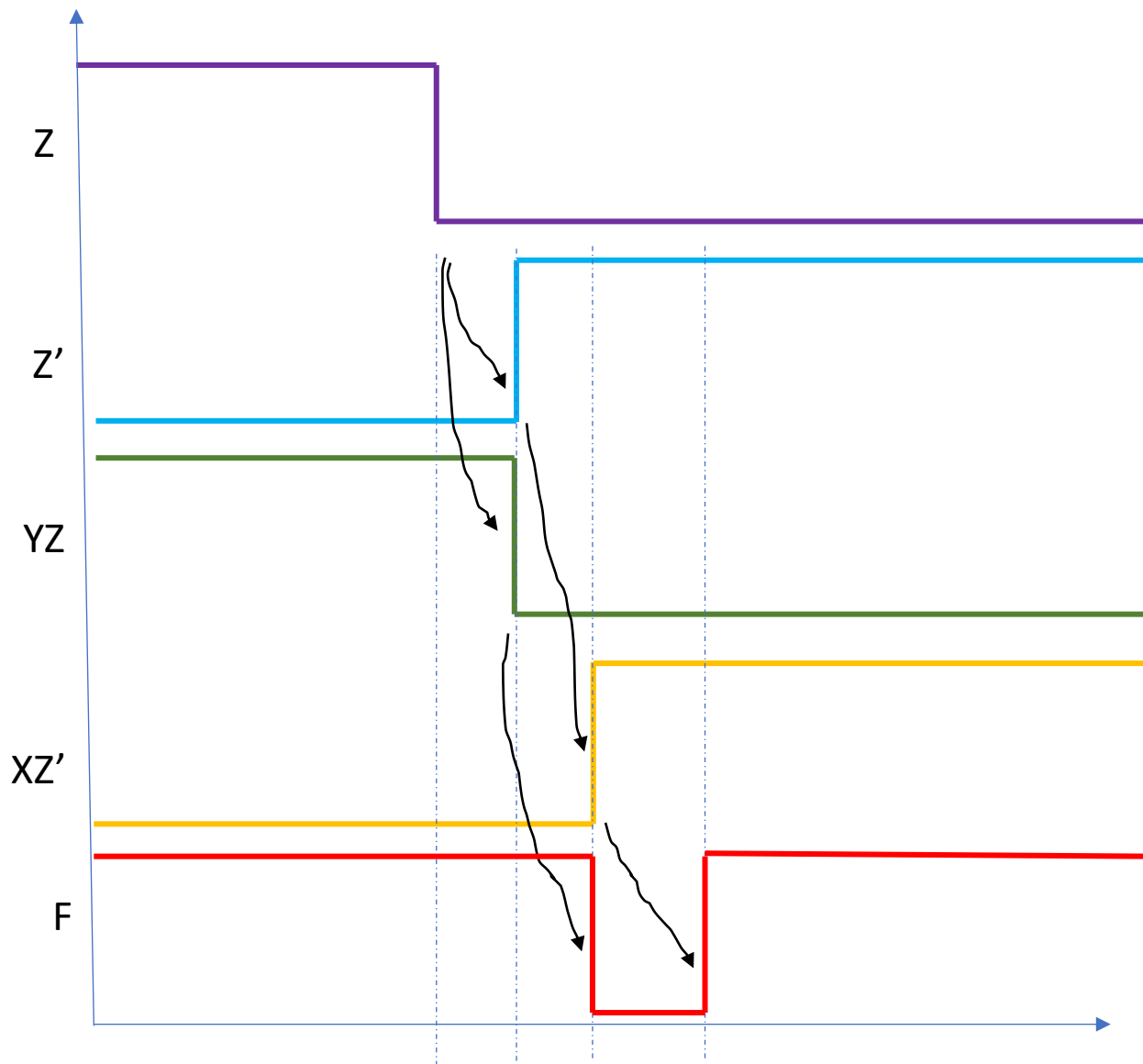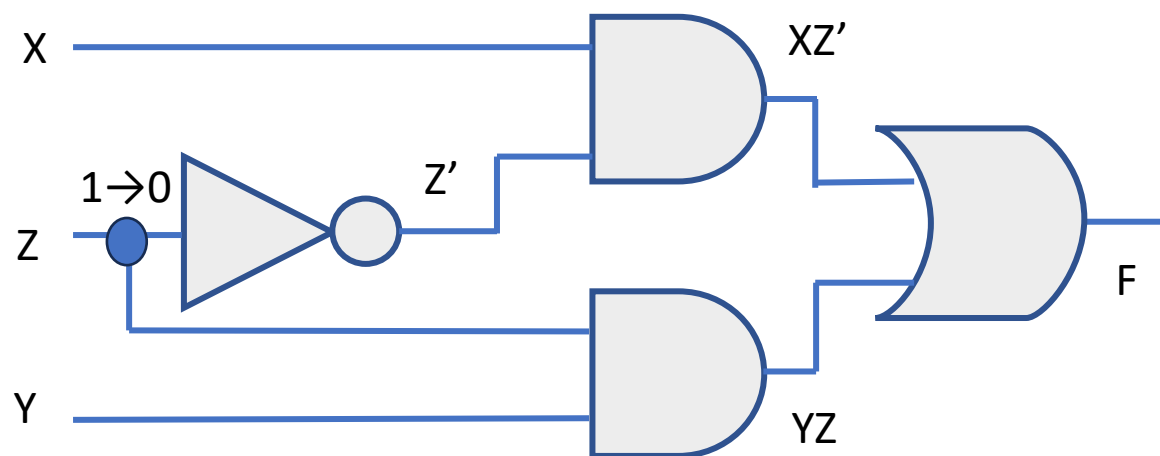


Static 1 Hazard Observed

# Example of Static 0 Hazard

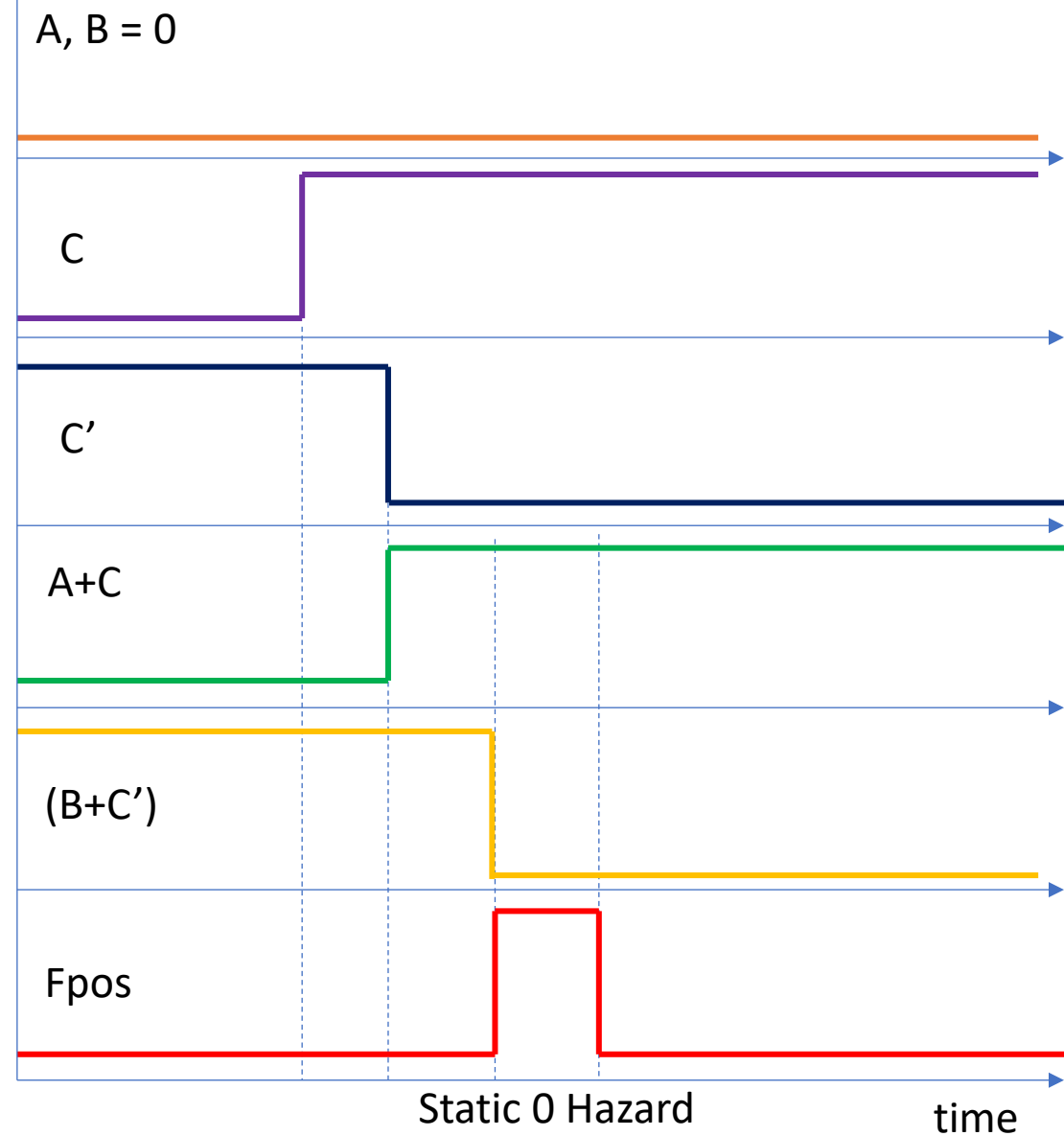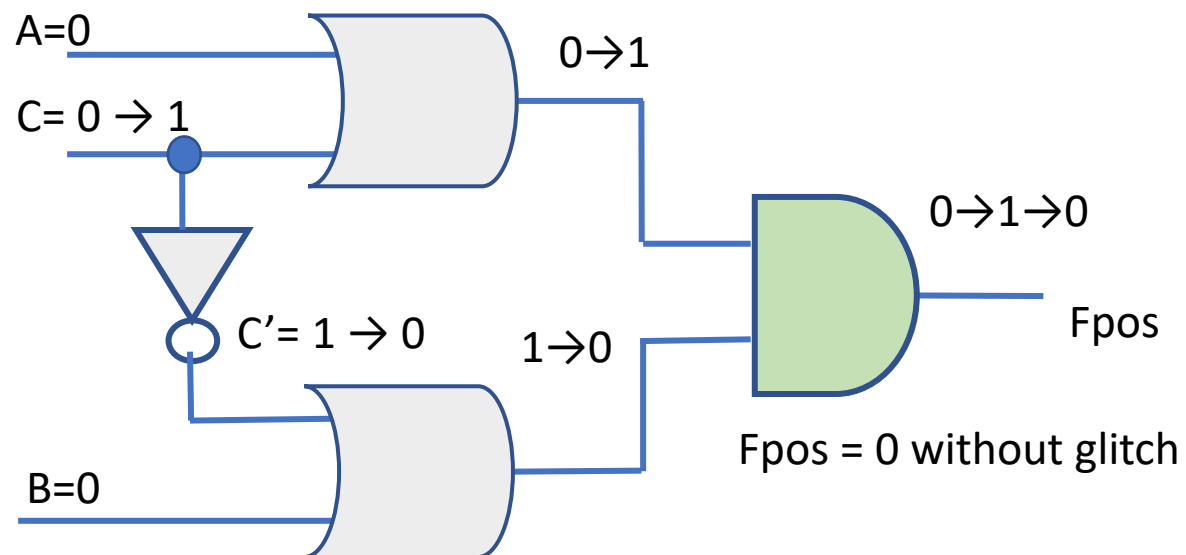

# K Maps to Identify Hazards

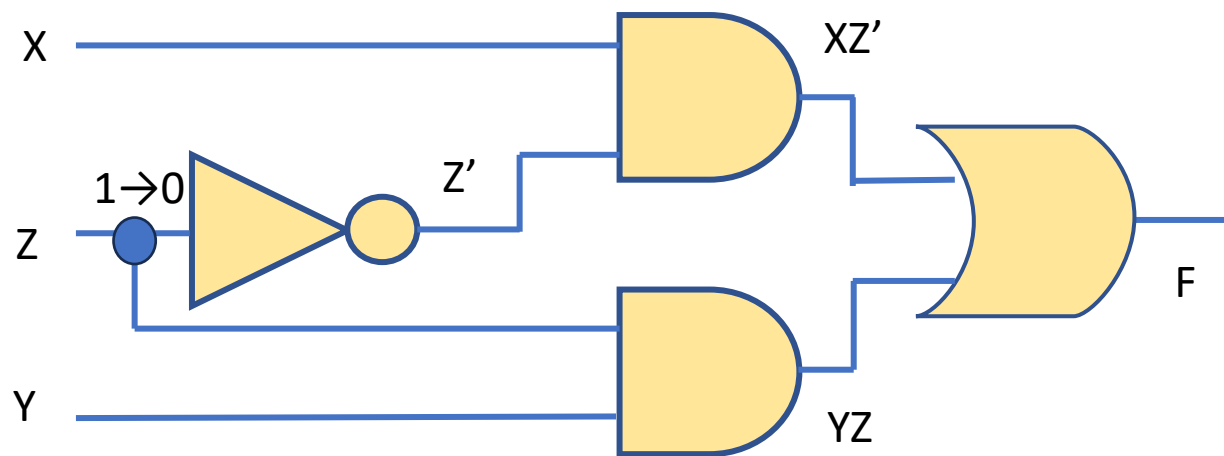

$$F = XZ' + YZ$$

| Z, XY | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 0     | 0  | 0  | 1  | 1  |
| 1     | 0  | 1  | 1  | 0  |


YZ

XZ'

# How to Know about Hazards?

- A properly designed two level SOP (AND-OR) circuit has no Static-0 Hazard
- This type of SOP circuits can have Static-1 Hazards
- Look at the K-Map again and we notice that there is no single product term that covers the inputs  $XYZ=111$  and  $XYZ=110$ . Thus glitch to 0 is possible if the AND gate covering the other combination goes to 1.
- To Eliminate Such Hazards:
- Include an extra product term (AND gate) to cover the hazard input. This is where the adjacent 1s exist in K-Maps but are not covered. This is called 'Adding a Consensus Term'


# Hazard Free two level SOP Circuit

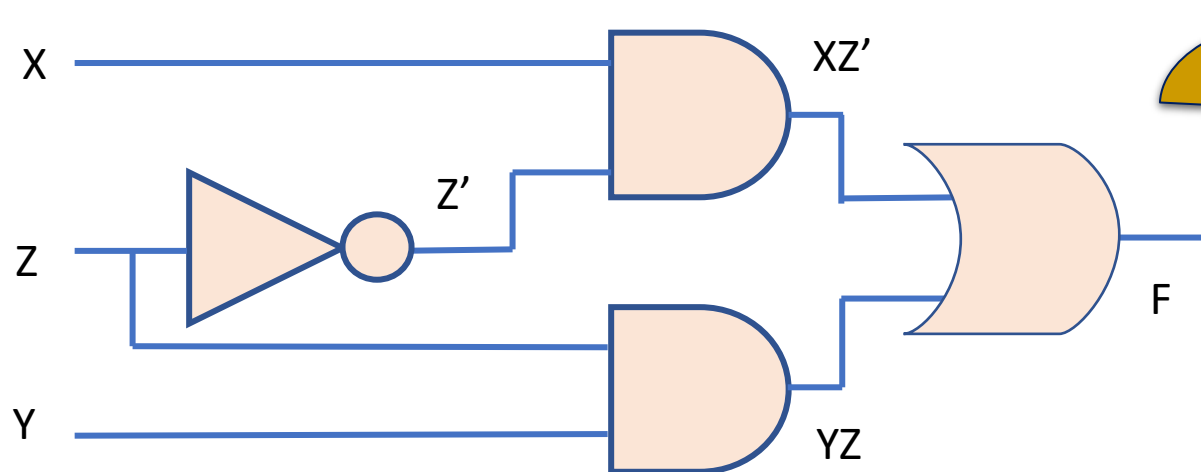

K-Map for  $F(X, Y, Z)$ :

| Z, XY | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 0     | 0  | 0  | 1  | 1  |
| 1     | 0  | 1  | 1  | 0  |

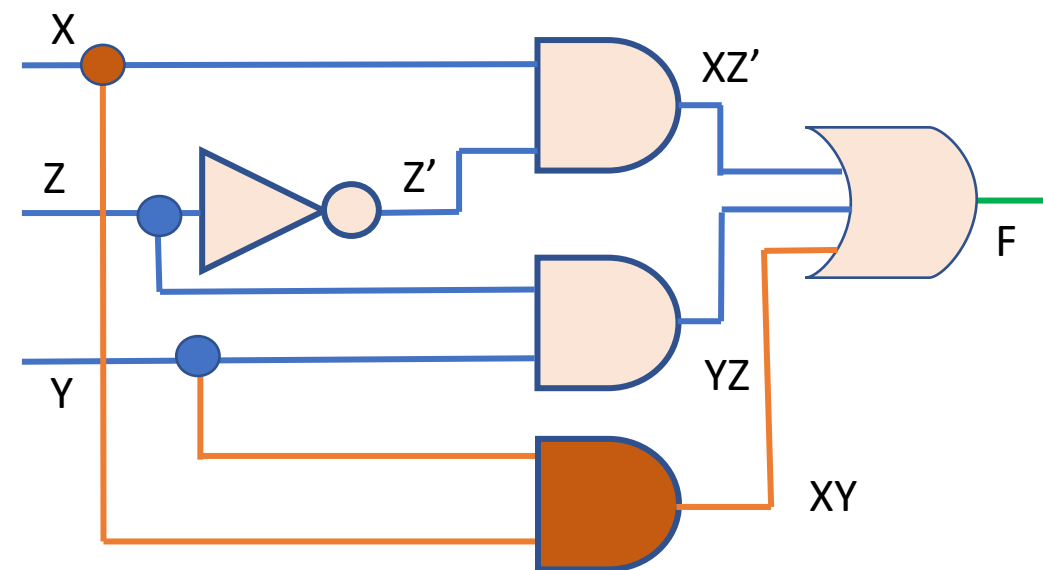Groupings:  $XZ'$  (top row),  $YZ$  (left column), and Consensus Term  $XY$  (the 1s at (0,1) and (1,1)).



$F$  including Consensus Term =  $XY + YZ + XZ'$

**Final Hazard Free Circuit  
Including Extra Consensus Circuit**

**The Adjacent 1s in K-Map are now Covered**

# Using K-Map to Identify Static 1 Hazard in 4 input variables

| AB, CD | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 00     | 0  | 1  | 1  | 0  |
| 01     | 1  | 1  | 0  | 0  |
| 11     | 1  | 1  | 1  | 1  |
| 10     | 0  | 0  | 1  | 1  |

Given K-Map with Minimal Grouping

**Identify the Hazards**

**Adjacent 1s that are not in the same group**

# K-Map Groups to Eliminate Static 1 Hazard

| YZ, WX | 00 | 01 | 10 | 11 |
|--------|----|----|----|----|
| 00     | 0  | 1  | 1  | 0  |
| 01     | 1  | 1  | 0  | 0  |
| 11     | 1  | 1  | 1  | 1  |
| 10     | 0  | 0  | 1  | 1  |

$XY'Z'$  (points to cell 01, 10)  
 $W'Z$  (points to cell 01, 00)  
 $WY$  (points to cell 11, 11)

Minimal Expression:  
 $F = XY'Z' + W'Z + WY$



| AB, CD | 00 | 01 | 10 | 11 |
|--------|----|----|----|----|
| 00     | 0  | 1  | 1  | 0  |
| 01     | 1  | 1  | 0  | 0  |
| 11     | 1  | 1  | 1  | 1  |
| 10     | 0  | 0  | 1  | 1  |

$W'XY'$  (points to cell 01, 00)  
 $WXZ'$  (points to cell 10, 00)  
 $YZ$  (points to cell 11, 11)

Hazard Free Expression:  
 $F = XY'Z' + W'Z + WY + W'XY' + YZ + WXZ'$



# K-Map Grouping to Eliminate Static 0 Hazard

POS = Grouping of Zeros

| AB, CD | 00 | 01 | 10 | 11 |
|--------|----|----|----|----|
| 00     | 1  | 1  | 0  | 0  |
| 01     | 1  | 1  | 1  | 1  |
| 11     | 0  | 0  | 1  | 1  |
| 10     | 0  | 0  | 0  | 0  |

$(B + C')$

$(A' + C)$

Minimal Mapping without Hazard Consideration

$$F = (A' + C) (B + C')$$

| AB, CD | 00 | 01 | 10 | 11 |
|--------|----|----|----|----|
| 00     | 1  | 1  | 0  | 0  |
| 01     | 1  | 1  | 1  | 1  |
| 11     | 0  | 0  | 1  | 1  |
| 10     | 0  | 0  | 0  | 0  |


$(A' + B)$

Additional Cover for Static 0 Hazard prevention

$$F = (A' + C) (B + C') (A' + B)$$

Now free from Static 0 Hazard

# Example of Static 0 Hazard

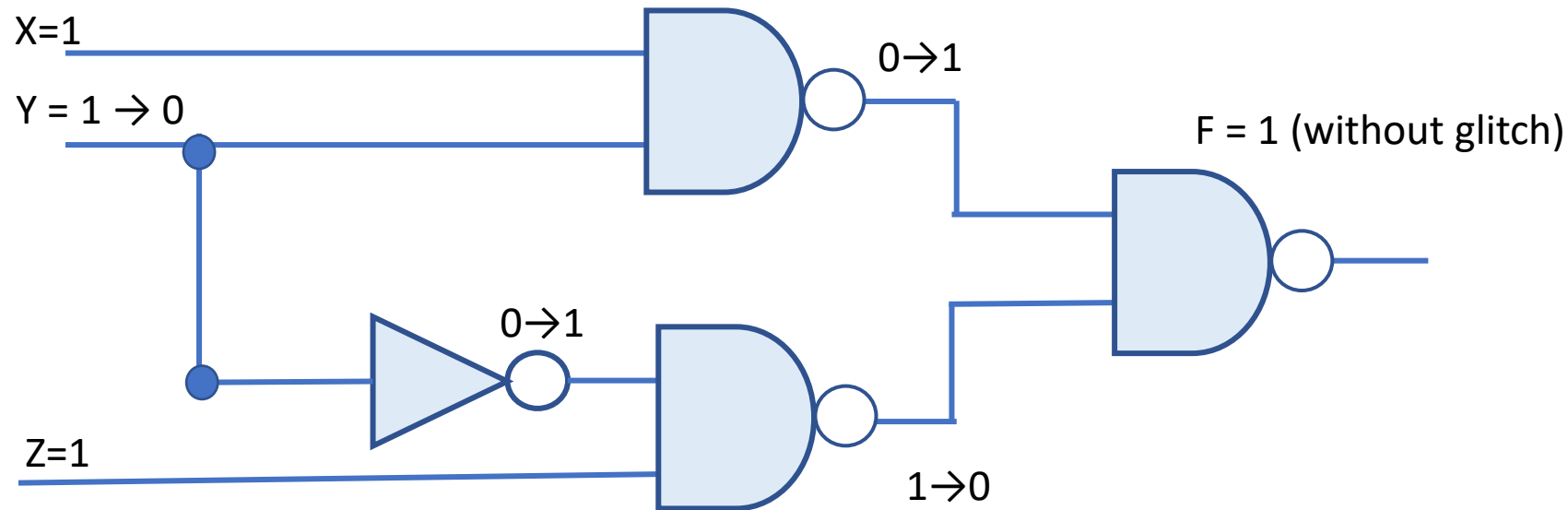


$$F = (X + Y') \cdot (Y + Z)$$

When  $Y$  changes from 1 to 0, both inputs of Nand Gate  $F$  may be equal to 1, Causing the output to momentarily go to 0 when it should have stayed at 1.

# Dynamic Hazards

- Dynamic Hazard is the possibility of an output changing more than once as the result of a single input transition.
- These can occur if there are multiple paths with different delays from the input to the output
- Dynamic Hazards do not occur in properly designed two level AND-OR or OR-AND Circuits.
- Thus remove all Static-1 and Static-0 Hazards in the two-level SOP or POS design and the possibility of Dynamic Hazards is minimized.

# Circuit containing Dynamic Hazard

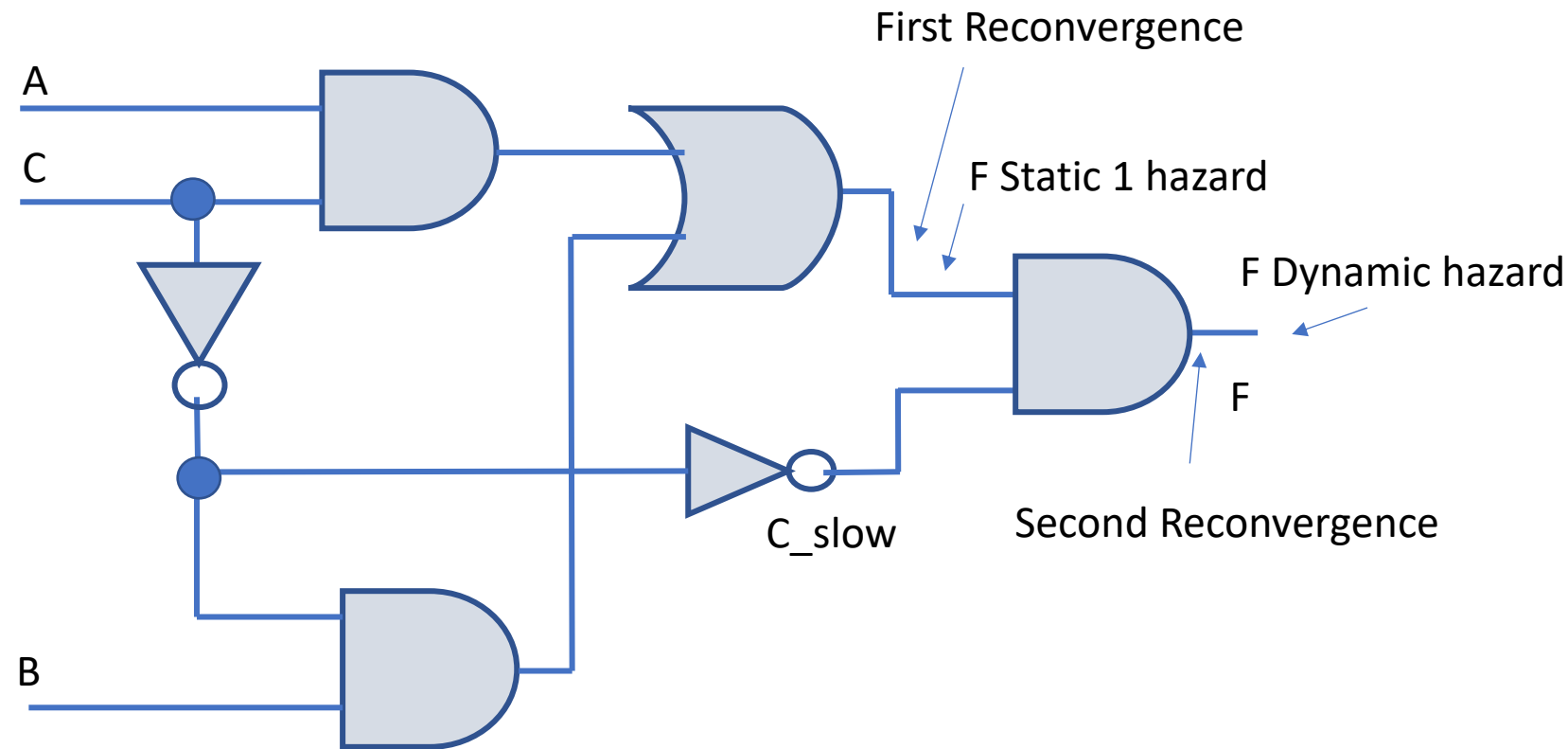

Try changing  
ABC from 110 to 111

**Solution: Make K Map and add redundant cover for C**

