

Lecture 11

EE 421 / CS 425

Digital System Design

Fall 2024

Shahid Masud

Topics


- Communication Signaling across modules at different clock speeds
(Revision – How clock is good and can be bad?) Quick Review
- -----
- Computer Arithmetic Circuits
- Basic Element – Full Adder
- Ripple Carry Adder – Timing Issues
- Bit Serial Adder – Concept of Throughput and Latency
- Carry Look Ahead Adder
- Carry Select Adder

Quiz 3
Next Monday

Self-Timed and Speed Independent Circuits



- Having a completed Synchronous system is at times too challenging for a complex and fast digital system
- The limiting problem becomes how to distribute a single global clock without introducing intolerable clock skew
- The alternate is to partition the digital system into locally clocked pieces that communicate with each other using delay-insensitive signaling techniques (i.e. local clock for local communication)
- Each block proceeds at its own speed without the need for a global clock, synchronizing local communication whenever needed
- Usually a Request-Response Signaling method is employed

Data Transfer in Complex Modular Design

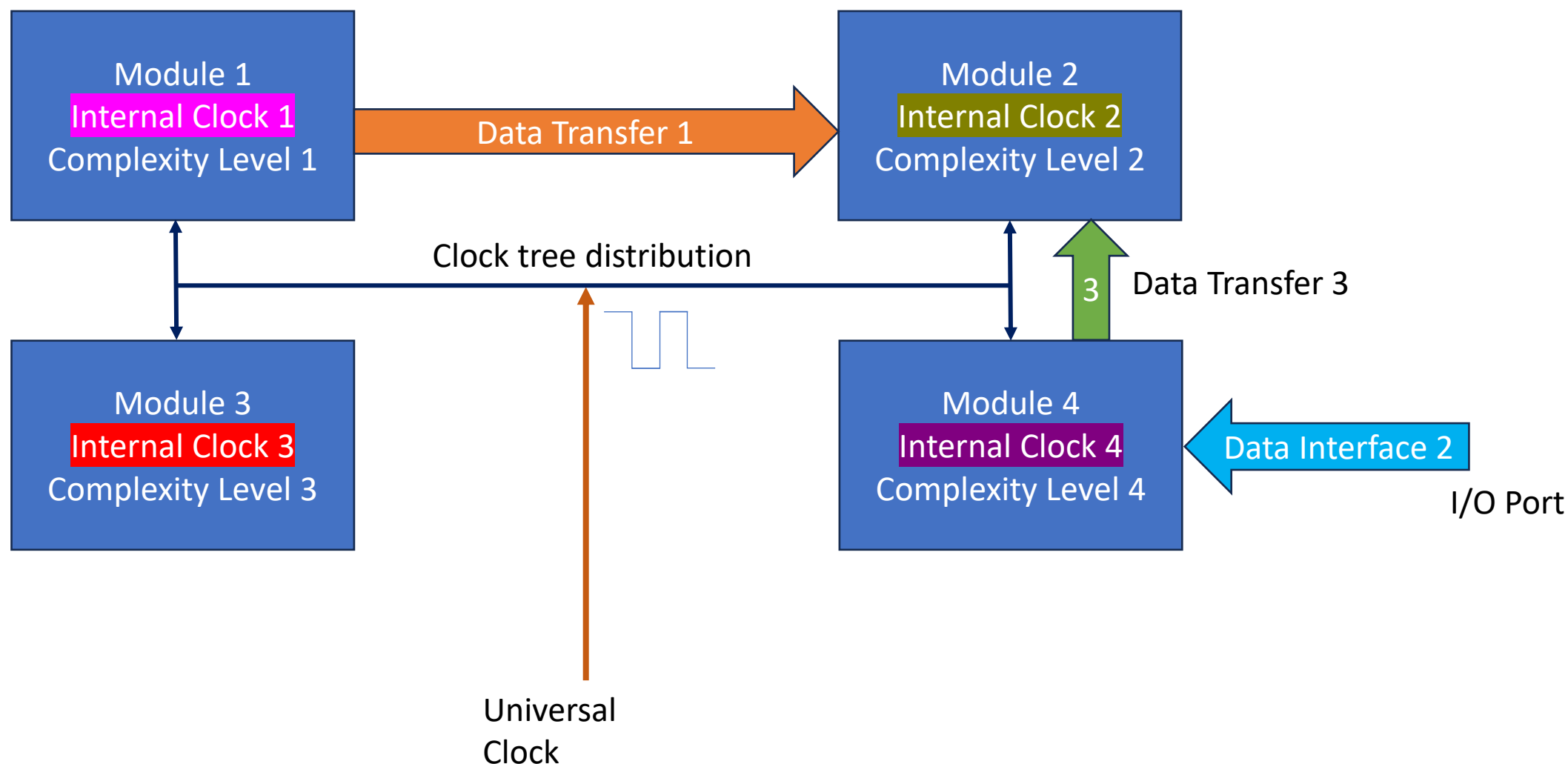


Request / Acknowledge Signaling

Independently clocked Subsystems

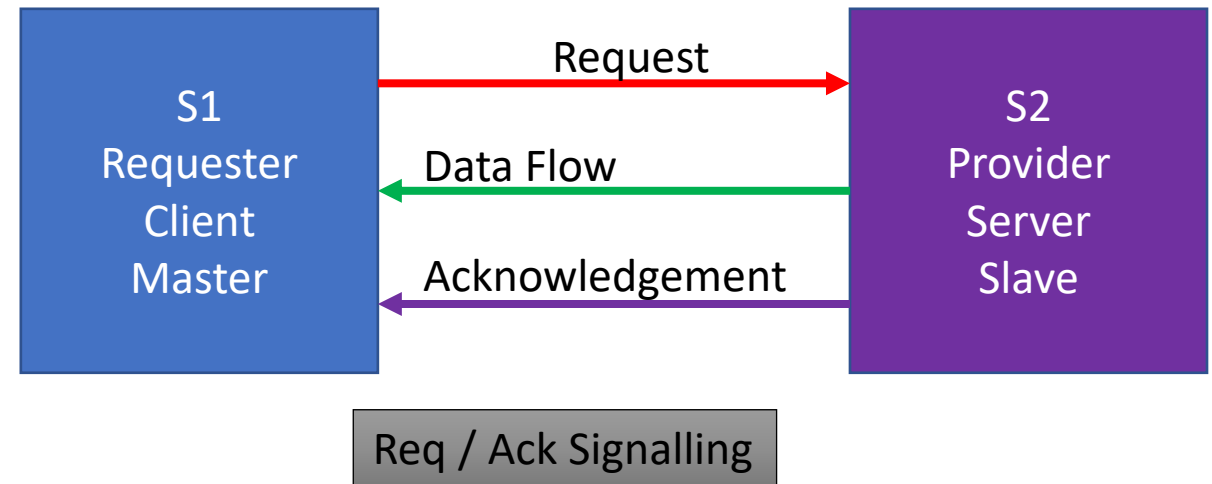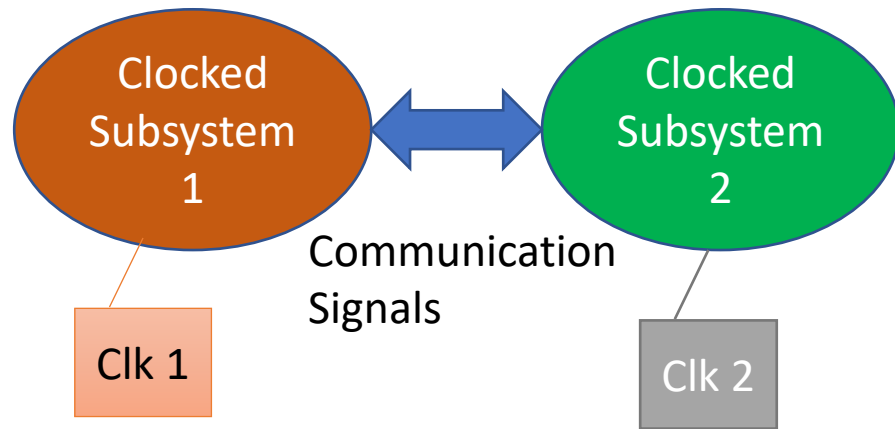


Synchronous Req / Ack Signaling

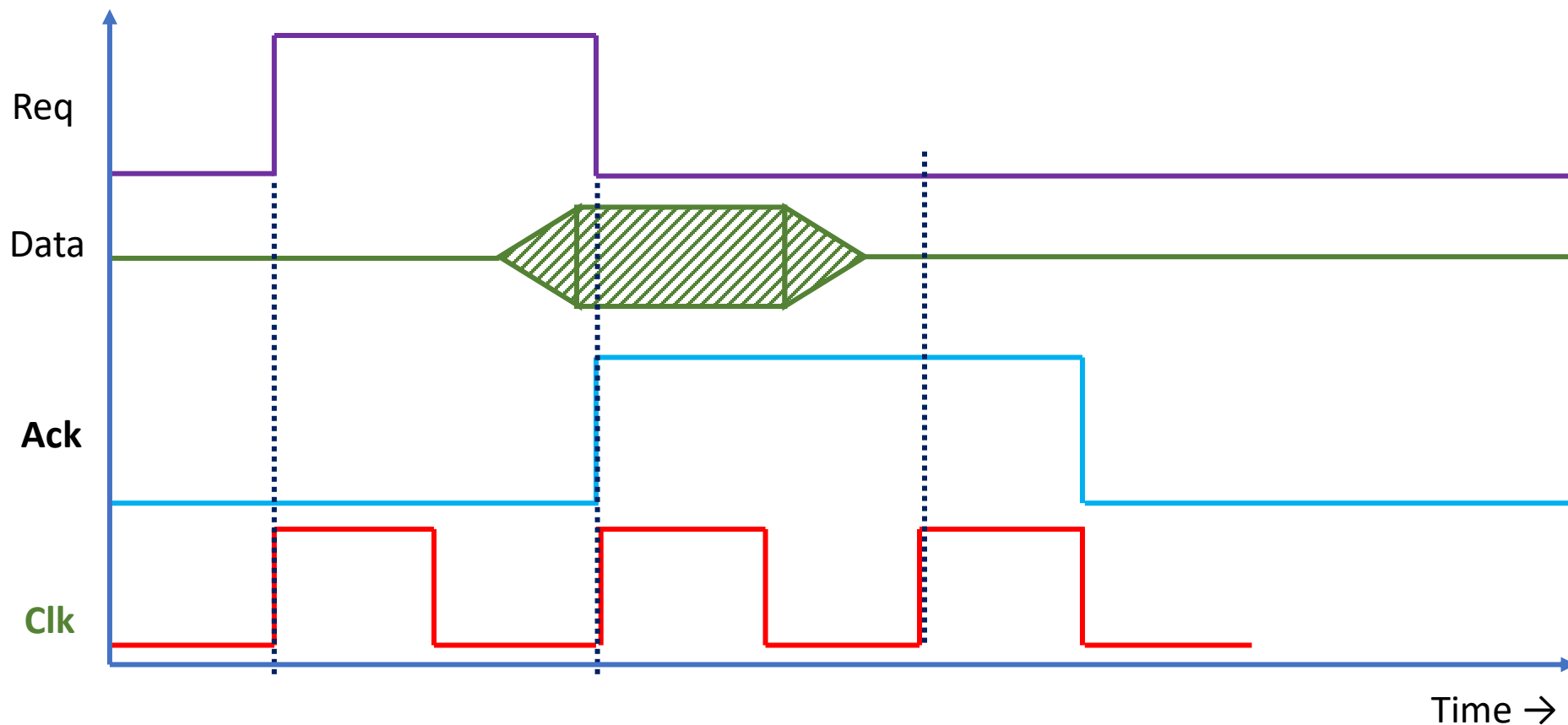

Req and Ack signals are synchronized to **Clk**


Synchronous Req with Wait Signaling

 


Slave can delay the Master by asserting Wait signal as it prepares the data and needs more clock cycles
 When the slave un-asserts Wait signal, it acknowledges that data is now available for the Master to read
 All interface signals are synchronized with Clock edge

Four Cycle Asynchronous Signaling

 RTZ – Return to Zero Signaling with No Clock




Two Cycle Asynchronous Signaling

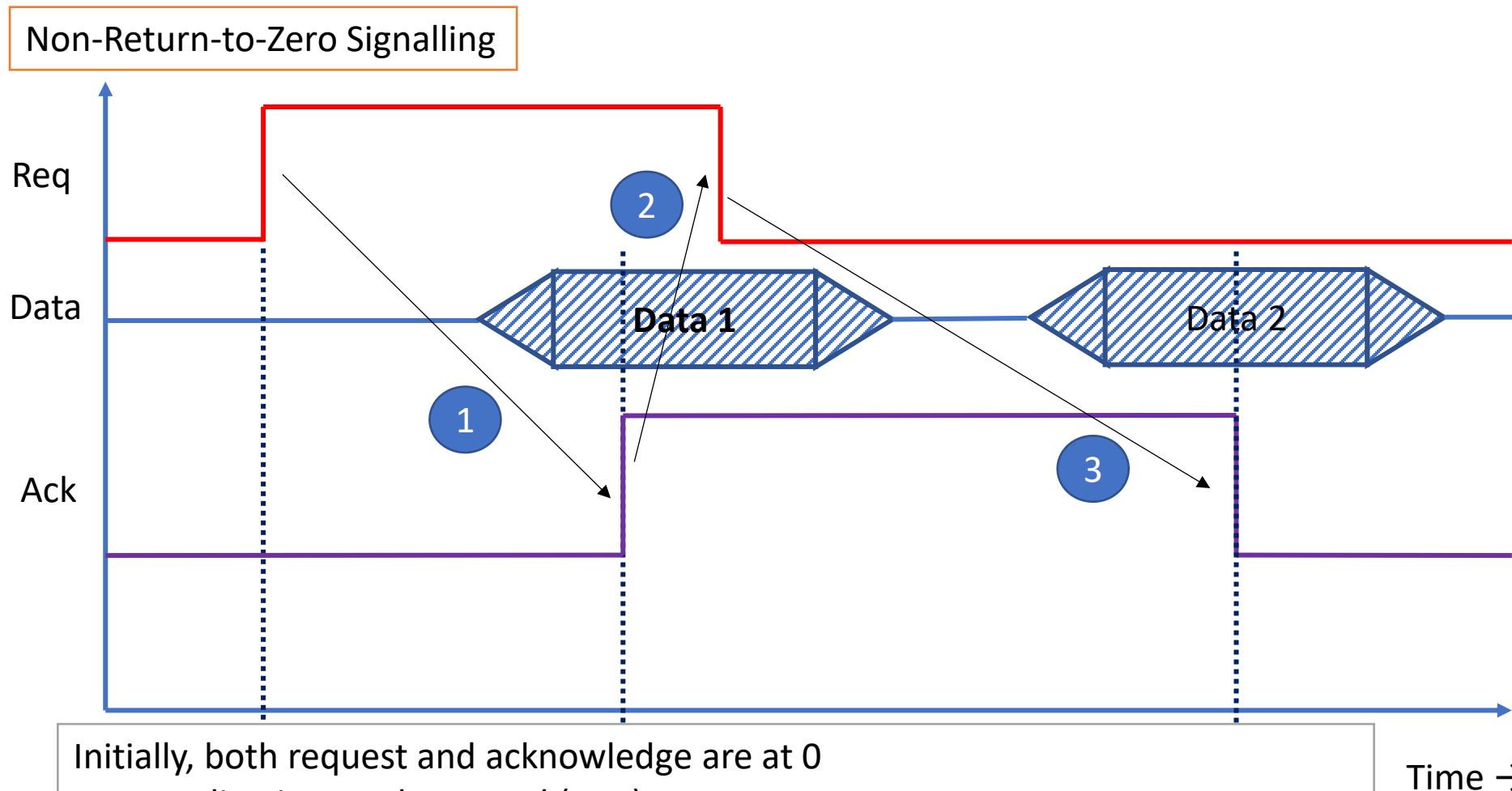

Initially, both request and acknowledge are at 0
 Request line is complemented (to 1)
 Slave notices change in Req, provides data, and complements the Ack line (to 1)
 Further request and acknowledgement is by complementing the respective state

Self-Timed Circuits

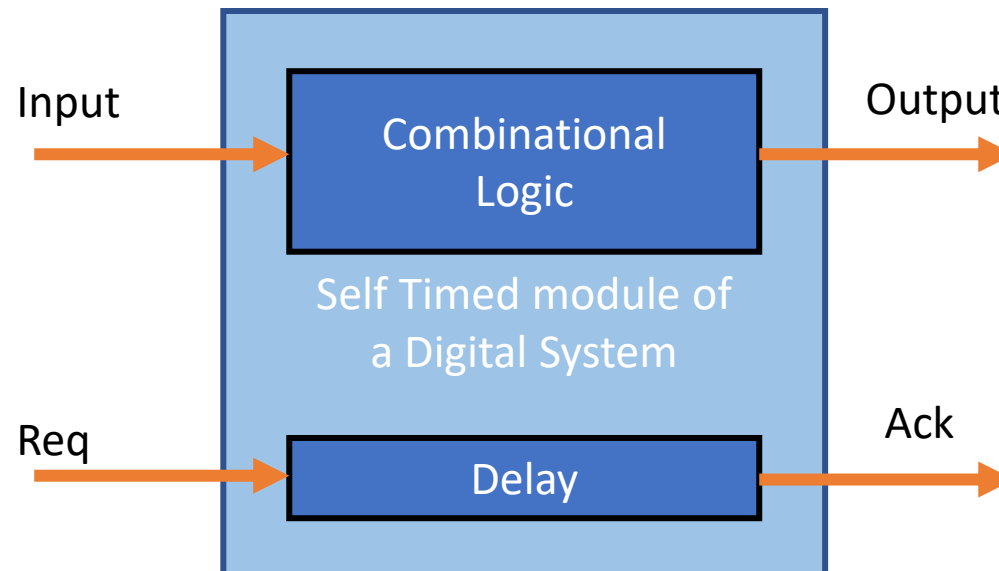- A self-timed circuit can determine on its own when a request has been serviced by mimicking the worst-case propagation delay path by using special logic to delay the request signal.
- This guarantees sufficient time to compute the correct output.



Computer Arithmetic

Study Data path and Control path of a binary hardware arithmetic unit

Computer Arithmetic Circuits


- Generally, the digital system design falls into one of the following categories:
 - **Data handling** – acquisition, storage, retrieval, compression, search, etc.
 - **Data processing** – filtering, de-noising, object detection, pattern recognition
- Computer Arithmetic is an important functional block of both aspects, especially plays an important part in Data Processing
- Efficient arithmetic circuits can improve the **speed – area – energy performance nexus** in a complex digital system

Basic Functional Block – Full Adder

X_i	Y_i	C_i	C_{i+1}	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\text{Sum } S_i = X_i \oplus Y_i \oplus C_i$$


 
$$C_{i+1} = X_i \cdot Y_i + C_i (X_i \oplus Y_i)$$



Full Adder Circuit

$$\text{Sum } S_i = X_i \oplus Y_i \oplus C_i$$
  
$$C_{i+1} = X_i \cdot Y_i + C_i (X_i \oplus Y_i)$$




$$C_{i+1} = X_i \cdot Y_i + C_i (X_i \oplus Y_i)$$

$$\text{Sum } S_i = X_i \oplus Y_i \oplus C_i$$

Multiple Bits – Ripple Carry Adder

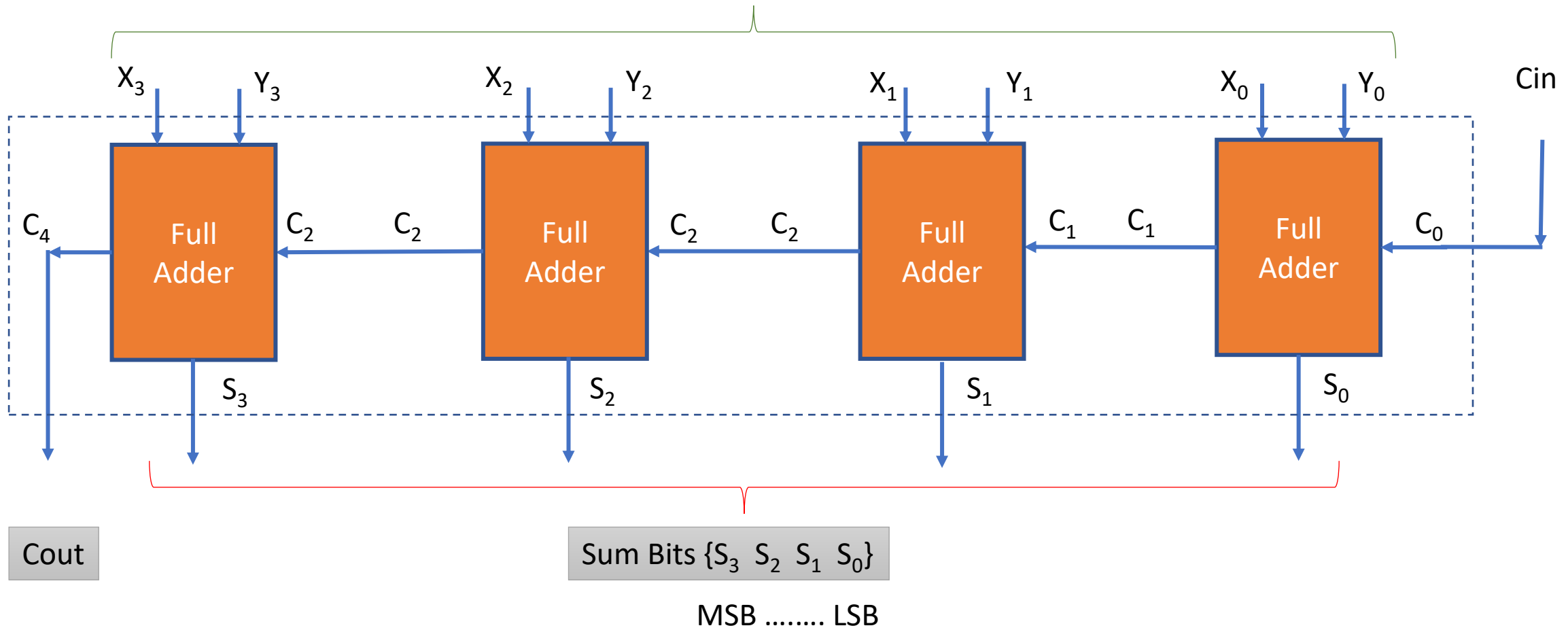Input Numbers $\{X_3 X_2 X_1 X_0\}$ and $\{Y_3 Y_2 Y_1 Y_0\}$, Carry Input at Cin



Timing Issues in Ripple Carry Adders

❖ Delay between Y_i and C_{i+1}
 = 1 EXOR + 1 AND + 1 OR (= Critical Path)


❖ Suppose delays through gates are:
 EXOR = 20ns, AND = 10ns, OR = 10ns

❖ Then Delay between Y_i and C_{i+1}
 = 20ns + 10ns + 10ns = 40ns


❖ Worst case delay through N adders
 = $N \times 40\text{ns}$

❖ For 32-bit data;
 Delay through 32-bit RCA =
 $32 \times 40\text{ns} = 1280\text{ns} = 1.28\mu\text{s}$

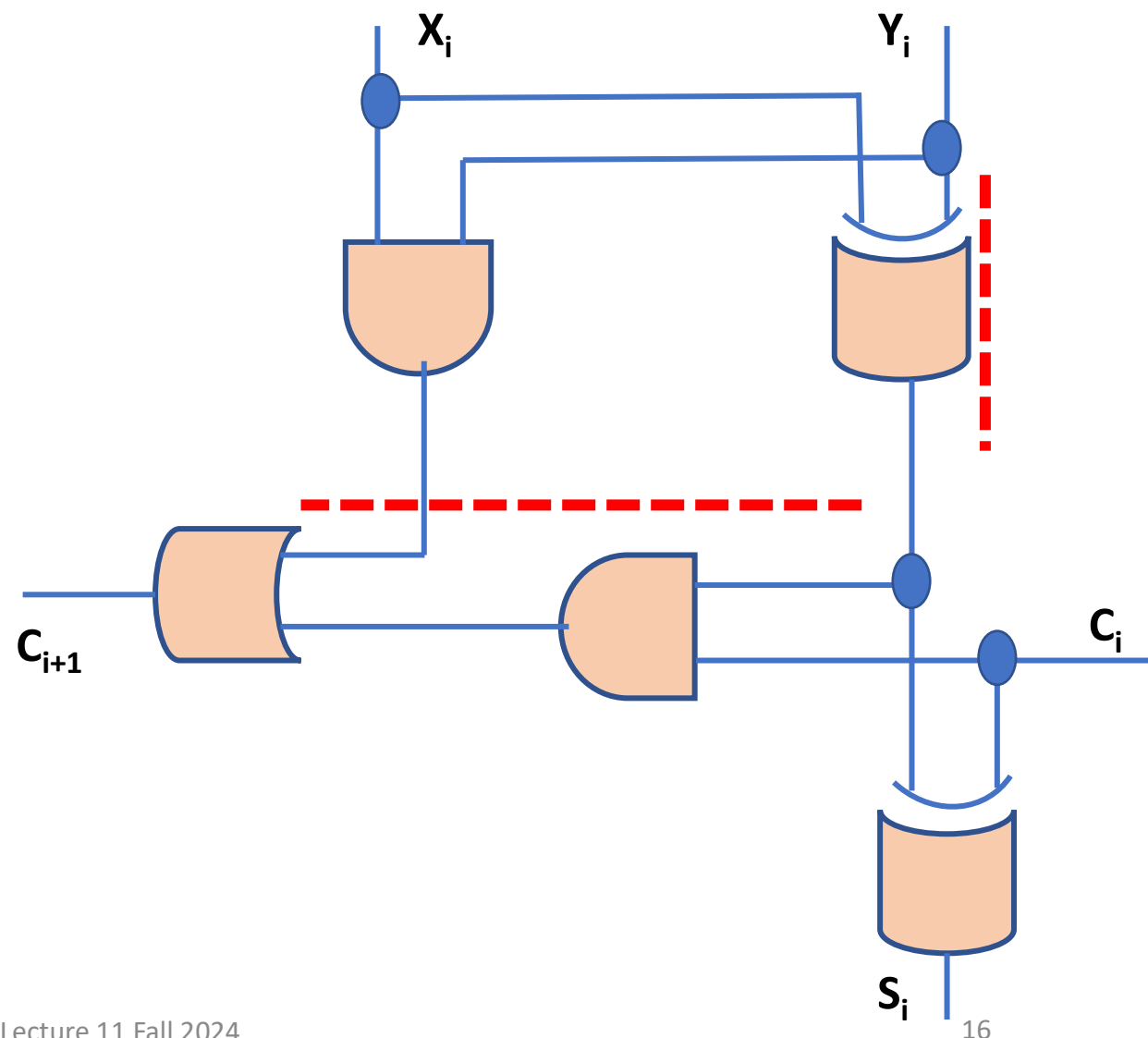❖ Corresponds to Maximum Data Throughput
 = $1/(1.28\mu\text{s}) = 0.78\text{ MHz}$ (too slow in today's terms)




Delay of Ripple Carry Full Adder

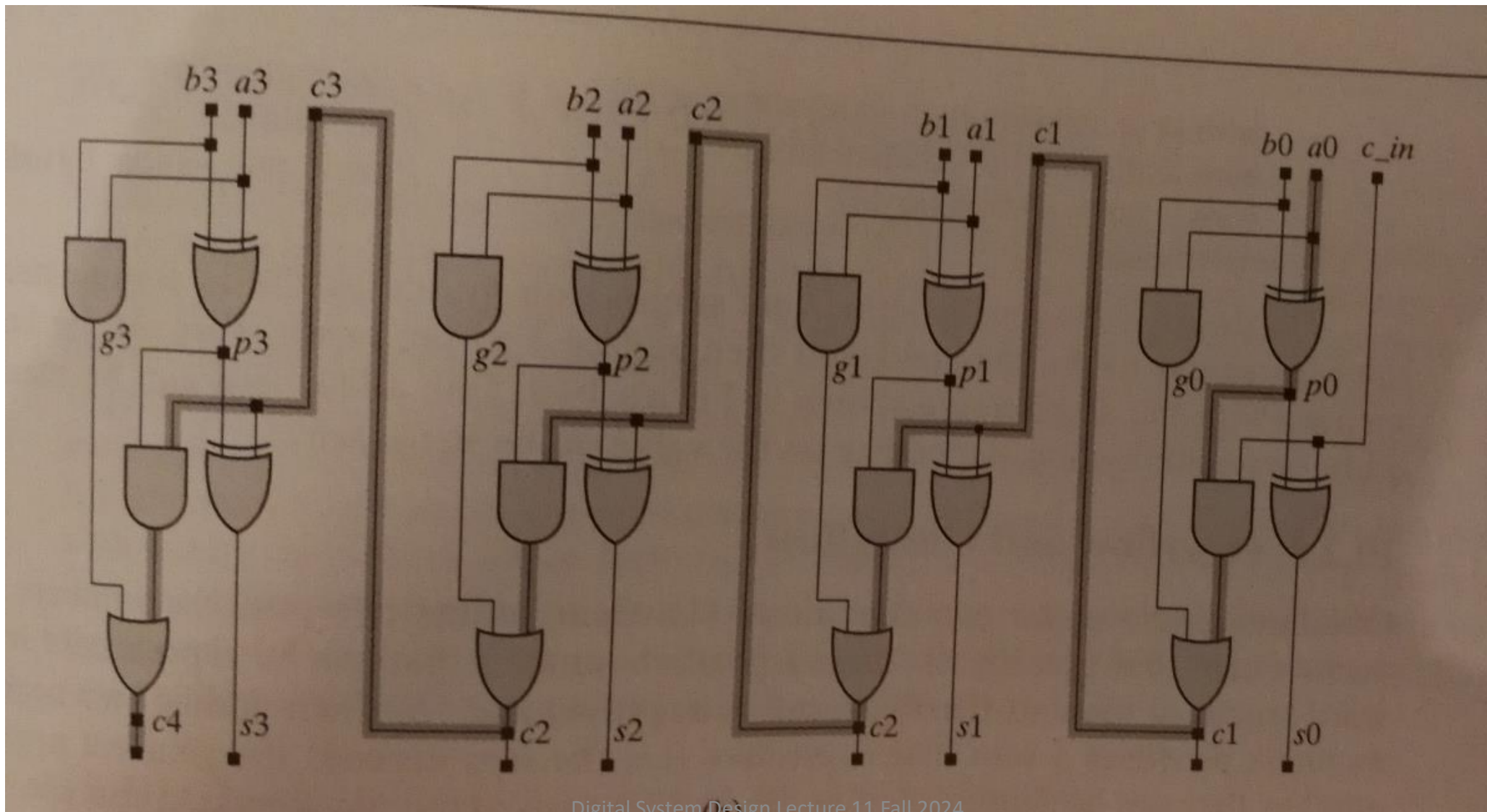


Compare with Critical Path of Full Adder

REVIEW

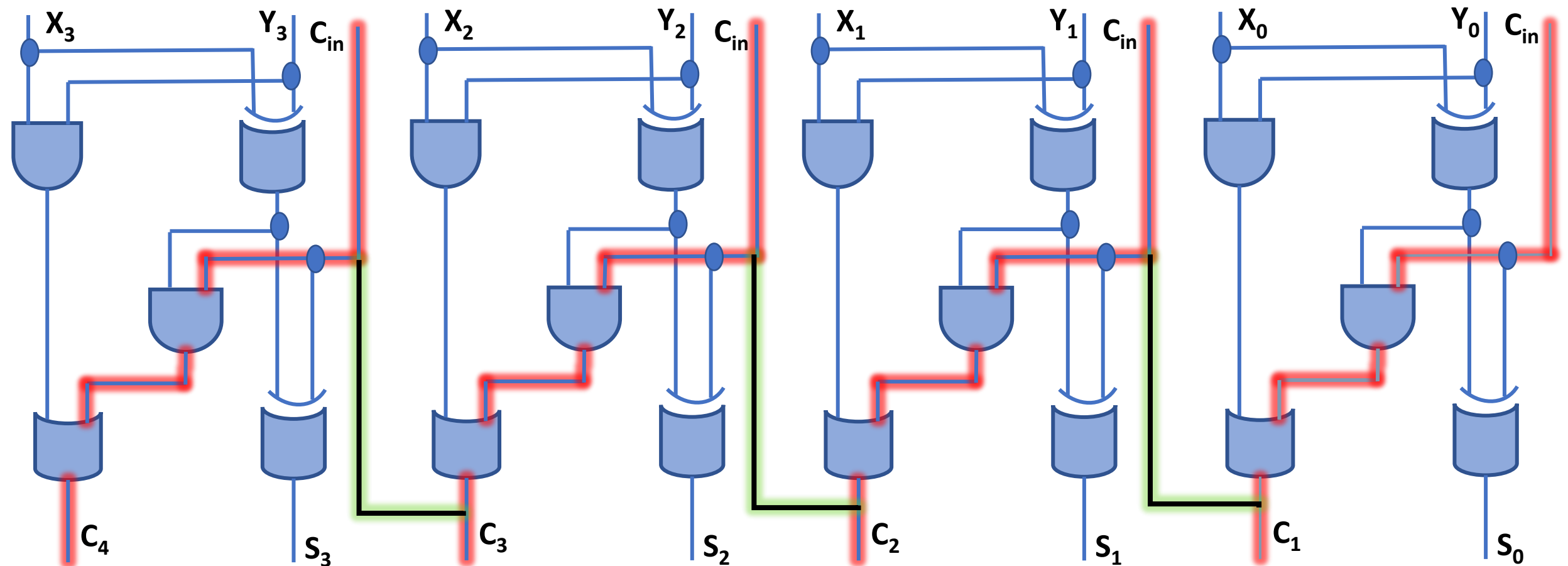

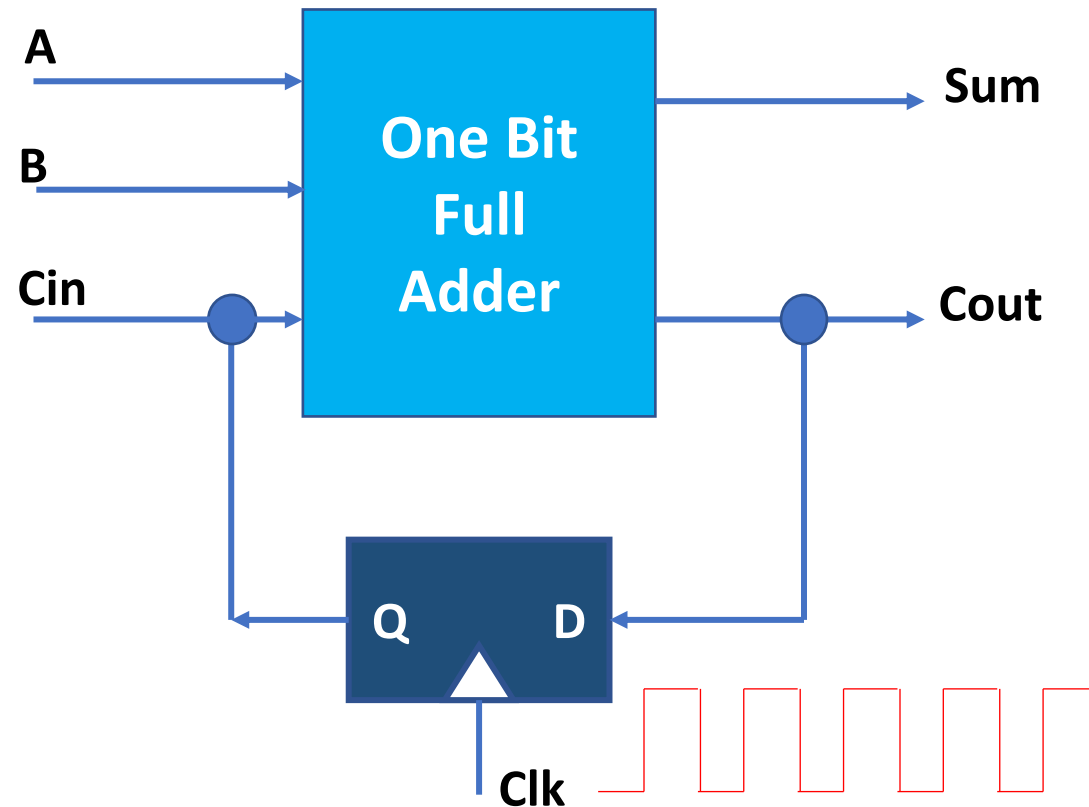
Multi-bit Adder – Using 1-Bit Serial Adder



All inputs and outputs are one-bit

What is the **Critical Path**?
 And **Maximum Delay**?
 And **Maximum Throughput**?

8-Bit, Bit-Serial Full Adder

 

All inputs and outputs are one-bit

What is the Critical Path?
And Maximum Delay?
And Maximum Throughput?

Timing Considerations in Bit-Serial Design

- It is an extreme example of a **pipelined** design
- What is **Critical Path**?
- What is **Latency**?
- What is **Data Throughput**?
- What is **maximum clock speed achievable**?

Definitions related to timing performance

- **Latency:** Amount of time before the appearance of first correct output
- **Throughput:** Amount of processed data available at the output port, per unit time
- **Critical Path:** The combinational logic path with maximum number of circuit elements that the input travels before reaching the output
- **Maximum Achievable Clock Speed:** Limited by Critical Path

Carry Lookahead Adder

Carry Lookahead Adder – A type of fast adder

- In Ripple Carry Adder, the Carry Input C_{in} propagates through all Adder circuits before reaching the final Carry Out, C_{out} . Thus, there is a Long carry chain that makes the Critical Path worse.
- In Carry Lookahead Adder (CLA), the Carry Circuit is separated from the Sum circuit and both work independently. This reduces the number of gates in Critical Path and the Adder can work faster.

Basic Functional Block – Full Adder

Truth Table of 1-Bit Full Adder

A_i	B_i	C_i	C_{i+1}	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Boolean Expressions for Sum and Carry Out

$$\text{Sum } S_i = A_i \oplus B_i \oplus C_i$$

$$C_{i+1} = A_i \cdot B_i + C_i (A_i \oplus B_i)$$

Boolean Algebra formulation of Sum and Cout in Carry Lookahead Adder

Define bits as follows:

A_i and B_i are data bits at i^{th} cell of the adder

C_i is the carry in into the i^{th} cell

S_i is Sum output bit of the i^{th} cell

C_{i+1} is the Carry Out of the i^{th} cell

Define two signals generate G_i and propagate P_i :

$$G_i = A_i \cdot B_i$$

$$P_i = A_i \oplus B_i$$

$$S_i = (A_i \oplus B_i) \oplus C_i$$

Also

$$S_i = P_i \oplus C_i$$

$$\text{Carry Out} = C_{i+1}$$

$$C_{i+1} = ((A_i \oplus B_i) \oplus C_i) + (A_i \cdot B_i)$$

Also

$$C_{i+1} = (P_i \cdot C_i) + G_i$$

$$\text{Sum } S_i = A_i \oplus B_i \oplus C_i$$

$$C_{i+1} = A_i \cdot B_i + C_i (A_i \oplus B_i)$$

Algorithmically:

$$S_i = P_i \oplus C_i$$

And

$$C_{i+1} = (P_i \cdot C_i) + G_i$$

Carry Look Ahead Boolean Equations – S0, S1

$$S_0 = P_0 \oplus C_0$$

$$C_1 = (P_0 \cdot C_0) + G_0$$

$$S_1 = (P_1 \oplus C_1)$$

$$= P_1 \oplus ((P_0 \cdot C_0) + G_0)$$

$$C_2 = (P_1 \cdot C_1) + G_1$$

$$C_2 = (P_1 \cdot P_0 \cdot C_0) + (P_1 \cdot G_0) + G_1$$

$$\text{where } C_1 = (P_0 \cdot C_0) + G_0$$

Carry Lookahead Boolean – S2, C3

$$S_2 = P_2 \oplus C_2$$

$$S_2 = P_2 \oplus [P_1 \cdot P_0 \cdot C_0 + P_1 \cdot G_0 + G_1]$$

$$C_3 = P_2 \cdot C_2 + G_2$$

$$= P_2 \cdot [P_1 \cdot P_0 \cdot C_0 + P_1 \cdot G_0 + G_1] + G_2$$

$$C_3 = P_2 \cdot P_1 \cdot P_0 \cdot C_0 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot G_1 + G_2$$

Carry Lookahead Boolean – S3 and C4

$$S_3 = P_3 \oplus C_3$$

$$S_3 = P_3 \oplus [P_2 \cdot P_1 \cdot P_0 \cdot C_0 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot G_1 + G_2]$$

$$C_4 = (P_3 \cdot C_3) + G_3$$

$$C_4 = P_3 \cdot [P_2 \cdot P_1 \cdot P_0 \cdot C_0 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot G_1 + G_2] + G_3$$

Recap:

Define two signals generate G_i and propagate P_i :

$$G_i = A_i \cdot B_i$$

$$P_i = A_i \oplus B_i$$

$$S_i = (A_i \oplus B_i) \oplus C_i$$

Also

$$S_i = P_i \oplus C_i$$

$$\text{Carry Out} = C_{i+1}$$

$$C_{i+1} = ((A_i \oplus B_i) \oplus C_i) + (A_i \cdot B_i)$$

Also

$$C_{i+1} = (P_i \cdot C_i) + G_i$$

Since $C_{i+1} = G_i + P_i \cdot C_i$, therefore:

$$C_1 = G_0 + P_0 \cdot C_0$$


$$C_2 = G_1 + P_1 \cdot C_1$$

$$C_3 = G_2 + P_2 \cdot C_2$$

$$C_4 = G_3 + P_3 \cdot C_3$$

The Carry Out at any stage can be generated from P_i , G_i and C_0 ;
Without waiting for carry to ripple through all the previous stages

Block Diagram of 4-Bit CLA

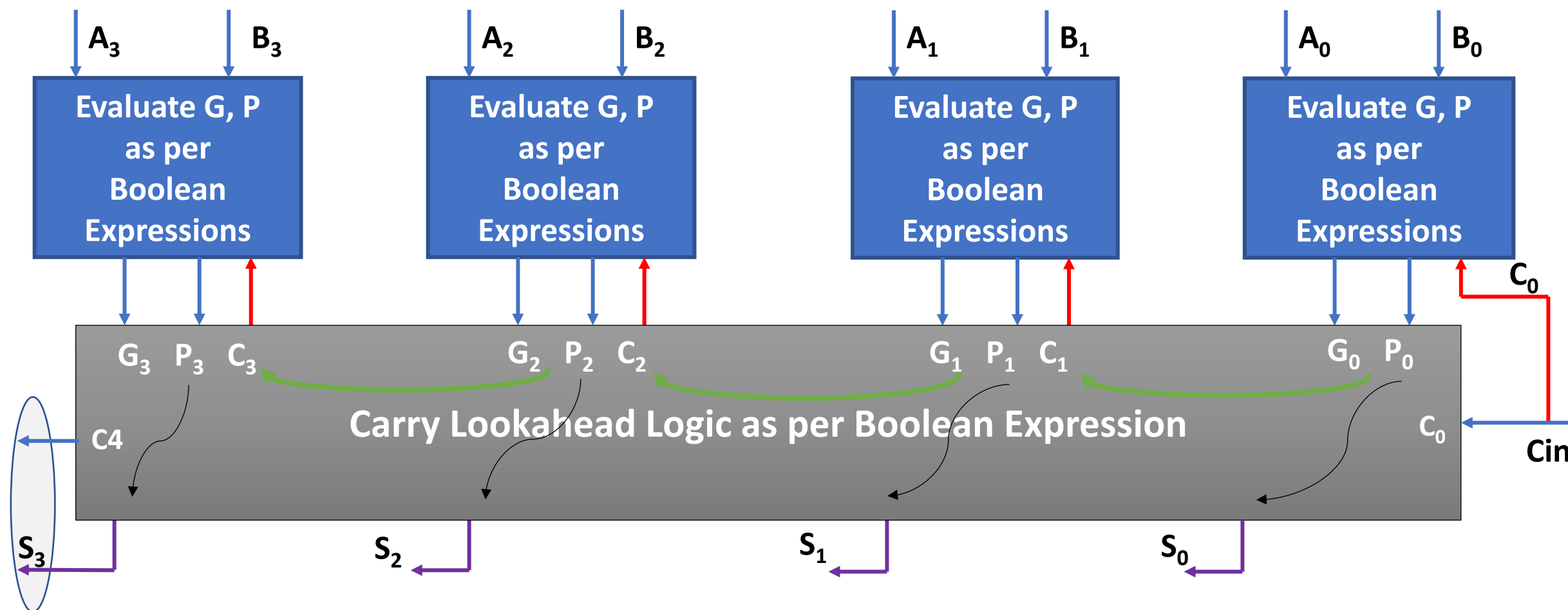

Delay of 4-Bit CLA Adder

**4-Bit CLA Adder
Showing Critical Path**

Estimate Maximum Clock Speed?


 



Diagram from Ciletti course text book

Compare with Critical Path of Full Adder

REVIEW

 


Compare with Critical Path of Full Adder

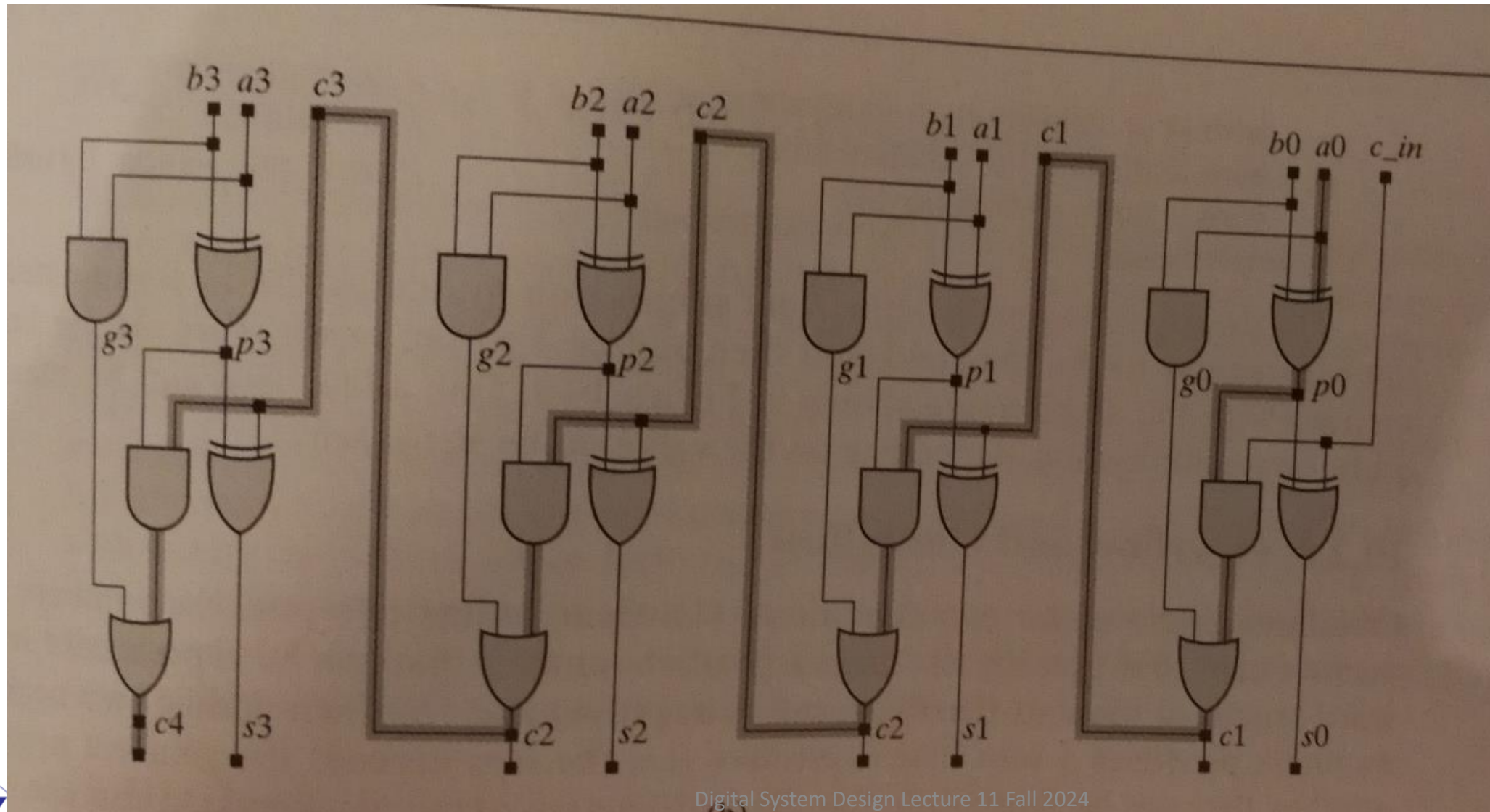


2 Level CLA Generation

2 Levels of look ahead

no rippling
of carry

 

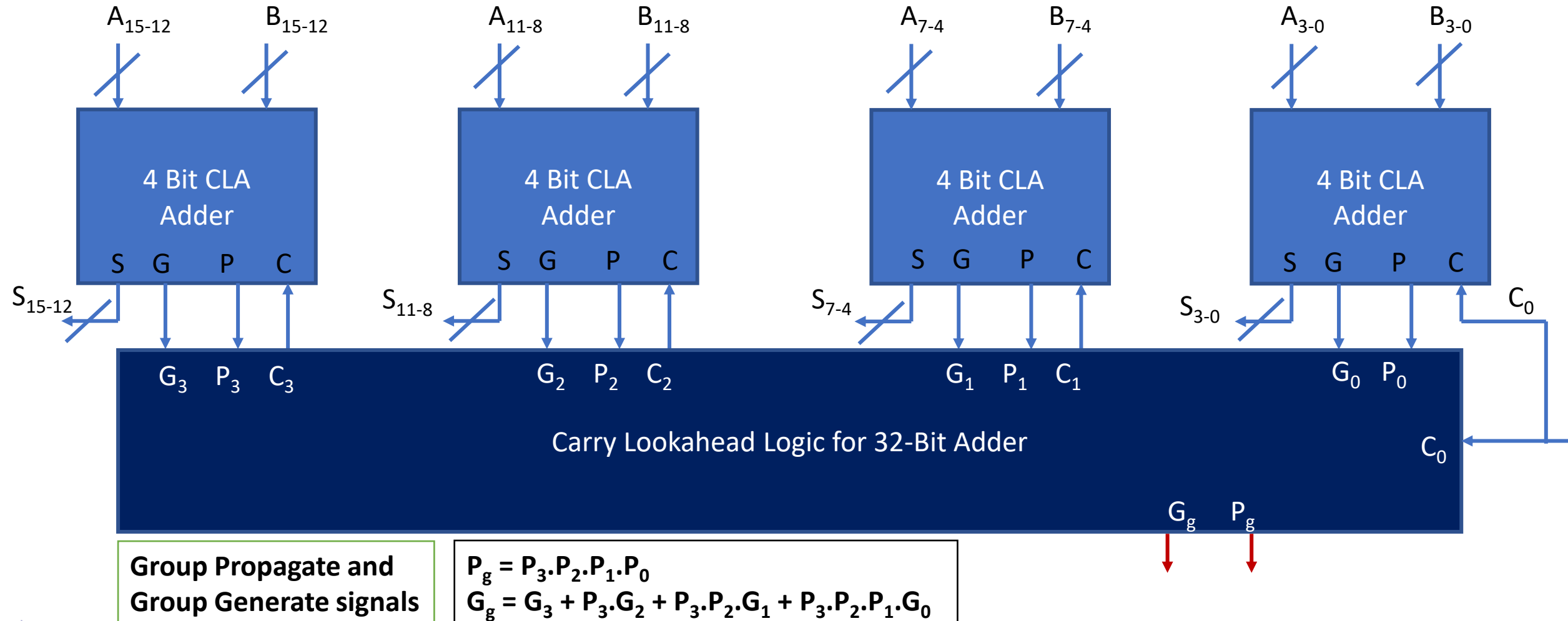
16-Bit CLA – Gates with many inputs needed?



Carry Select Adder

Carry Select Adder - Principle


Carry-Select Adder

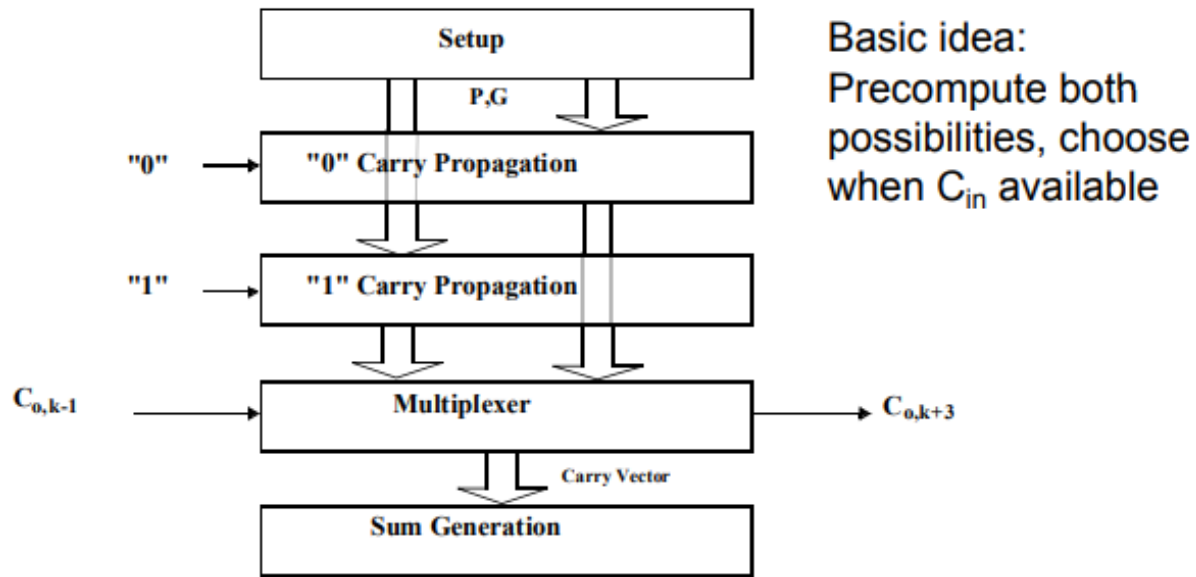

EECS 427 F08


Lecture 7

24

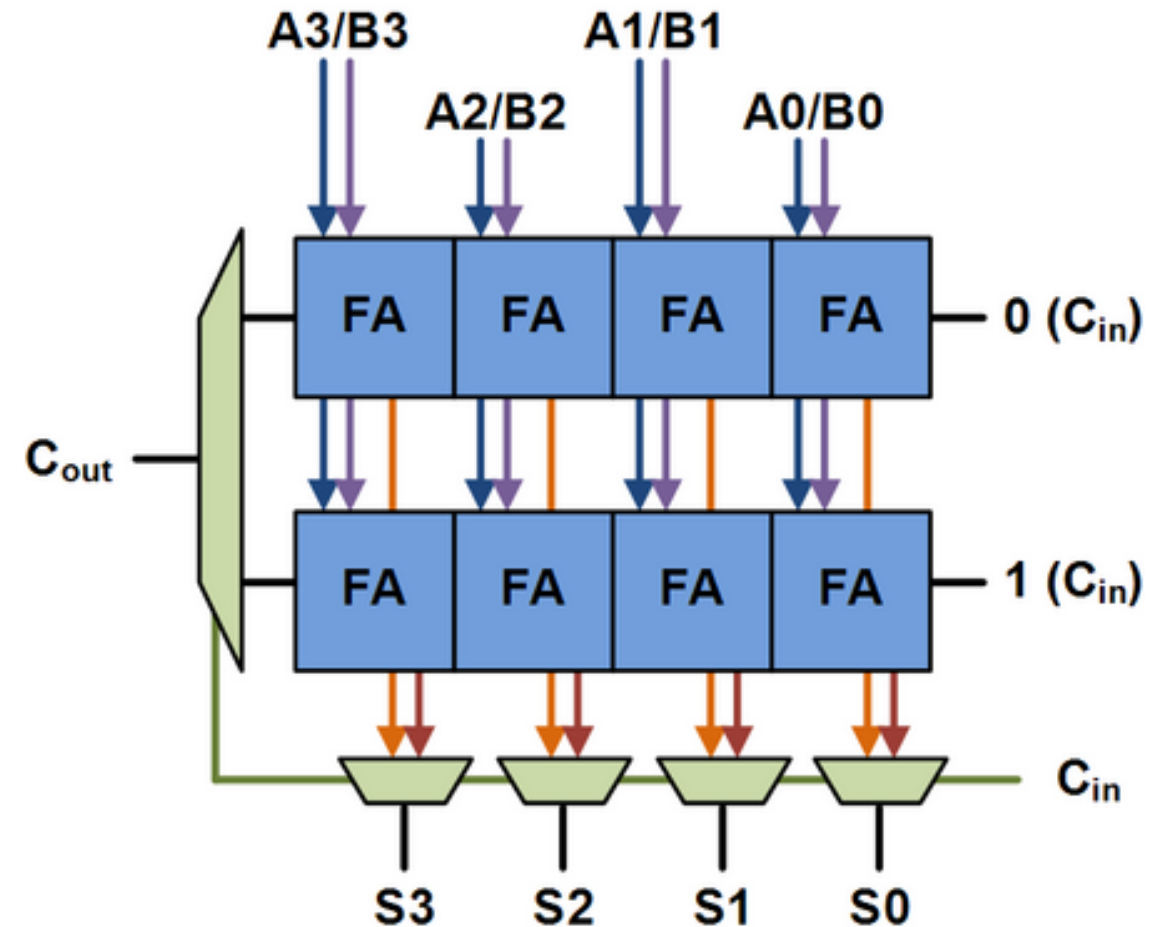


Ref: https://en.wikipedia.org/wiki/Carry-select_adder

Carry Select Adder – Uniform Size Adders

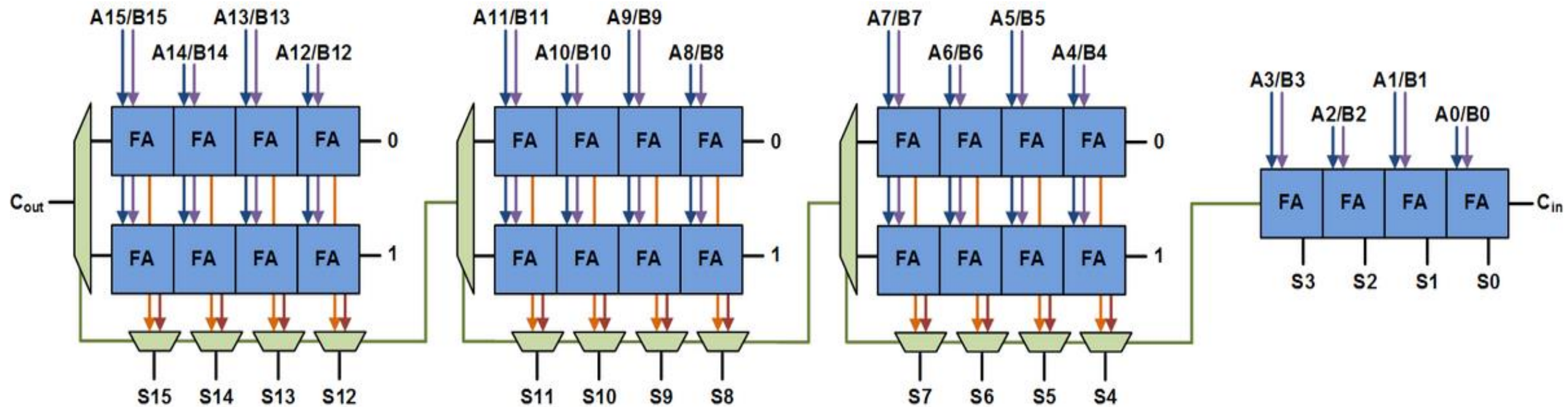


 Carry Select Adder – Variable Size Adders



Carry Select Adder Critical Path

Carry Select Adder: Critical Path

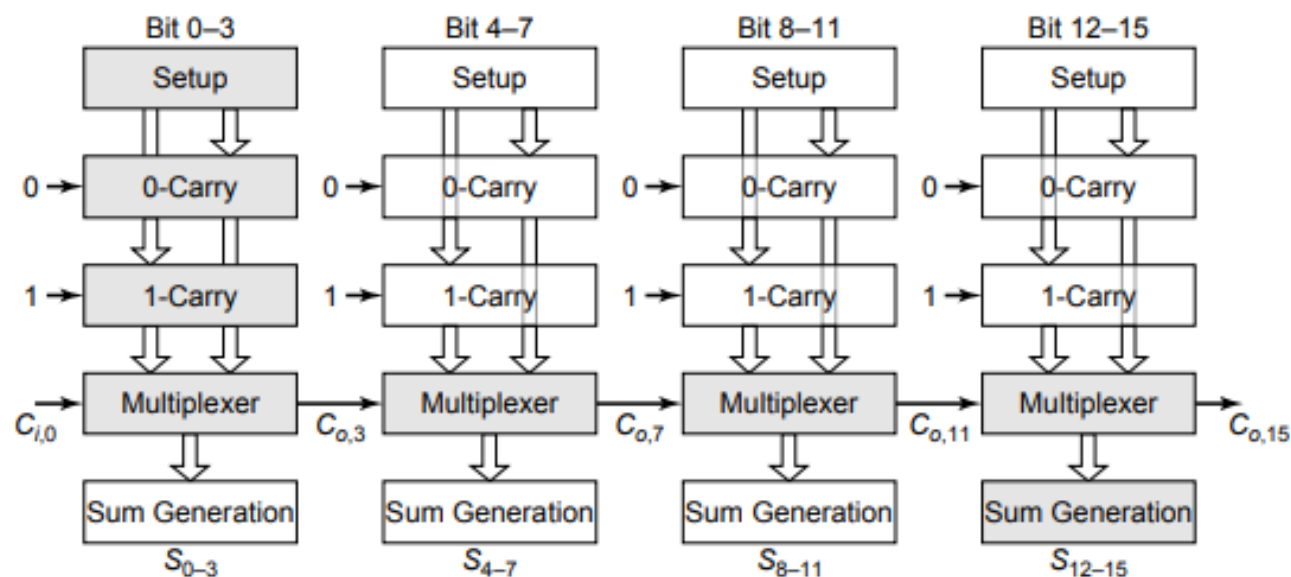



$$t_{add} = t_{setup} + Mt_{carry} + (N/M)t_{mux} + t_{sum}$$

Carry Select Adder

Carry Select Adder

For a group Sum &
Carry is already
calculated

Simply select based on
carry

 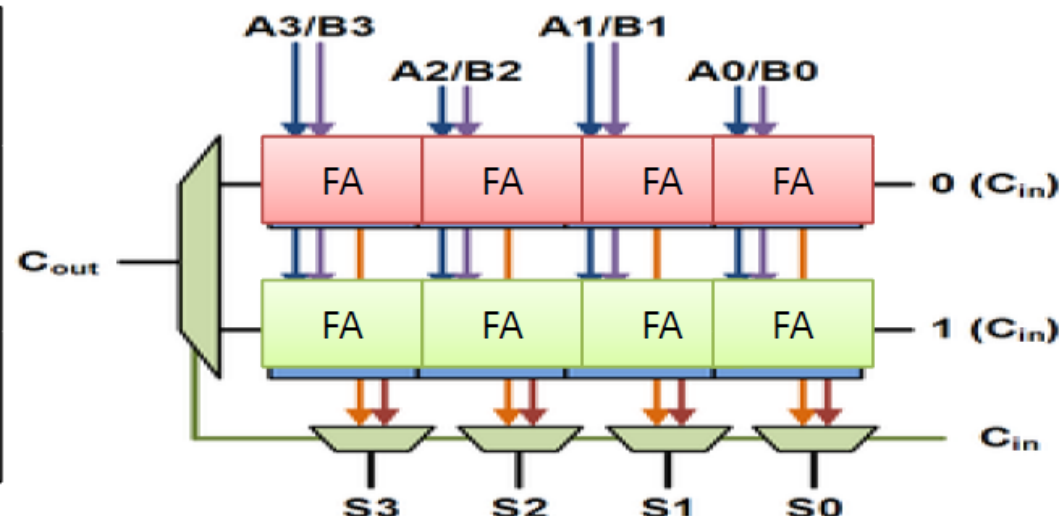

16