

Lecture 18

EE 421 / CS 425

Digital System Design

Fall 2024

Shahid Masud

Topics

- Floating Point Adder and Multiplier Operation
- Digital Circuit Design for Floating Point Module
- Introduction to Programmable Logic Hardware Device
- Nomenclature and types
- Logic Array Circuits
- PLA and PAL
- Programmable Logic Devices – PLD

Floating Point Arithmetic – Digital Design


$$N = (-1)^S \times (1+F) \times 2^E$$

E.g. $91.820734 \times 10^{-34}$


- ❖ A signed-magnitude system for the fractional part and a biased notation for the exponent
- ❖ Three subfields
 - ❖ Sign S
 - ❖ Fraction F (or Significand or Mantissa)
 - ❖ Exponent E
- ❖ Sign bit is 0 for positive numbers, 1 for negative numbers
- ❖ Fractions always start from **1**.xxxx, hence the integer **1** is not written (register has xxxx)
- ❖ Exponent is biased by +127 (add 127 to whatever is in register bits)
- ❖ Normalize: Express numbers in the standard format by shifting of bits and adding / subtracting from Exponent register

IEEE 754 Floating Point Representation

Single Precision IEEE 754

 

Double Precision IEEE 754

 

Examples of Floating Point Representation

$-(13.45)_{10}$
 $= (1101.01\ 1100\ 1100\ 1100\ \dots)^2$; this is un-normalized
 $= (1.10101\ 1100\ 1100\ 1100\ 1) \times 2^3$; normalized
 Fraction part is 10101 1100 1100 1100 1
 Biased Exponent is $3+127 = 130$
 Sign = 1

5.0345
 $= 101.0000\ 1000\ 1101\ 0100\ 1111\ 110$; this is un-normalized
 $= 1.01\ 0000\ 1000\ 1101\ 0100\ 1111\ 110 \times 2^2$; normalized
 Biased Exponent = $2+127 = 129 = (1000\ 0001)_2$
 Fraction = 01 0000 1000 1101 0100 1111 110
 Sign = 0

Floating Point Multiplication

Consider two floating point numbers:
 $(F_1 \times 2^{E1})$ and $(F_2 \times 2^{E2})$

The product of these two numbers is:
 $= (F_1 \times 2^{E1}) \times (F_2 \times 2^{E2})$
 $= (F_1 \times F_2) \times 2^{(E1+E2)}$
 $= F \times 2^E$

Sign of result depends on Sign of the two numbers

Floating Point Multiplication Steps

1. Normalize the two numbers if not done already
2. The exponents of the Multiplier (E1) and the multiplicand (E2) bits are added and the base value is subtracted from the added result; The subtracted result is put in the exponential field of the result block $\rightarrow E1+E2-\text{bias}$
3. Multiply the two fractions (or significands)
4. S1, the signed bit of the multiplicand is XOR'd with the multiplier signed bit of S2. The result is put into the resultant sign bit.
5. The mantissa of the Multiplier (M1) and multiplicand (M2) are multiplied and the result is placed in the resultant field of the mantissa (truncate/round the result for 24 bits) $\rightarrow M1 * M2$
6. If the product is 0, adjust the proper representation of answer to 0
7. If the product fraction is too big, Normalize by shifting it right and incrementing the exponent
8. If the product fraction is too small, Normalize by shifting left and decrementing the exponent
9. Round to appropriate number of bits. If rounding results in loss of Normalization, then first Normalize and then do the rounding
10. If an exponent underflow (below -127) or overflow (above +127) occurs then generate an error condition

Bit-widths required

- Multiply the mantissa values including the hidden (guard) bits in rounding register. The resultant product of the 24 bits mantissas (M1 and M2) is 48 bits (2 bits are to the left of binary point)
- 8 bit adder (subtractor) needed for Exponent

Floating Point Multiplier Block Diagram - Example

Definitions:

St: Start of Floating Point multiplication operation

Mdone: Fraction multiplication is complete

FZ: Fraction is Zero

FV: Fraction overflow (too small or too big)

Fnorm: F is normalized

EV: Exponent overflow

Load: Load F1, E1, F2, E2 into respective registers

Adx: Add Exponent; also start of multiplication


SM8: Set exponent to -8 to handle special case of 0

RSF: Shift fraction right; also increment E


LSF: Shift fraction left; also decrement E

V: overflow indicator

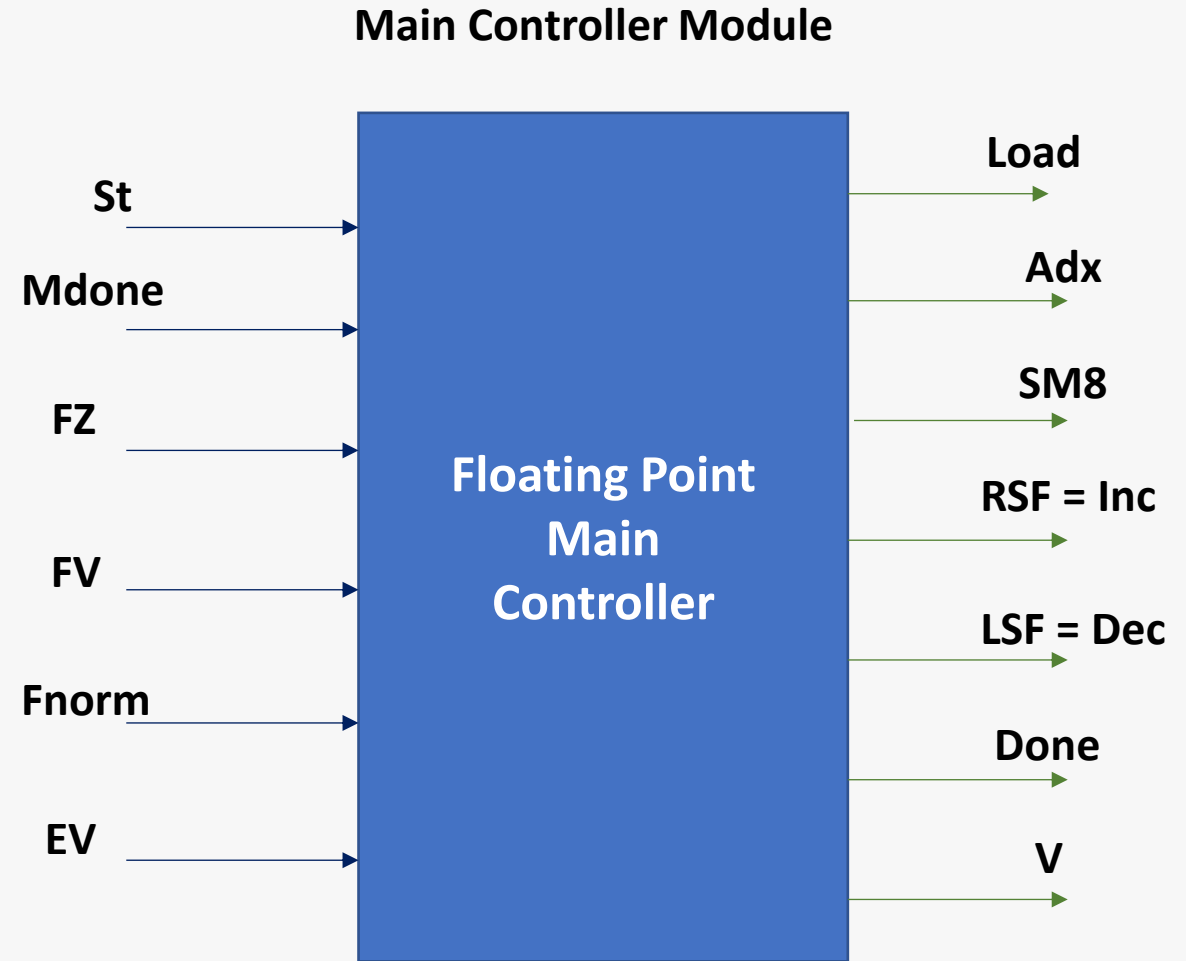Done: Floating Point multiplication is complete



Data Path of Floating Point Multiplier

 

Operation Details of Datapath

Pre Normalize Block for Adder and Subtractor : Calculate the difference between the smaller and larger exponent. Adjust the smaller fraction by right shifting it, determine if the operation is an add or subtract after resolving the sign bits. Check for NaNs on inputs.

Pre Normalize Block for Multiplication: Computes the sum/difference of exponents, checks for exponent overflow, underflow condition and INF value on an input.

Post Normalize and Round Unit - Normalize fraction and exponent. Also do all the roundings in parallel and then pick the output corresponding to the chosen rounding mode.

Exceptions Unit – This unit Generates the exception signals like sNaN, qNaN, Inf and Ine The IEEE standard defines two classes of NaNs(non numbers): i. quiet NaNs (qNaNs) : A qNaN is a NaN with the most significant fraction bit set. ii. signaling NaNs (sNaNs): A sNaN is a NaN with the most significant fraction bit clear.

The single precision floating point format is divided into three main parts corresponding to the sign , exponent and mantissa.

Multiplication of the two operands is done in three parts and thereby obtaining the Product.

The first part of the product which is the sign is determined by an exclusive OR function of the two input signs.

The exponent of the product which is the second part is calculated by adding the two input exponents. The third part which is the significand of the product is determined by multiplying the two input significands each with a '1' concatenated to it.

11

A multiplication of two floating-point numbers is done in four steps: • non-signed multiplication of mantissas: it must take account of the integer part, implicit in normalization. The number of bits of the result is twice the size of the operands (48 bits). • normalization of the result, the exponent can be modified accordingly . • addition of the exponents, taking into account the bias. • calculation of the sign.

Programmable Logic Reconfigurable Logic


Definition of Programmable Logic

- A family of semiconductor integrated circuits that can be reconfigured through:
 - special hardware-description-languages, and
 - associate Electronic Design Automation tools
 - Special configuration equipment

to produce a variety of hardware functionality from the same integrated circuit chip.

- The functionality in hardware can be erased and reconfigured in a manner analogous to design of a software system using microprocessor.
- All other types of semiconductors have fixed and pre-defined functionality.
- Performance vs Flexibility tradeoffs exist, as with any other digital system.

Programmable Logic Broad Classification

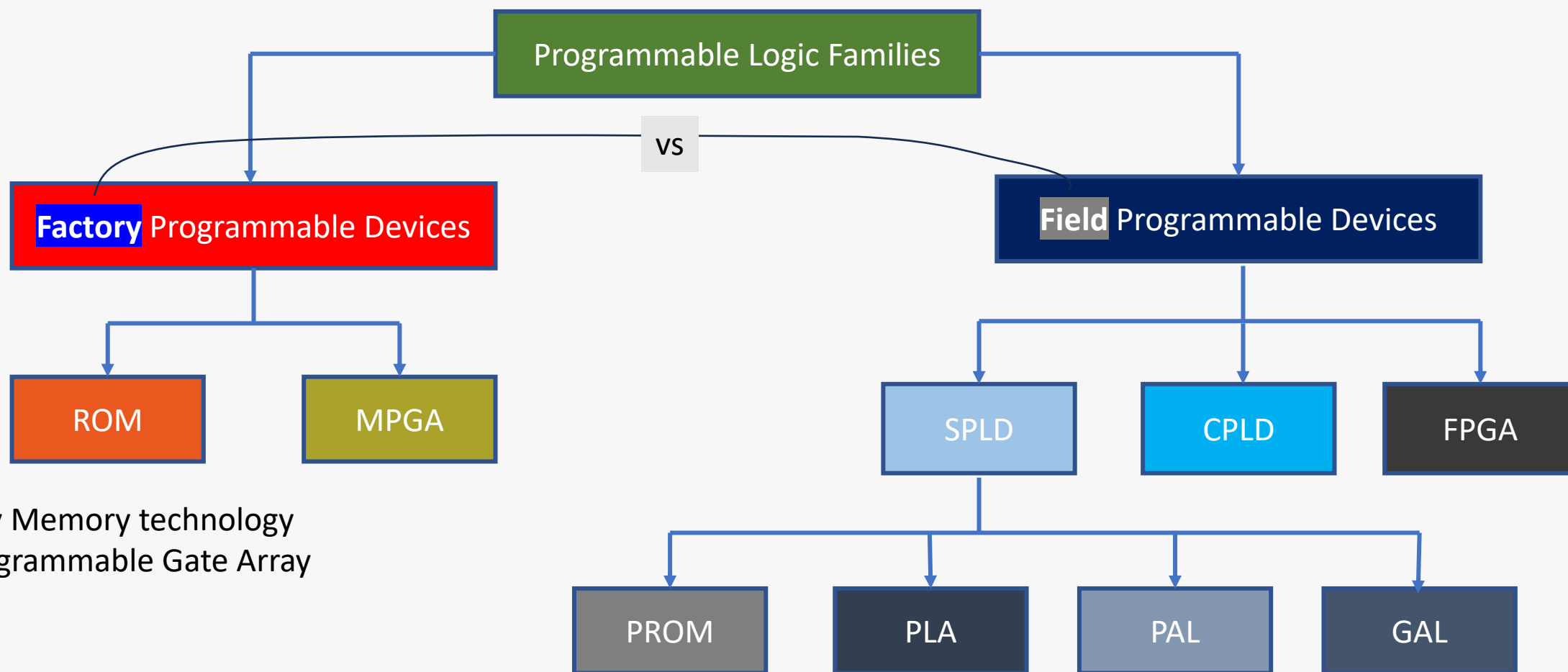


Read only Memory technology
Mask Programmable Gate Array

Simple and Complex Programmable Logic Devices


Field Programmable Gate Array

Generic Array Logic (complex PAL by lattice semi), Programmable Logic Array

Diode – Principle of operation

 


Forward Biased

 

Reverse Biased



Diode in logic gates

 

**When A=1, Diode is Reverse Biased
Hence Output Y = 1 through +VDD**


**When A=0, Diode is Forward Biased
Hence Output Y = 0 through A = 0 Volt**

Diode based AND Logic Array

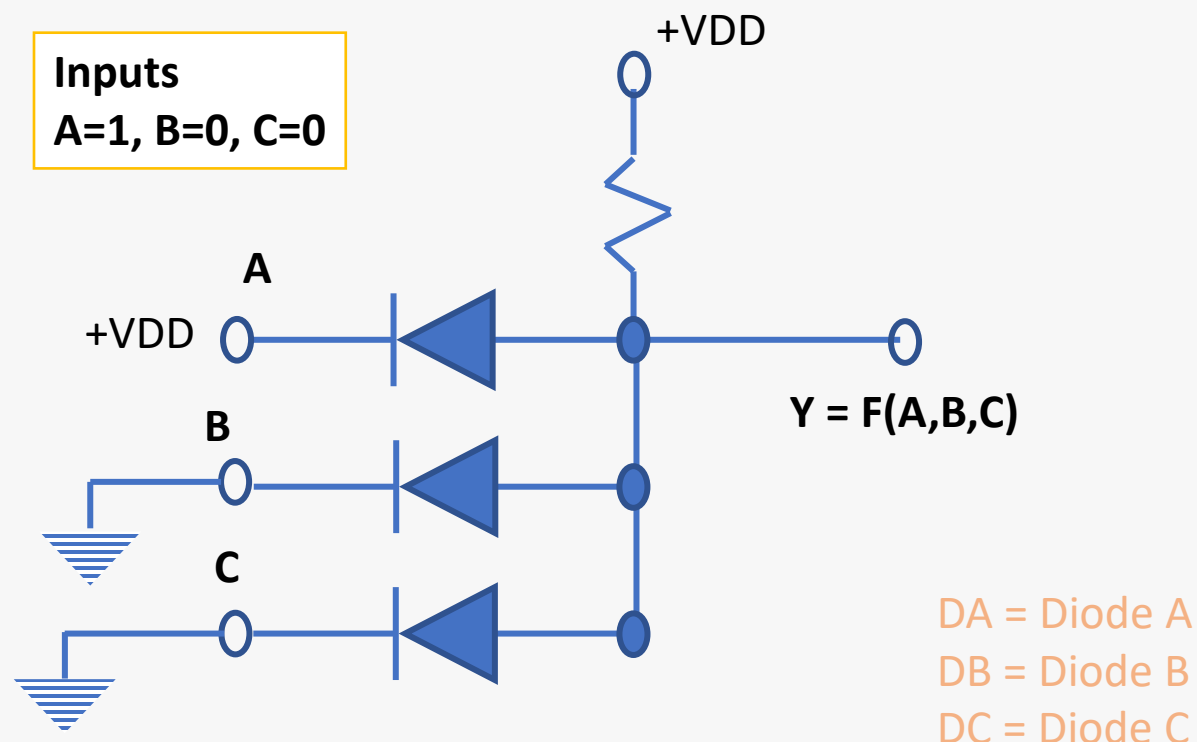 


DA=Open Circuit, DB = Forward Biased Short, DC = Forward Biased Short
Y= Logic '0' as it is Shorted to Zero due to DB or DC

Diode based OR array

 


Inputs A = 0, B = 1, C = 0

 

DA and DC = Open Circuit due to Zero input, DB = Short Circuit due to +VDD input
Y = +VDD Logic '1' due to DB being short circuit, other paths are open circuit

Diode based AND-OR Array

 

Diode as fuse


Momentarily apply a higher voltage where open circuit path is required



Desired paths from AND gates and OR gates will be retained, others will be blown out



Desired Paths are selected through a MASK during final stages of FABRICATION PROCESS

MOS Transistor as Switch

 


Programming is achieved through controlling GATE Voltage
 High GATE Voltage will ensure flow of current, like a short circuit
 Low GATE Voltage will ensure no flow of current, like an open circuit

 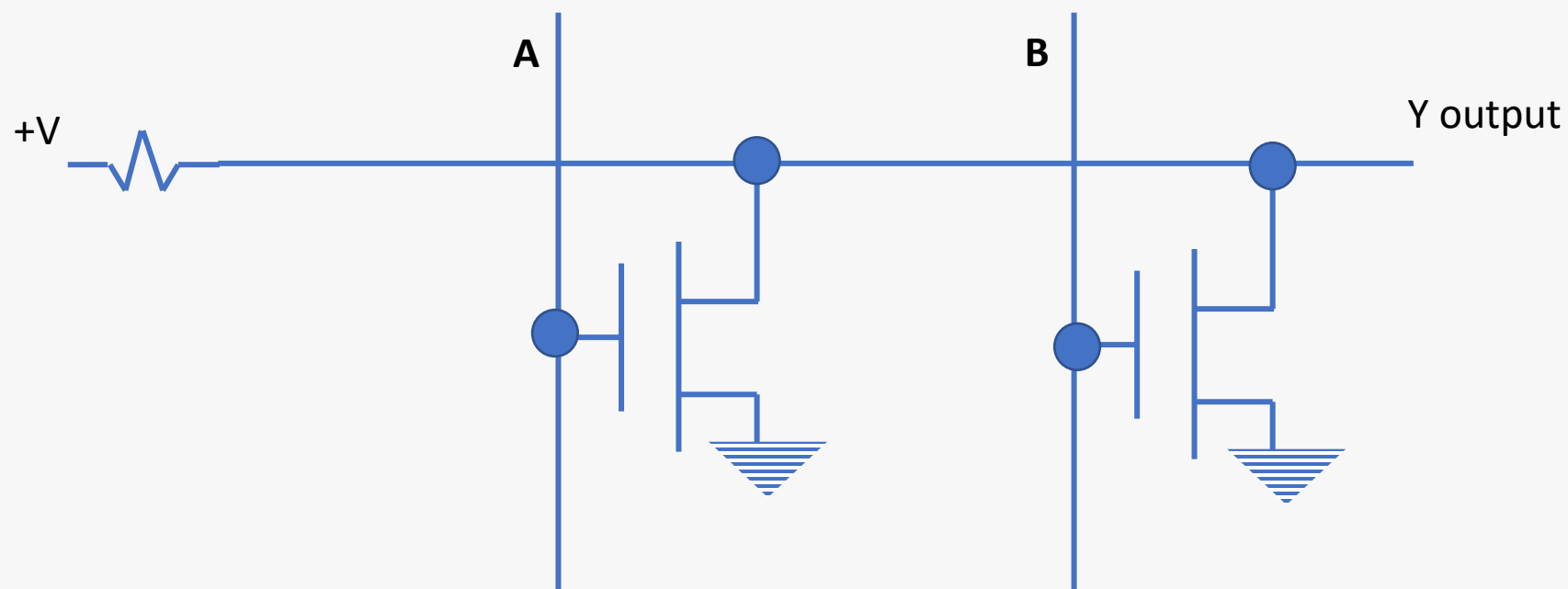Logic Gates Design with Transistor Switches



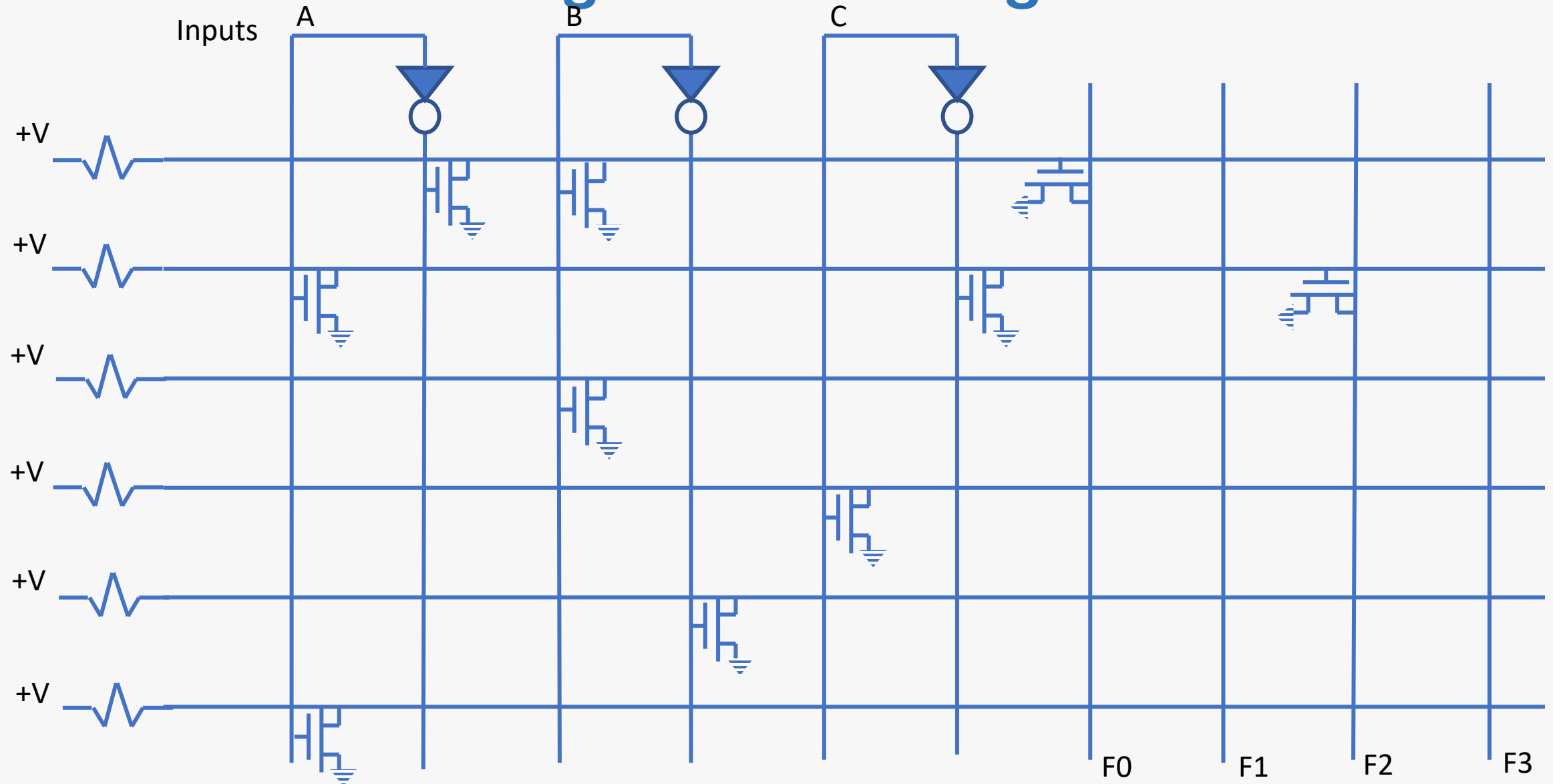
Transistors as Programmable Logic Switches



Different logic functions are realized through transistor switches

outputs

AND-OR Logic Array

 

PLA = Programmable
Logic Array
Comprises Programmable
AND-OR Gates