

Lecture 4

EE 421 / CS 425

Digital System Design

Fall 2024


Shahid Masud

Topics


Some examples from WinLogiLab (from last time)

FROM BEHAVIOUR TO IMPLEMENTATION

 - Connecting logic expression to physical circuits: Boolean Algebra, K-Maps to logic gates, XOR
- Combinational Logic Implementation using functional mapping to Decoders, Memory and Multiplexers
- Implementation Constraints



Gates (Primary Gates)

 

PHYSICAL GATES


BEHAVIOURAL MODELS

A	F
0	1
1	0

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1


A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

Gates (Compound Gates)

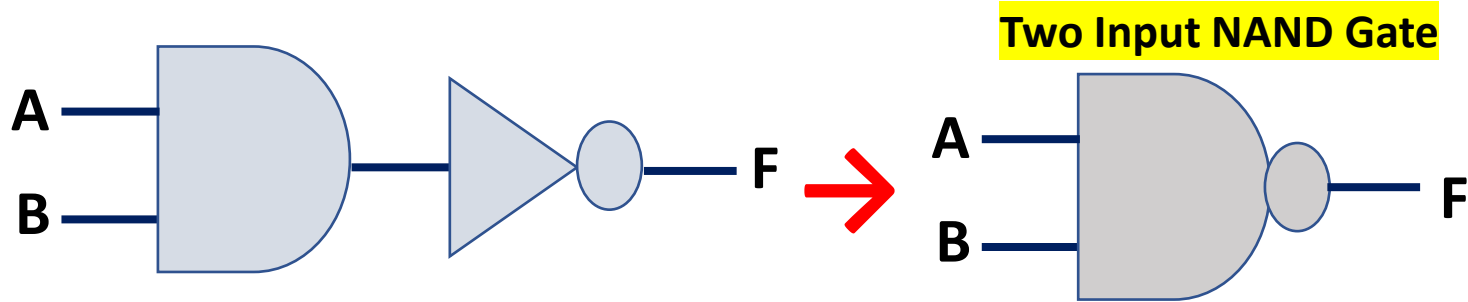

AND Gate followed by Inverter


A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

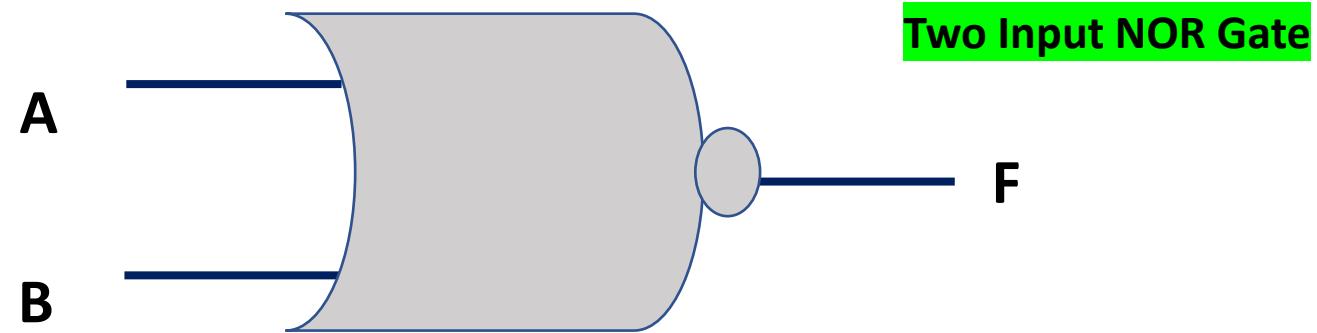

OR Gate followed by Inverter


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

3 Input Compound Gates

 

Three Input NAND Gate

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

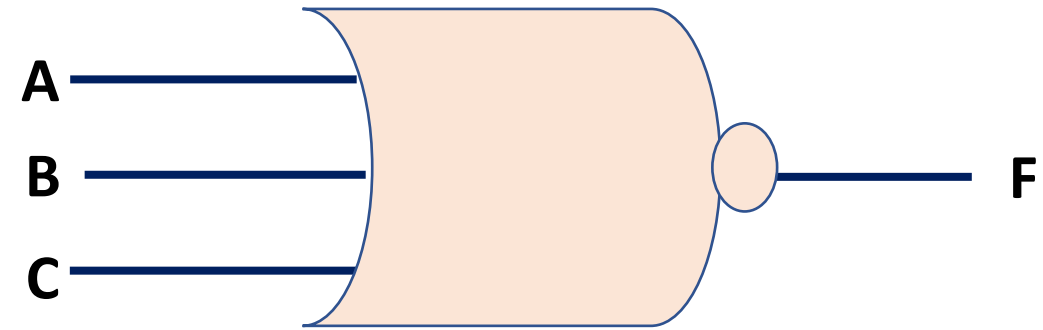


Three Input NOR Gate

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


A Question about Compound Gates

 Is this 3 input Nand gate same as the configuration on the right?




Are these equivalent
Circuits?

Or Not Equivalent??

 

Complex Gates – the XOR and XNOR

Two Input Exclusive OR Gate

 


$$F = \bar{A}B + A\bar{B}$$

$$F = A \oplus B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

The XNOR Complex gate


Two Input Exclusive NOR Gate

 

A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

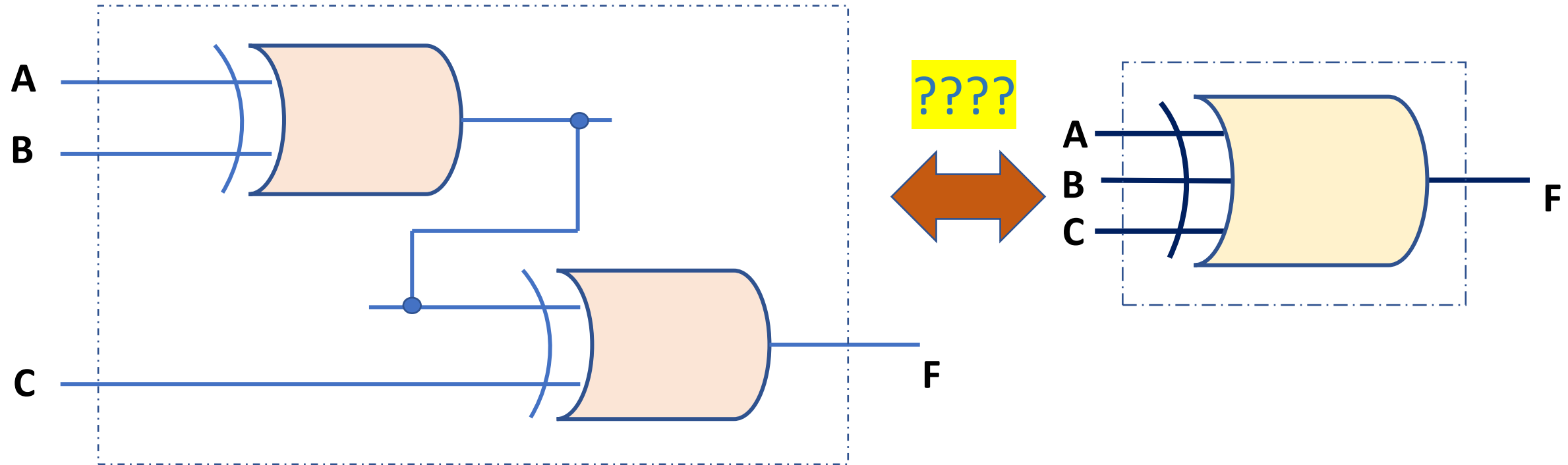
Question?

Are these two gates equivalent, Yes? Or No?



$$F = A \oplus B \oplus C$$

Three Input XOR Gate

 

$$F = A \oplus B \oplus C$$

A	B	C	$(A \oplus B)$	$(A \oplus B) \oplus (C)$	F
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	1	1
0	1	1	1	0	0
1	0	0	1	1	1
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	1

K Map of $(A \oplus B) \oplus (C)$

C, AB	00	01	11	10
0	0	1	0	1
1	1	0	1	0

This is the right way to work with XOR Gates

(but not the NAND or NOR gates)

Functional Digital Circuits – MSI (Medium Scale Integration)


Circuits that are formed from simple, compound or complex gates

Examples:

- Adder/Subtractor circuits
- Decoders
- Multiplexers
- Parity Checkers
- Memory Elements
- Counters, Modules
- SIPO, PISO, or FIFO, LIFO, – Require **REGISTERS**
- Etc.

Direct Implementation of
Complex Logic Functions

1 Bit Full Adder Circuit

 

Truth table represents **behaviour** of inputs and outputs

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

K-Map for Sum Function

Cin, AB →	00	01	11	10
0	0	1	0	1
1	1	0	1	0


$$Sum = A \oplus B \oplus Cin$$

K-Map for Cout Function


Cin, AB →	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$Cout = AB + ACin + BCin$$

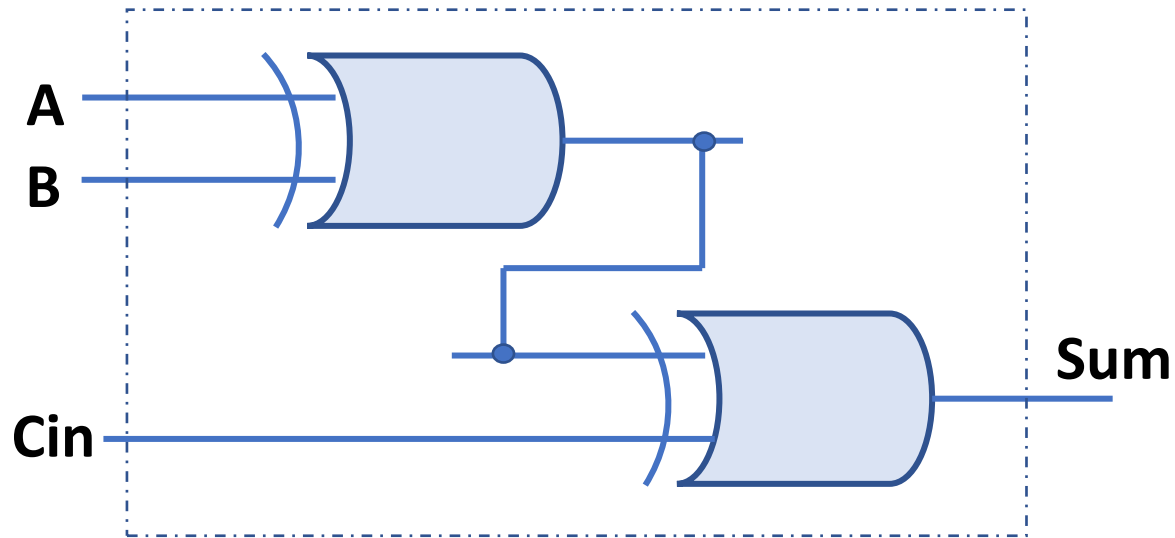Full Adder Implementation using Logic Gates





$$Sum = A \oplus B \oplus Cin$$

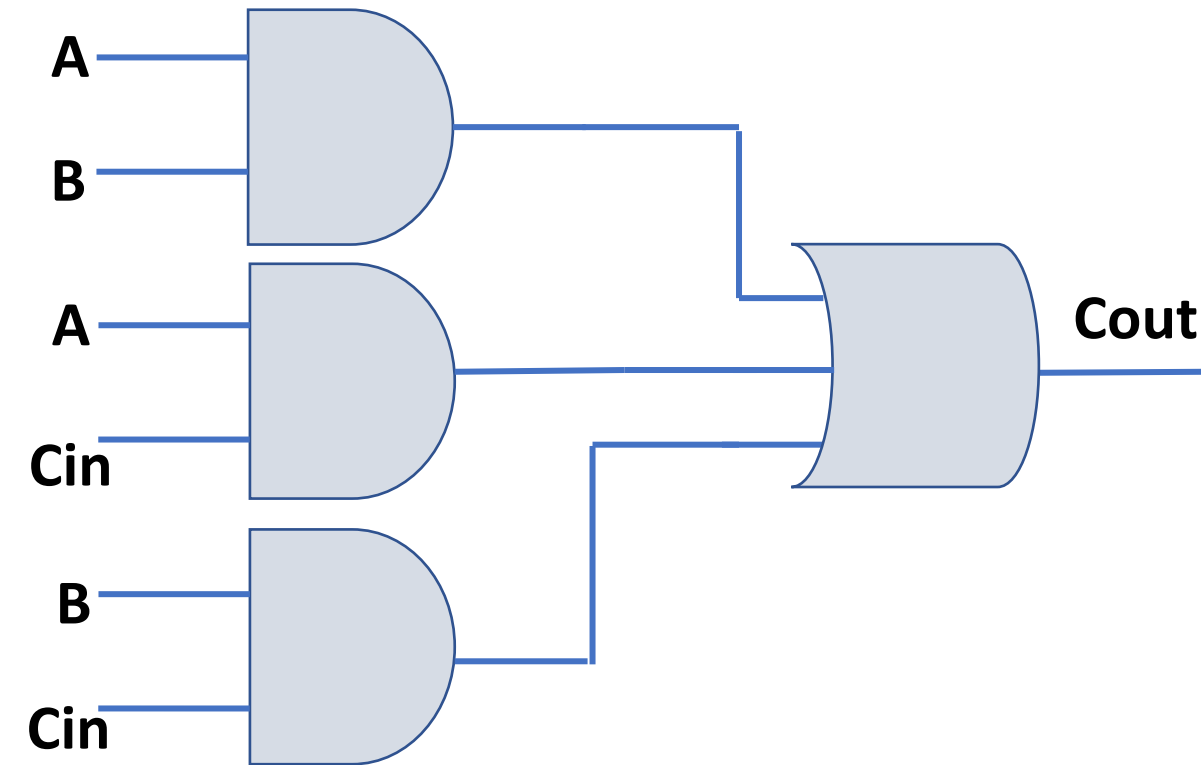


$$Cout = AB + ACin + BCin$$

Encoders and Decoders Functional Chips

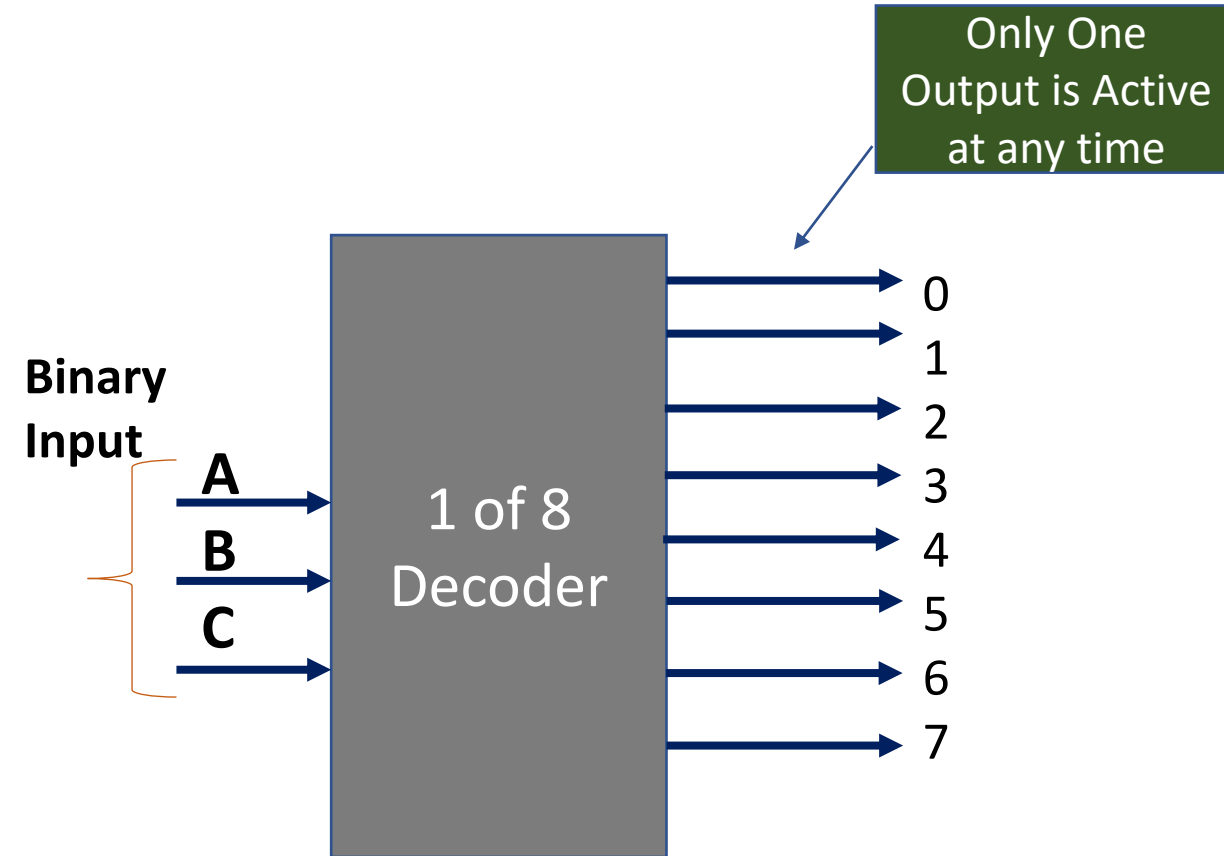 

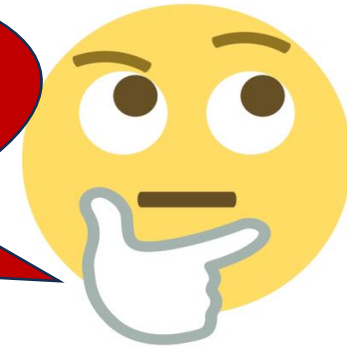Remember: We are dealing
with 'Complex' and 'High
Speed Circuits'




Logic Implementation vs Functional Mapping

Low Level Gates

High Level Functional Modules

Design Complexity


Full Adder Mapping on Decoder

 


Inputs		Outputs		
A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum Minterms = {1, 2, 4, 7}

Cout Minterms = {3, 5, 6, 7}

 

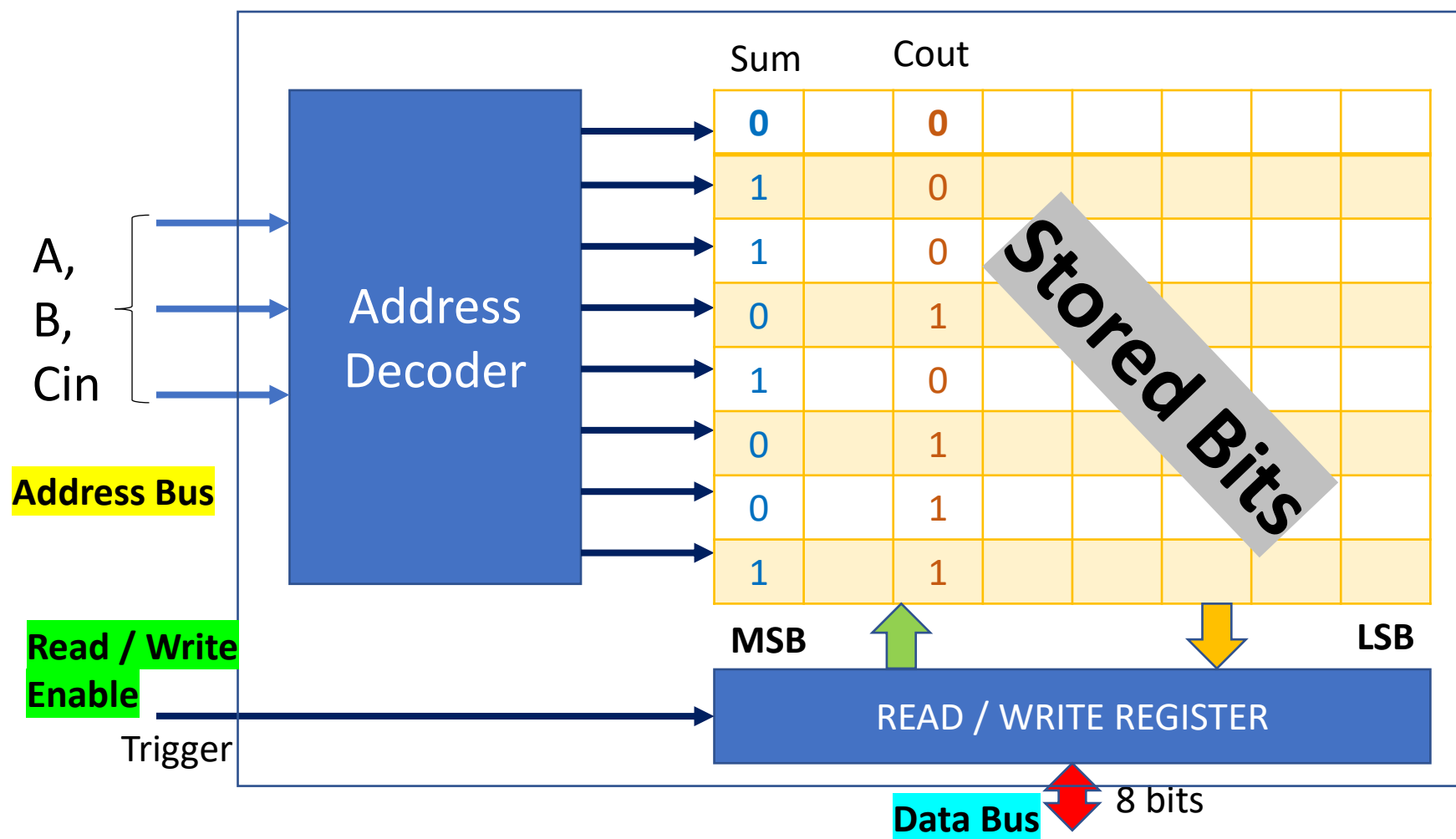
Memory Storage (RAM or ROM) as a functional logic block – **Lookup Tables**



Truth Table Outputs are Programmed in the memory Lookup Table

MSB output (Bit 7) is Sum
MSB-2 output (Bit 5) is Cout

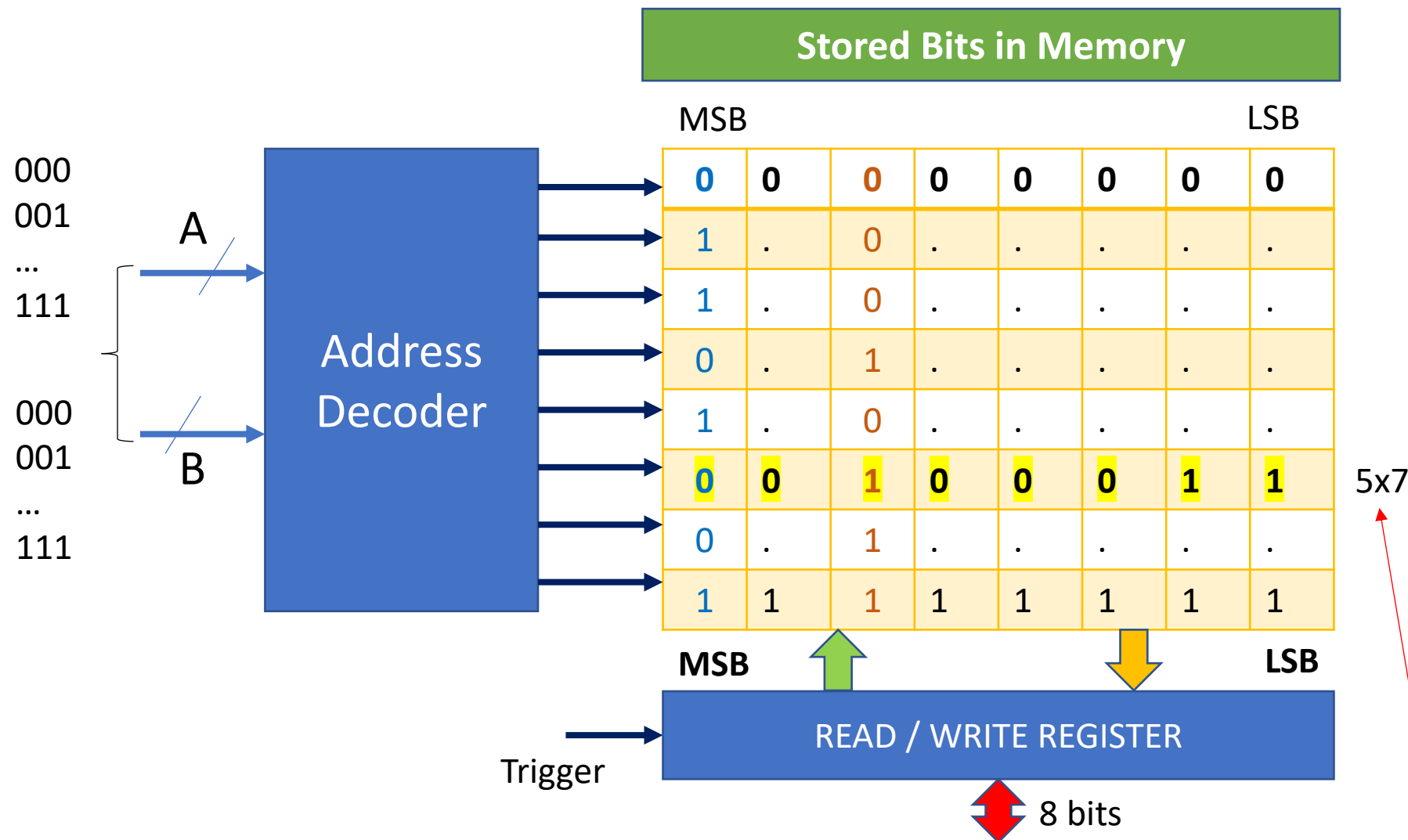Implement 3 bit x 3 bit Multiplier using Memory





Truth Table Outputs are Programmed in the memory Lookup Table

A	B	AxB	Data
0	0	0	00 H
0	1	0	00 H
...
0	7	0	00 H
0	1	0	00 H
1	1	1	01 H
2	1	2	02 H
...
3	2	6	06 H
...
5	7	35	23 H
...

Multiplexer MUX Functional Module


Selects one of many inputs at the output

 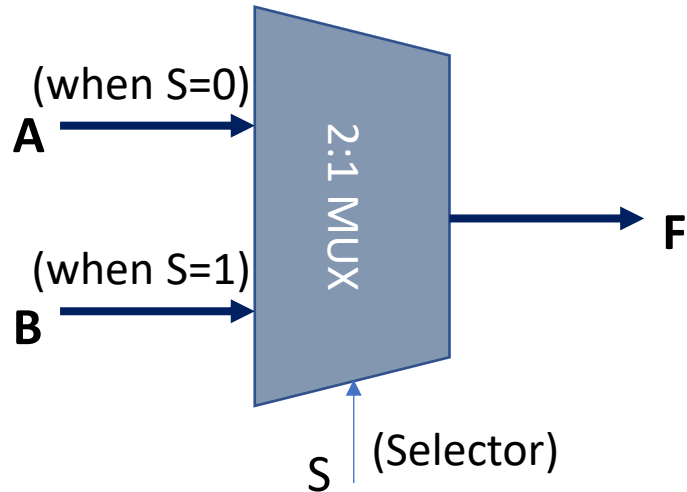

$$F = \bar{S}A + SB$$


Inputs		Select	Output
A	B	S	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

4 to 1 MUX

 

Inputs				Select		Output
A	B	C	D	S1	S0	F
A	B	C	D	0	0	A
A	B	C	D	0	1	B
A	B	C	D	1	0	C
A	B	C	D	1	1	D

8 to 1 MUX

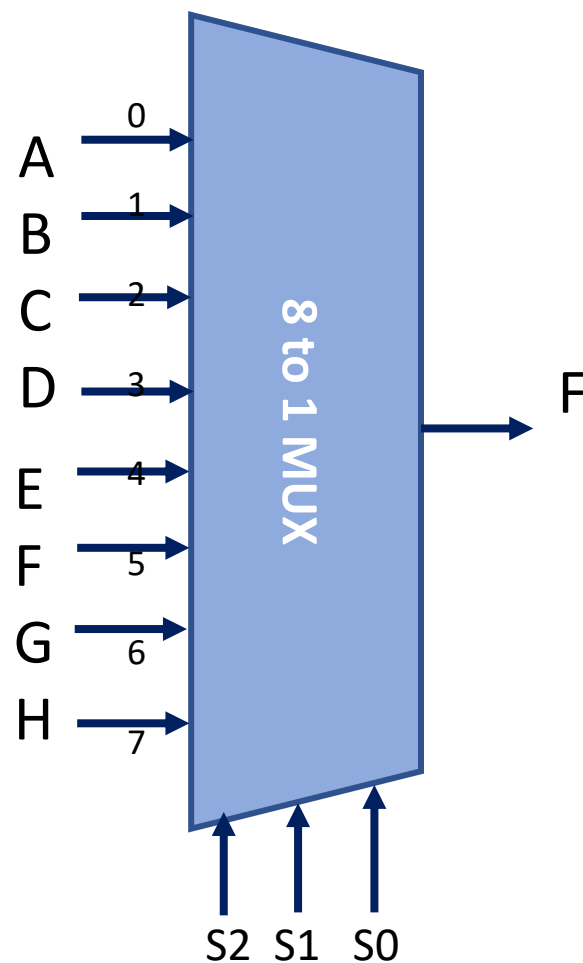

Input Lines								Select lines			Output
A	B	C	D	E	F	G	H	S2	S1	S0	F
A	B	C	D	E	F	G	H	0	0	0	A
A	B	C	D	E	F	G	H	0	0	1	B
A	B	C	D	E	F	G	H	0	1	0	C
A	B	C	D	E	F	G	H	0	1	1	D
A	B	C	D	E	F	G	H	1	0	0	E
A	B	C	D	E	F	G	H	1	0	1	F
A	B	C	D	E	F	G	H	1	1	0	G
A	B	C	D	E	F	G	H	1	1	1	H

Map a full adder to a 4 to 1 MUX

Full Adder Truth Table

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

MUX Selector Groups (2 Bits, 4 groups)

Select = 00

Observations

Sum output follows Cin; Cout remains 0

Select = 01

Sum output follows Cin'; Cout follows Cin


Select = 10

Sum output follows Cin'; Cout follows Cin

Select = 11

Sum output follows Cin; Cout remains 1

AND
Selector is same as inputs
AB

 

Mapping 16 Minterms to a 8 to 1 MUX

Output

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

3 Select Lines so
8 groups

Observations

F follows D

F follows D

F follows D'

F remains 0


F remains 0

F follows D

F remains 1

F remains 1


Mapping

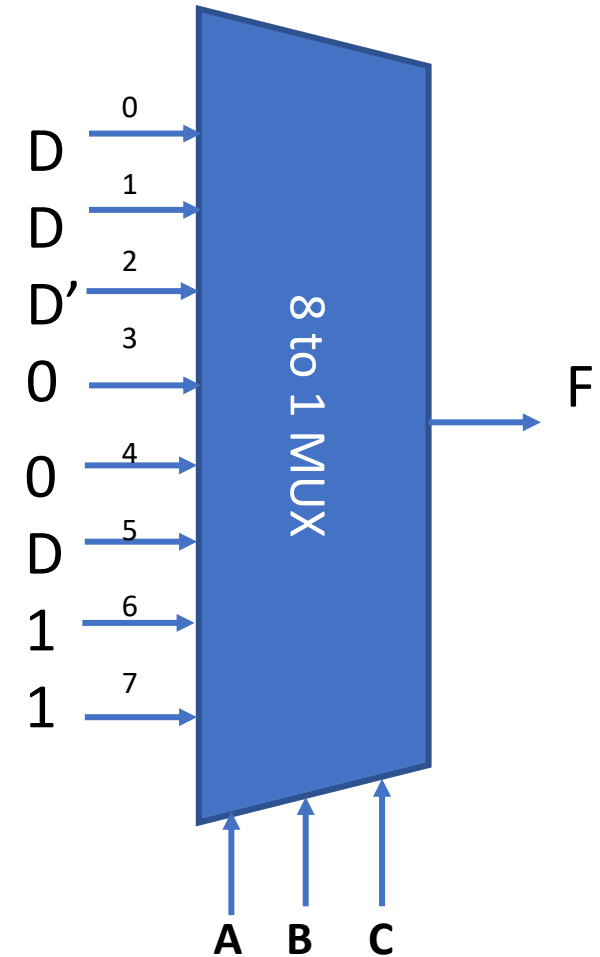

Minterms {1, 3, 4, 11, 12, 13, 14, 15}

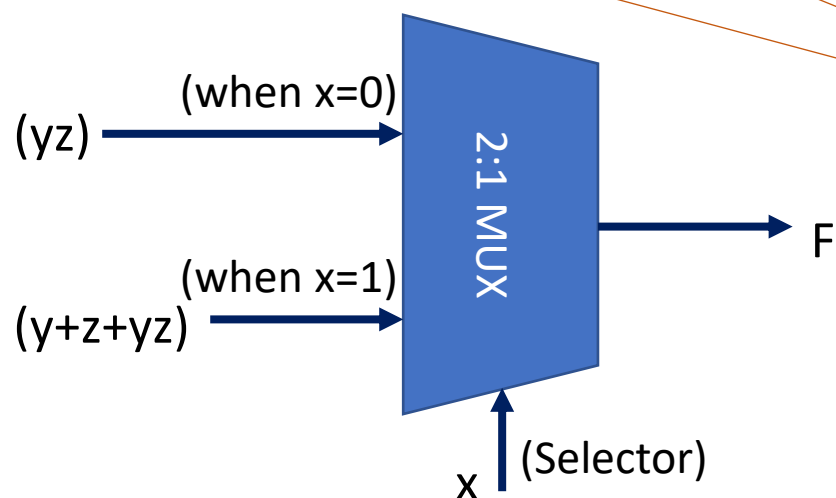Example: Implement logic functions using only 2 to 1 MUXes


$F = x'(yz) + x(y+z+yz)$, use x as selector input



Now we have to find a way to map (yz) and $(y+z+yz)$ into 2 to 1 MUX

Use y as select lines

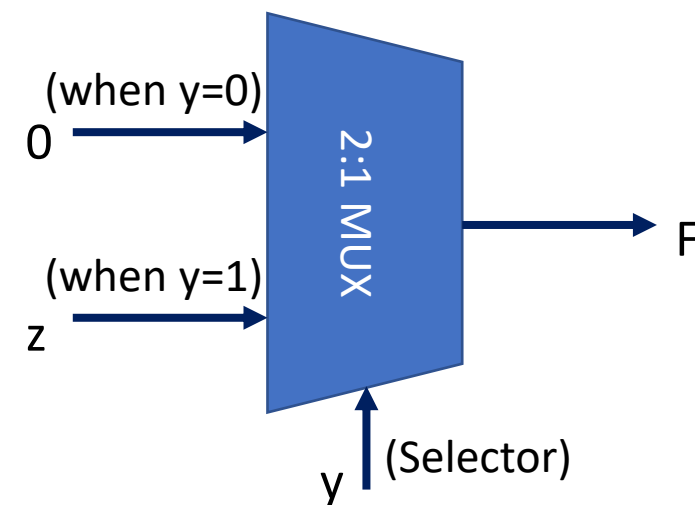For (yz) ; when $y = 0$, output is 0
when $y = 1$, output is z




Contd - Mapping only on 2 to 1 MUX

Let $G = (y+z+yz)$

Then $G = y + z(y+y') + yz$


$G = y(1+z+y) + z(y')$

$G = y(1) + y'(z)$

 

Implementation of $F = x'(yz) + x(y+z+yz)$

 Full implementation using only 2 to 1 MUX



Conclusion

- Behaviour of Digital System is described in Truth Table or Boolean Algebra
- For Implementation of this Behaviour, we can use:
 - Logic Gates – detailed and elaborate gate level design - Complicated
 - Decoders
 - Multiplexers
 - Memory

High Level Mapping to
Manage COMPLEXITY