

Lecture 7

EE 421 / CS 425

Digital System Design

Fall 2024

Shahid Masud

Topics


- Three State Drivers (or Buffers)
- D and T Flipflops
- Some Examples of DFF based Circuits:
 - Shift Registers
 - Counters
- Analyzing DFF based Circuits
- Synthesizing DFF Based Counters or Sequencers

Remember:
Quiz 2 Next Week


Three State Buffers for Processor Buses

- Buses are multi-wire signal paths that connect multiple functional units in a computer system, e.g., Address bus, peripheral bus, etc.
- Simplifies design and architecture of a computer system
- Tradeoff is that the access to the bus has to be managed to avoid conflicts
- Three state hardware devices provide a dynamic interface between a bus and a circuit, providing signals when enabled else an open circuit
- The input goes to the output of the tri-state buffer when enable signal is asserted


Three State Bus Drivers

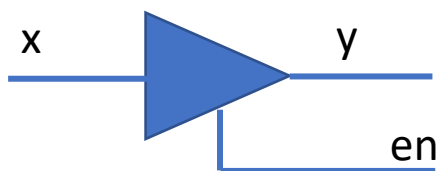

x	en	y
0	0	Hi_Z
0	1	0
1	0	Hi_Z
1	1	1

 

x	en	y
0	0	0
0	1	Hi_Z
1	0	1
1	1	Hi_Z

 


Typical Bus Structure utilizing 3-state buffers




Inverting and Non-Inverting 3-State Buffers / Drivers Exist

The Enable can be active high or active low

 Buffers with Hysteresis Loop are available for better noise immunity



D Flipflops – Behaviour and Equation

   



Characteristic Equation:

$$Q(t+1) = D$$

Q after clock pulse gets value of D

D	Q(t+1)
0	0; Reset
1	1; Set

T Flipflop – Behaviour and Equation

 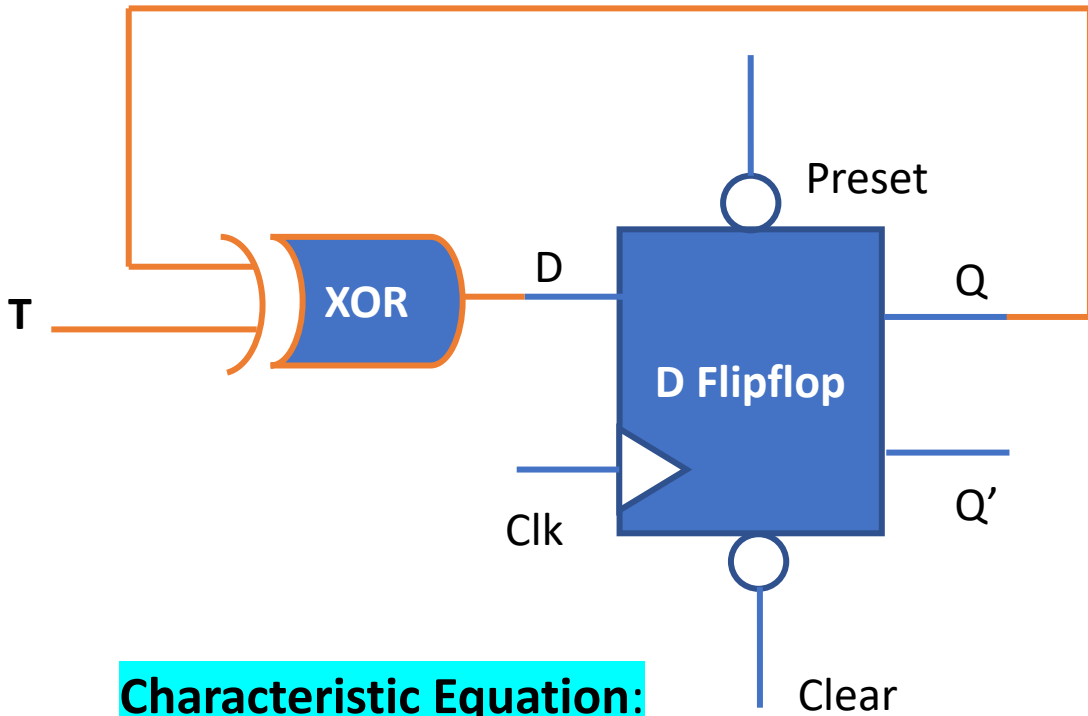


Characteristic Equation:

$$Q(t+1) = T \oplus Q$$

$$= T'Q + TQ'$$

T	Q(t+1)
0	Q(t); No change
1	Q'(t); Toggle or Complement

 

In this course,



**We will mostly use D Flipflops
and sometimes T Flipflops**

We want to study complex and high speed designs

Sequential Circuits: Counters, Sequencers, State Machines


- **Counters:** count in a fixed sequence, up or down
- **Sequencers:** sequence through a pre-defined arbitrary sequence
- **State Machines:** Sequential and Combinational Circuits work together to go one of many next states based on current inputs

Moving Through Register Chain

 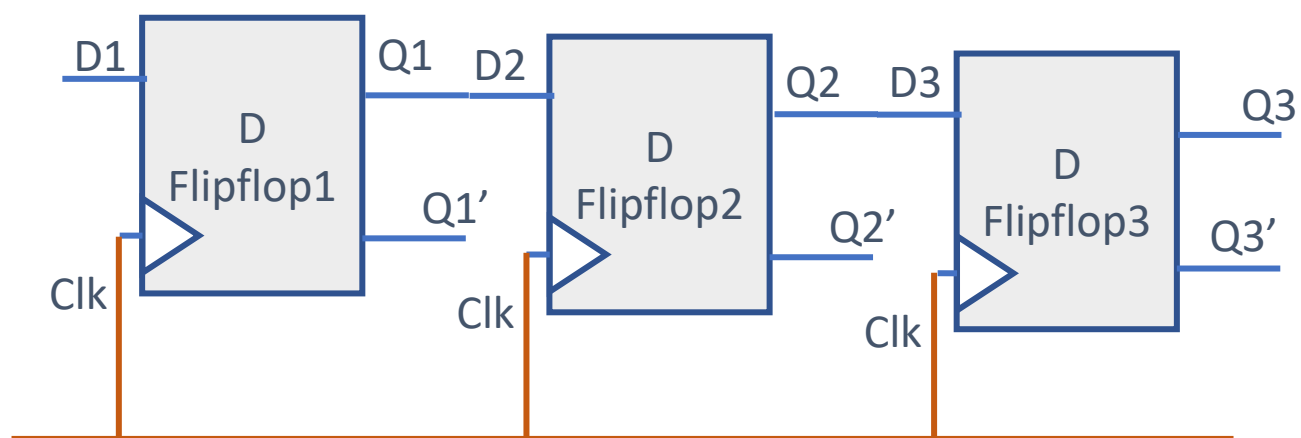

3 DFF Shift Register Timing Diagram from a website

 
Look closely at the Area close to Clock transition, Shaded pink lines



We assume that there is a small delay at Q state of each flipflop to make the timing diagram easily understandable.

But in reality, the situation would be a little more complicated than this simple time delay.

Cyclic Shift Register using D flipflops

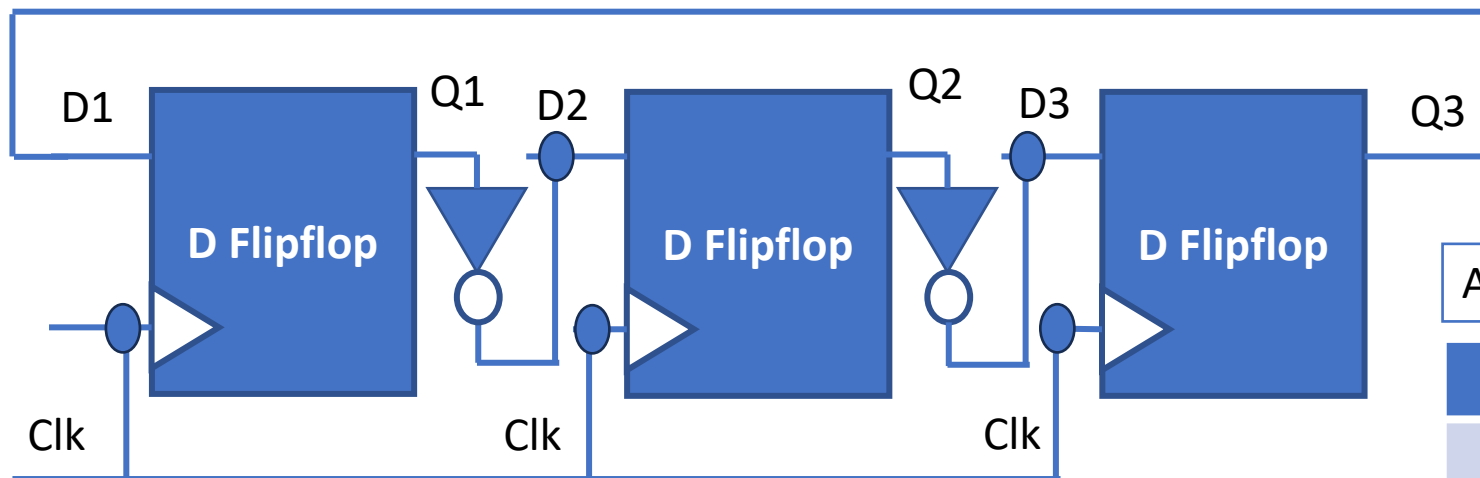

Assume all DFFs are Cleared to **0** at Startup

Clock No.	Q1	Q2	Q3
1	0	0	0
2	0	1	1
3	1	1	0
4	0	0	0
5	0	1	1
6	1	1	0
7	0	0	0
CONTINUE


After the clock edge:

$Q1(t+1)$ becomes same as $Q3(t)$

$Q2(t+1)$ becomes inverse of $Q1(t)$

$Q3(t+1)$ becomes inverse of $Q2(t)$

Tail Ring Counter Four Stage

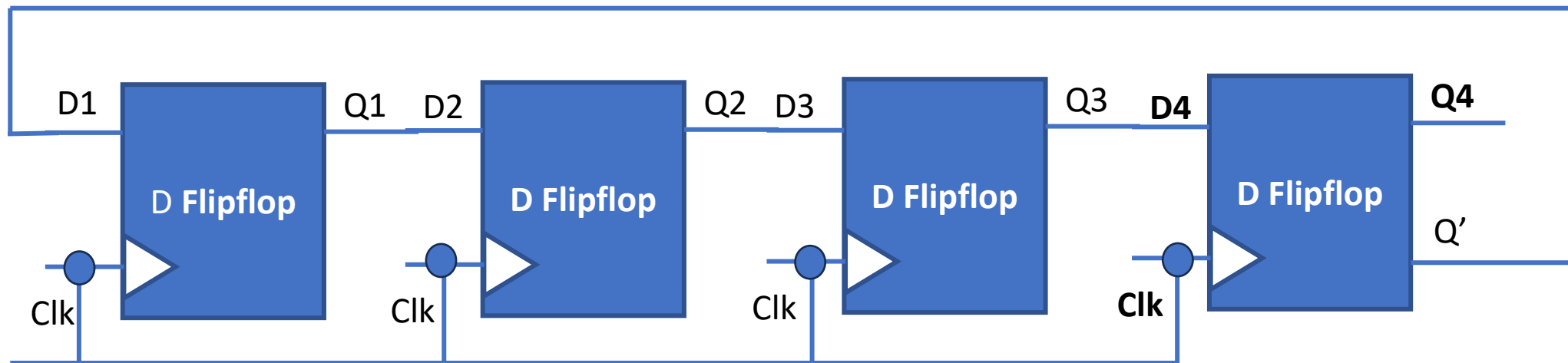


State
Transition
Table

Sequence No.	Q1	Q2	Q3	Q4
1	0	0	0	0
2	1	0	0	0
3	1	1	0	0
4	1	1	1	0
5	1	1	1	1
6	0	1	1	1
7	0	0	1	1
8	0	0	0	1
9	0	0	0	0

Analyze Sequential Circuits

- Concept of State Equations
- Concept of State Tables
- Logic Steering through Combinational Logic
- Arbitrary Counting and Sequencing

Example Sequential Circuit for Analysis

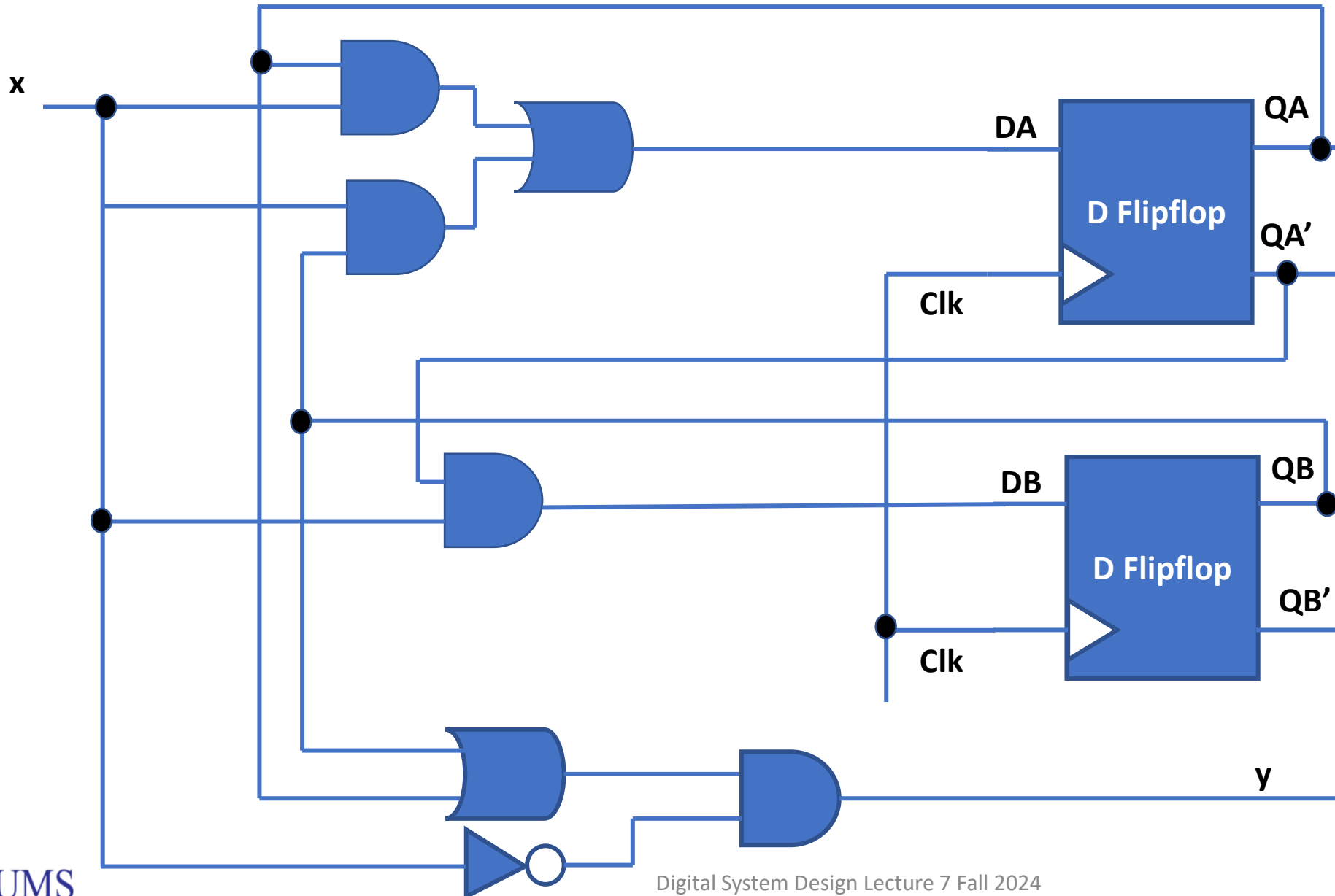

Determine State Equations

$$QA(t+1) = QA(t)x(t) + QB(t) x(t)$$

$$QB(t+1) = QA'(t) x(t)$$

$$y(t) = [QA(t) + QB(t)]x'(t)$$



Can be written in a simplified way:

$$QA(t+1) = QA.(x) + QB.(x)$$

$$QB(t+1) = QA'.(x)$$

$$y = (QA + QB).(x')$$


Determine State Table from State Equations

Present State	Present State	Input	Next State	Next State	Output
QA(t)	QB(t)	x	QA(t+1)	QB(t+1)	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Compact State Table

Present State		Next State				Output	
		When $x = 0$		When $x = 1$		$x = 0$	$x = 1$
$A(t)$	$B(t)$	$A(t+1)$	$B(t+1)$	$A(t+1)$	$B(t+1)$	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

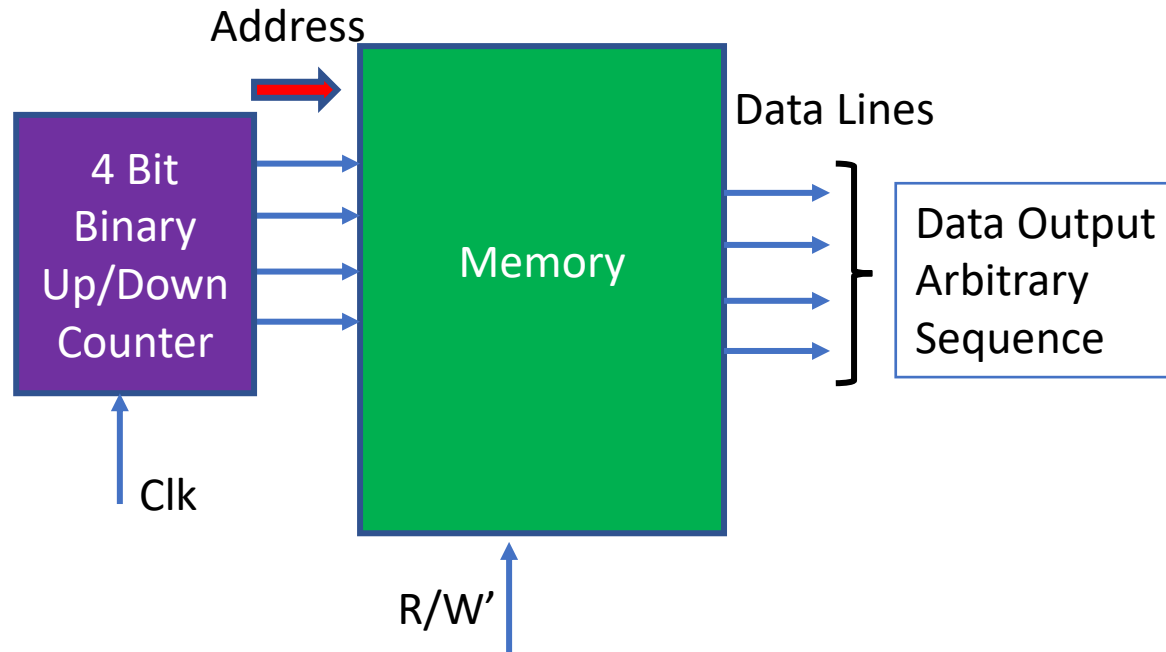Using Memory to design an arbitrary sequencer



**Desired Sequence is
Stored in Memory Locations**

Design of Synchronous Counter using DFF

- Express each number of sequence in binary code
- Use appropriate number of DFFs to represent entire sequence
- Make a State Table representing Present State and Next State
- Determine Excitation Logic Expression for Next States using K-Maps
- Complete the DFF Based Circuit using Excitation Expressions

Example Design of a Synchronous Counter (Sequencer)

Make a Synchronous Counter for sequence {0 → 3 → 6 → 9 → 12 → 0}

Step 1: Describe Behavior Through Truth Table

Desired Sequence In Binary form:

Clock No.	Sequence	Binary			
		Q3	Q2	Q1	Q0
1	0	0	0	0	0
2	3	0	0	1	1
3	6	0	1	1	0
4	9	1	0	0	1
5	12	1	1	0	0
6	0	0	0	0	0



Present State – Next State Table

Clock No.	Sequence	Present State				Next State			
		Q3(t)	Q2(t)	Q1(t)	Q0(t)	Q3(t+1)	Q2(t+1)	Q1(t+1)	Q0(t+1)
1	0	0	0	0	0	0	0	1	1
2	3	0	0	1	1	0	1	1	0
3	6	0	1	1	0	1	0	0	1
4	9	1	0	0	1	1	1	0	0
5	12	1	1	0	0	0	0	0	0
6	0	0	0	0	0	0	0	1	1

DFF make it convenient as Present State to Next State is only separated by a Clock Pulse

Make K-Maps to determine Next State using Next State Outputs as K-Map Entries

K-Map for D0 (Input that will give correct next state)

Q3Q2, Q1Q0	00	01	11	10
00	1		0	
01				1
11	0			
10		0		

State Equation:

$$D0 = Q3'Q2'Q1'Q0' + Q3'Q2Q1Q0'$$


K-Map for D1

Q3Q2, Q1Q0	00	01	11	10
00	1		1	
01				0
11	0			
10		0		

State Equation:

$$D1 = Q3'Q2'Q1'Q0' + Q3'Q2'Q1Q0$$

K-Map for D2

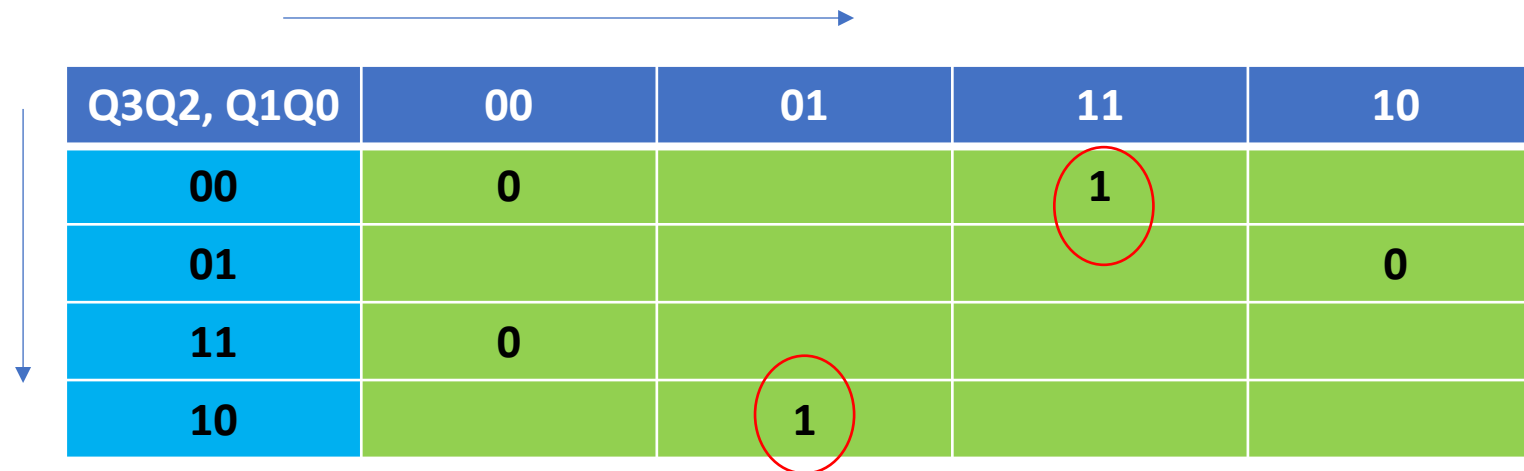

Q3Q2, Q1Q0	00	01	11	10
00	0		1	
01				0
11	0			
10		1		

State Equation:

$$D2 = Q3Q2'Q1'Q0 + Q3'Q2'Q1Q0$$


K-Map for D3

Q3Q2, Q1Q0	00	01	11	10
00	0		0	
01				1
11	0			
10		1		

State Equation:

$$D3 = Q3'Q2Q1Q0' + Q3Q2'Q1'Q0$$

Final Circuit Design of Sequencer

 

**Similar circuit for
Other inputs D1 to D3
to implement State Equations**

For example, state equations:

$$D0 = Q3'Q2'Q1'Q0' + Q3'Q2Q1Q0'$$

$$D1 = Q3'Q2'Q1'Q0' + Q3'Q2'Q1Q0$$

$$D2 = Q3Q2'Q1'Q0 + Q3'Q2'Q1Q0$$

$$D3 = Q3'Q2Q1Q0' + Q3Q2'Q1'Q0$$

