

Digital System Design

ELEC3342

Introduction to Field
Programmable Gate Array
(FPGA)



Dr. Hayden So


Department of Electrical and
Electronic Engineering

<http://www.eee.hku.hk/~elec3342>

FPGA – Not long ago...

- Field Programmable Gate Array
- Began as ASIC alternatives
 - ASIC that can be configured “in the field”
 - At power up, configuration is load to the chip
 - Chip acts as an ASIC until power down
- Used as...
 - Glue logic
 - ASIC pre-fabrication “Prototype”
 - ASIC replacement for small volume, fast time-to-market

Simplified View of an FPGA

 

Island-style Layout



Logic Block

Connection Block



Switch Block

I/O Block

Basic Idea:


- Logic blocks implement combinational logic + register
- Connect logic blocks through switches and connection boxes

Modern FPGAs


- Embedded processors
 - Soft+Hard: PowerPC/ARM
- On-chip memory
 - Soft+Hard
- On-chip FIFO
- Dedicated DSP blocks
 - 23x18 multipliers, pre adder
 - MAC
 - Floating point
- High speed Serial I/O
- Plenty of parallel I/O
 - Configurable impedance
 - Configurable delay
- On-chip clock management
 - MMCM, PLL, multiple clock regions
- On-chip hard IP:
 - Ethernet MAC
 - PCI endpoint
- On-chip ADC
- Size
 - > 1 million “equivalent ASIC gates”
- AI core
- System-level reconfiguration
- Dynamic Partial Reconfiguration
 - Reconfigure part of the chip while the rest continues to operate

Modern FPGA Layout

 - Island style connection
- Features arranged as columns
 - I/O columns on peripheral
 - Clock management next
 - Logic and Memory I/O next
- Modular design
- Clock routing in middle



Logic Block

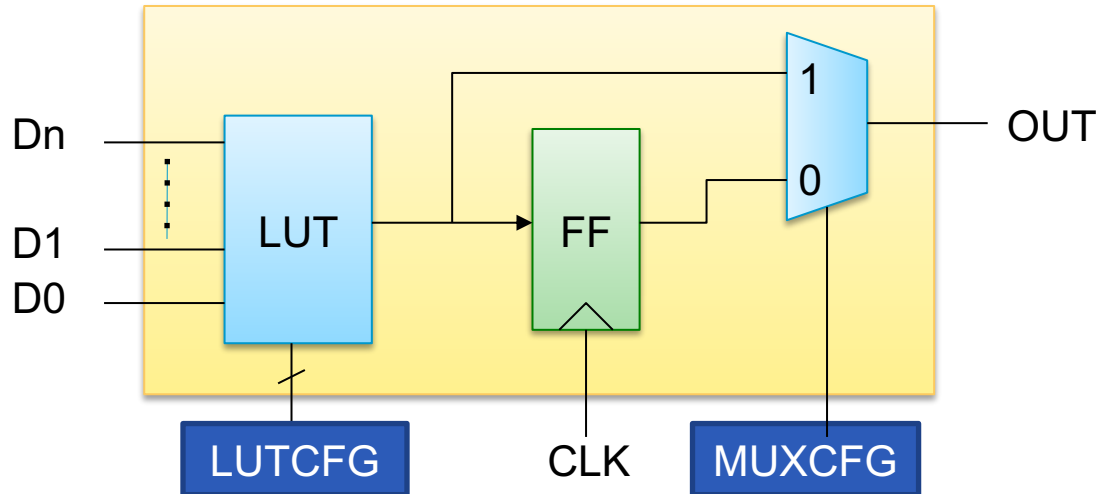


Xilinx: Configurable
logic block (CLB)
Altera: Logic and
Arithmetic Block (LAB)

- Each n-input lookup table (LUT) may be configured to perform ANY n-input combinational logic
- The result of the LUT is optionally registered by the FF
- Function controlled by configuration bits (LUTCFG, MUXCFG, etc)
 - Store in configuration memory

The LUT

 - LUT: Lookup Table
- A direct implementation of a truth table
 - Recall a TT uniquely defines a circuit



A	B	C	D	Q
0	0	0	0	0
0	0	0	1	0
...				
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

- An n-LUT implements any n-input combinational logic
 - Depends on LUT configuration

Making a 2-LUT from Truth Table



A B		<i>FALSE</i>	<i>AND</i>	...	<i>OR</i>	...	<i>NAND</i>	<i>TRUE</i>
0	0	0	0		0		1	1
0	1	0	0		1		1	1
1	0	0	0	...	1	...	1	1
1	1	0	1		1		0	1

16 possible ways




4 configuration bits

2-LUT: MUX Based



cfg3	cfg2	cfg1	cfg0	A	B	Q
0	0	0	0	0	0	0
0	0	0	0	0	1	0
0	0	0	0	1	0	0
0	0	0	0	1	1	0
0	0	0	1	0	0	0
0	0	0	1	0	1	0
...						
1	1	1	1	1	0	1
1	1	1	1	1	1	1


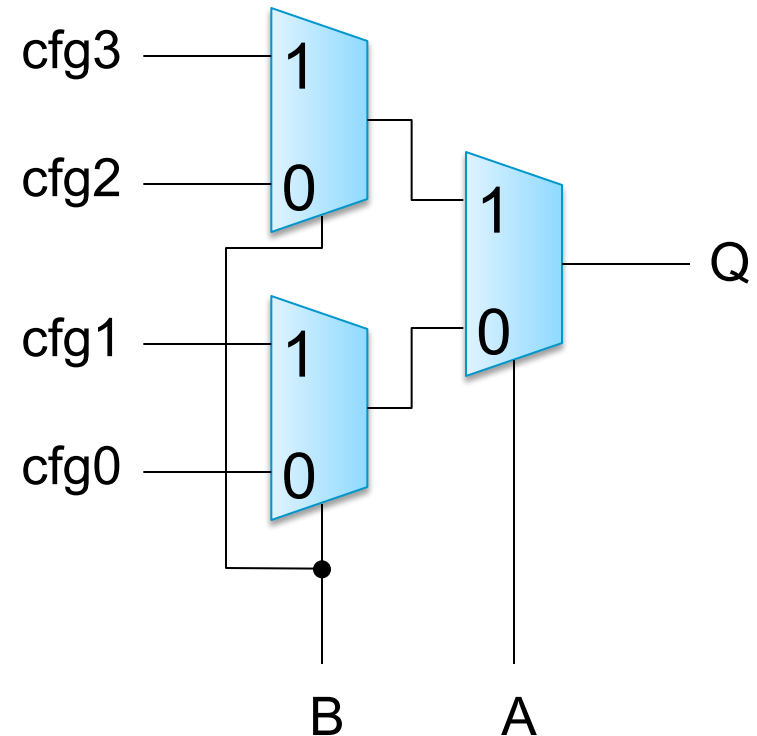


LUT in Real Life




- 3-LUT and 4-LUT are most common
- 6-LUT in latest Xilinx FPGA (Virtex-5, Virtex-6)
- SRAM based
 - Configurations are stored as SRAM “content”
 - Input signal acts like “address” that reads the SRAM content
- SRAM-based LUT can be reusable as a real SRAM if needed
 - Xilinx calls it Distributed RAM

Xilinx CLB

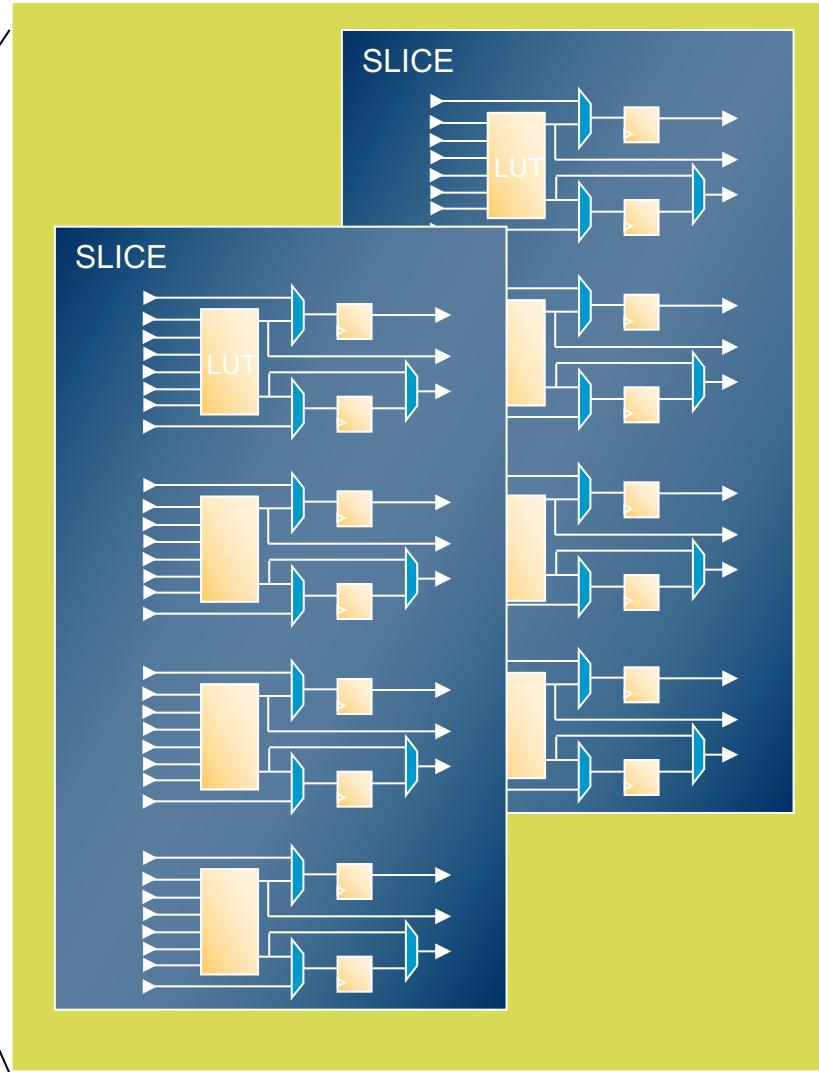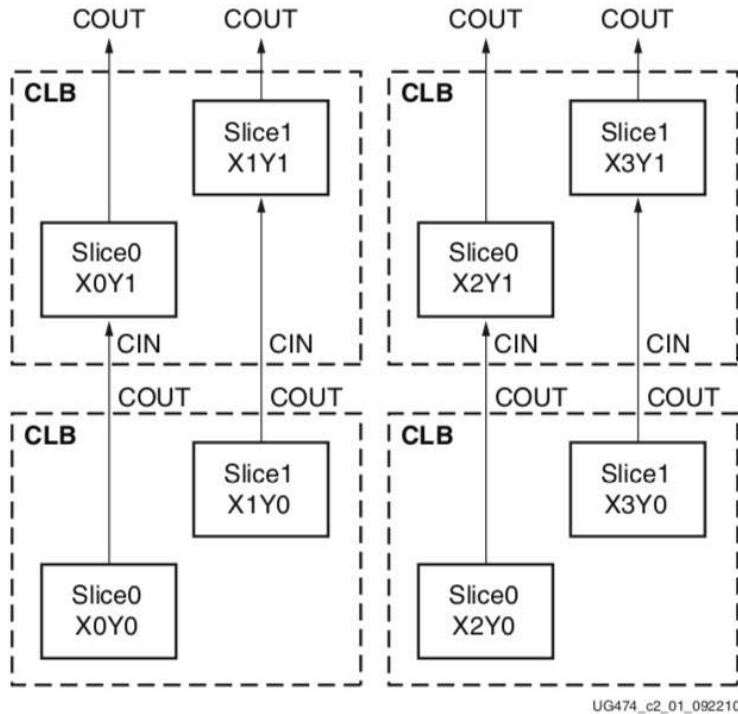


- 1 CLB → 2 Slices
- Slices connected vertically with dedicated carry chain

Xilinx Logic Slice (Overview)

 

- 1 Slice → 4 LUT-FFx2 pairs
- 6-LUT with additional muxes between LUTs within a slice
- Dedicated carry logic to create fast adders
 - Intra- and inter slices

Xilinx Logic Slice

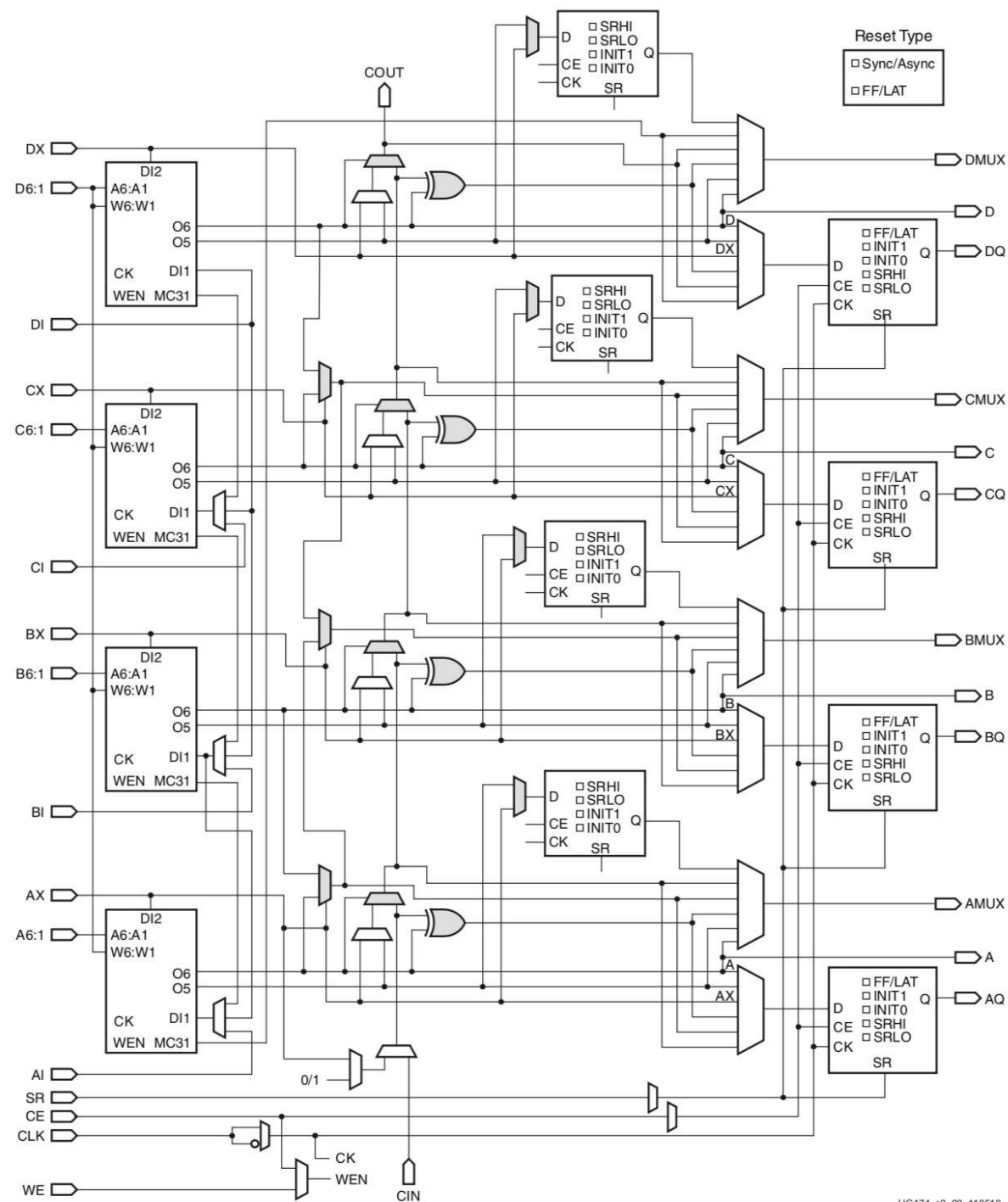


On-Chip Memory

- Modern FPGAs have 2 main types of on-chip memory
 - Dedicated on-chip memory (Block RAM)
 - LUT-based memory
- Both implemented with SRAM technologies
- Dedicated Block RAM has higher capacities, higher density due to dedicated internals
- LUT-based memory make memory out of the LUTs in Logic Blocks

LUT-based Memory

- Recall that the core of a logic block is 6-LUT
 - A look up table = a ROM
 - Configuring the content of the LUT turns it into a combinational circuit
- Standard FPGA configure LUT content through dedicated configuration logic
- Idea: expose the configuration logic to the LUT to a user application:
 - Configuration → writing to memory
 - Configuration bit → address
 - LUT data out → read data port
 - Configuration data → write data port


Turning a LUT into Memory

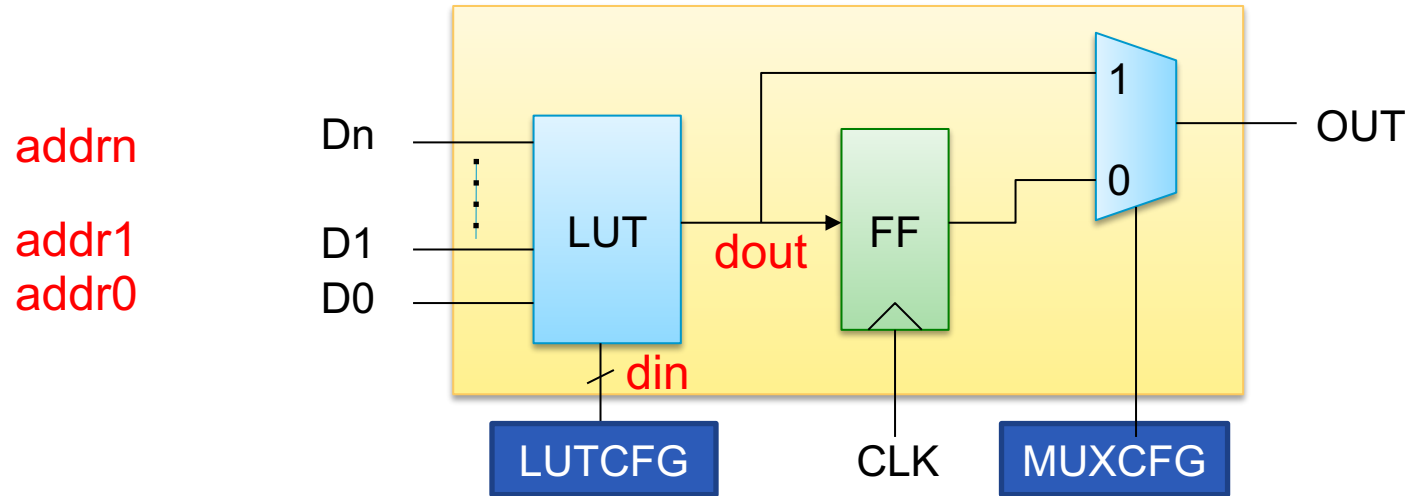

- Each 6-LUT becomes a 1-bit memory with 6 bit address (64 locations)
- b 6-LUTs in parallel → 64 x b memory


Hard Memory Block

 - Harden on-chip configurable memory
 - Xilinx: BRAM
- True dual-port memory
- Configurable:
 - 32k x 1 to 512 x 72 in one 36K block
 - Simple dual-port and true dual-port configurations
 - Built-in FIFO logic
 - 64-bit error correction coding per 36K block
 - Adjacent blocks combine to 64K x 1 without extra logic





DSP Slice

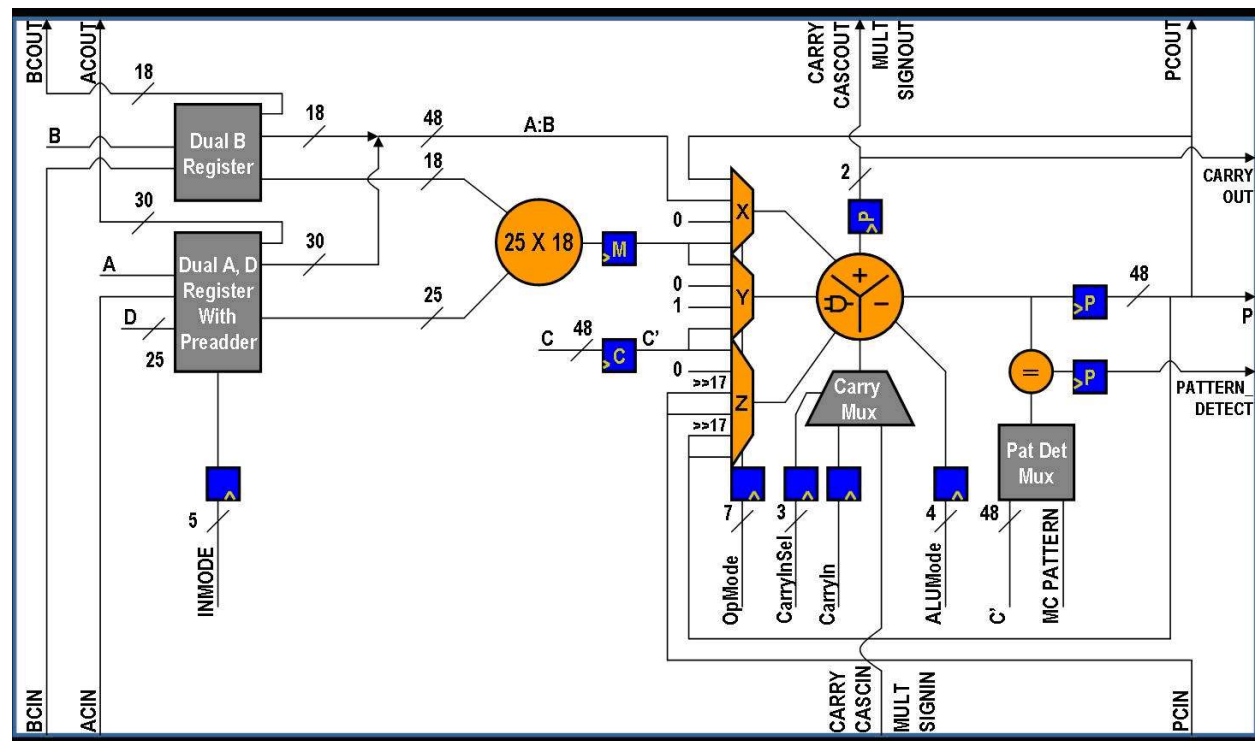
- All 7 series FPGAs share the same DSP slice
 - 25x18 multiplier
 - 25-bit pre-adder
 - Flexible pipeline
 - Cascade in and out
 - Carry in and out
 - 96-bit MACC
 - SIMD support
 - 48-bit ALU
 - Pattern detect
 - 17-bit shifter
 - Dynamic operation (cycle by cycle)



FPGA Routing

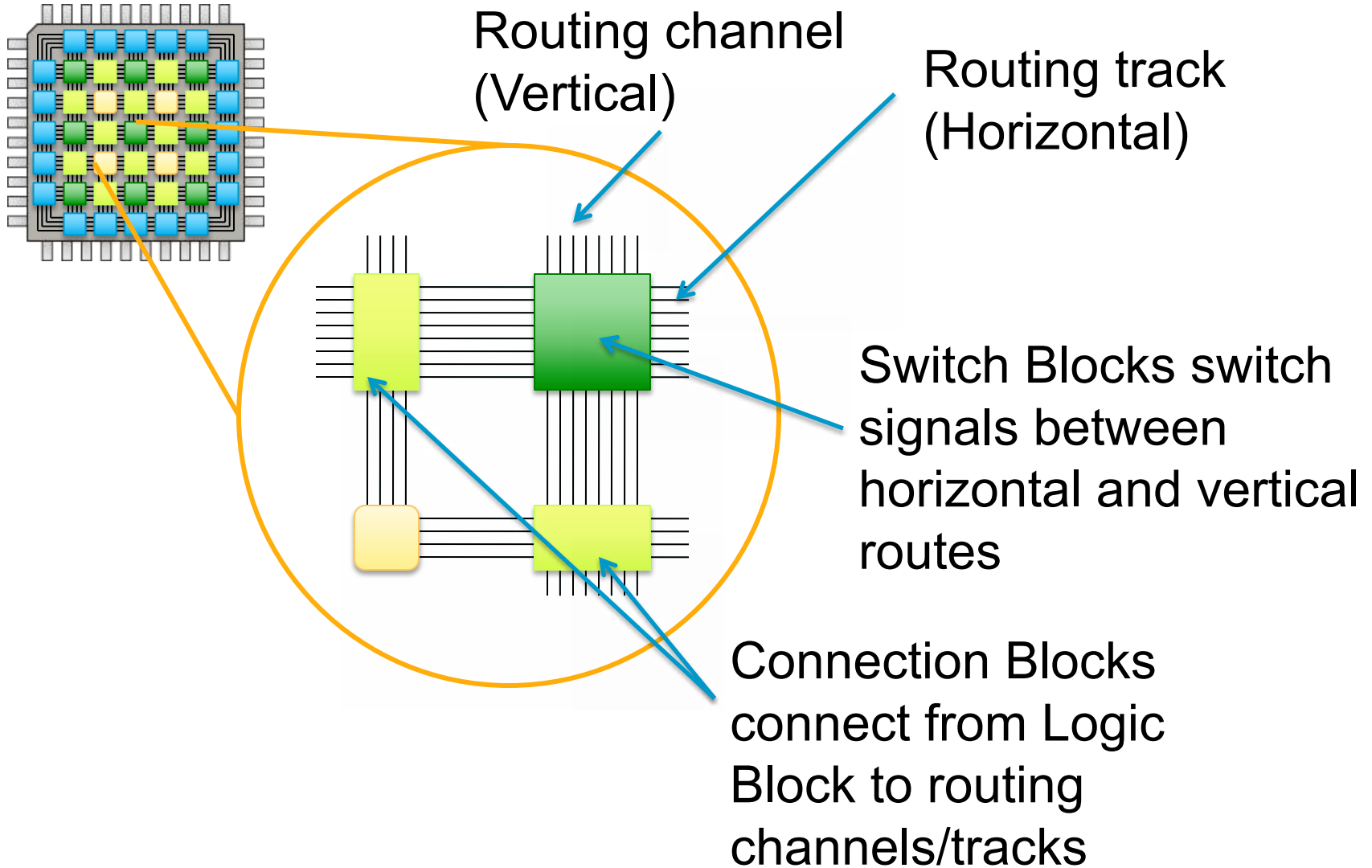 


Programmable Switches

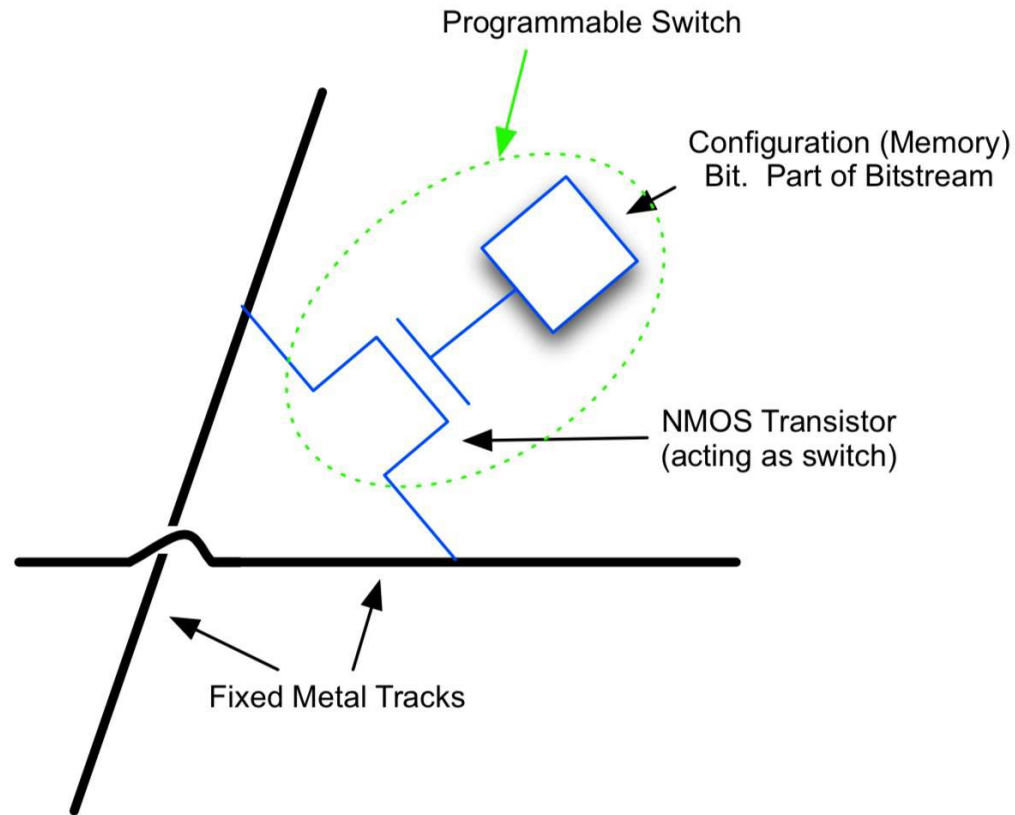


- Simple connection:
 - Connect 2 wires by a single transistor
- 1 configuration bit per connection

Programmable Switches

 

**Unbuffered
Connection**


**Buffered
Connection**

 

**Buffered Uni-Directional
Connection**


- Common to have **buffered, unidirectional** connection in modern FPGAs

Setting up a route

 


- Make connection by setting switches along route between logic blocks

Setting up a route

 


- Make connection by setting switches a along route between logic blocks

Switch Block

 


- Goal of a switch block is to connect physical wires.
- Problem: too many possible connections
- Fully connected graph:
 - Too large, too expensive, too much power


Many Topologies

 

Disjoint

 


Universal

 

Wilton

I/O Block

 


I/O blocks

- Configure each pin to be input, output, or input/output
- Different voltage standard
 - LVTTL, PCI, etc
- Single-end signal → diff signals
- Internal routing make sure that any internal signal can be routed to any external pin
 - Allow PCB fixup


Input/Output Blocks

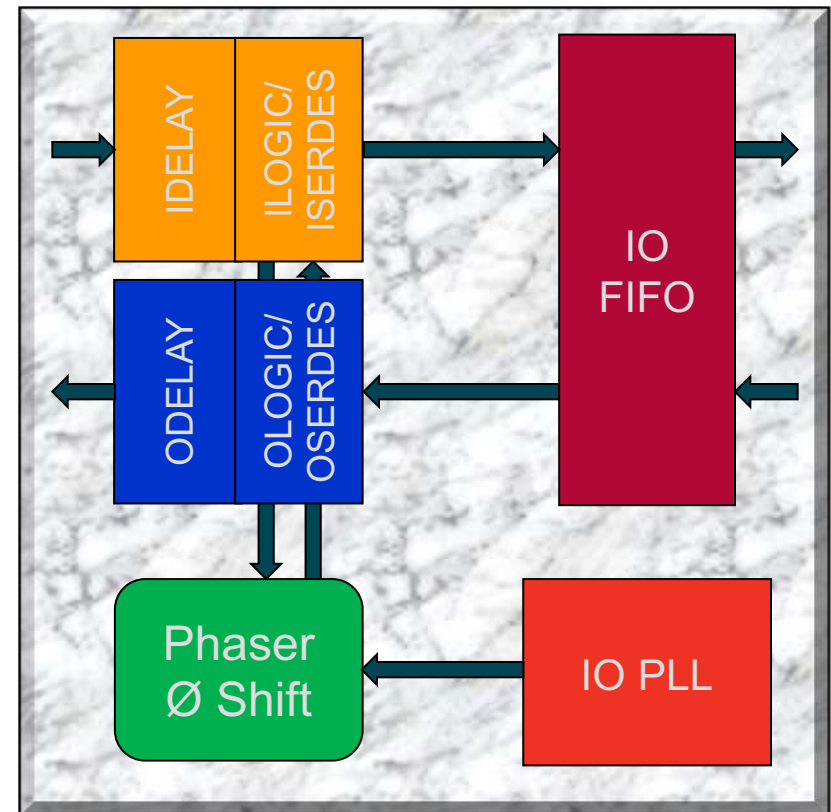- Two distinct I/O types
 - High range: Supports standards up to 3.3V
 - High performance: Higher performance with more I/O delay capability
 - Supports I/O standards up to 1.8V
- Extension of logic layer functionality
 - Wider input/output SERDES
 - Addition of independent ODELAY
- New hardware blocks to address highest I/O performance
 - Phaser, IO FIFO, IO PLL




Clocking Resources

- Based on the established Virtex-6 FPGA clocking structure
 - All 7 series FPGAs use the same unified architecture
- Low-skew clock distribution
 - Combination of paths for driving clock signals to and from different locations
- Clock buffers
 - High fanout buffers for connecting clock signals to the various routing resources
- Clock regions
 - Device divided into clock regions with dedicated resources
- Clock management tile (CMT)
 - One MMCM and one PLL per CMT
 - Up to 24 CMTs per device

 

FPGA, ASIC Crossover

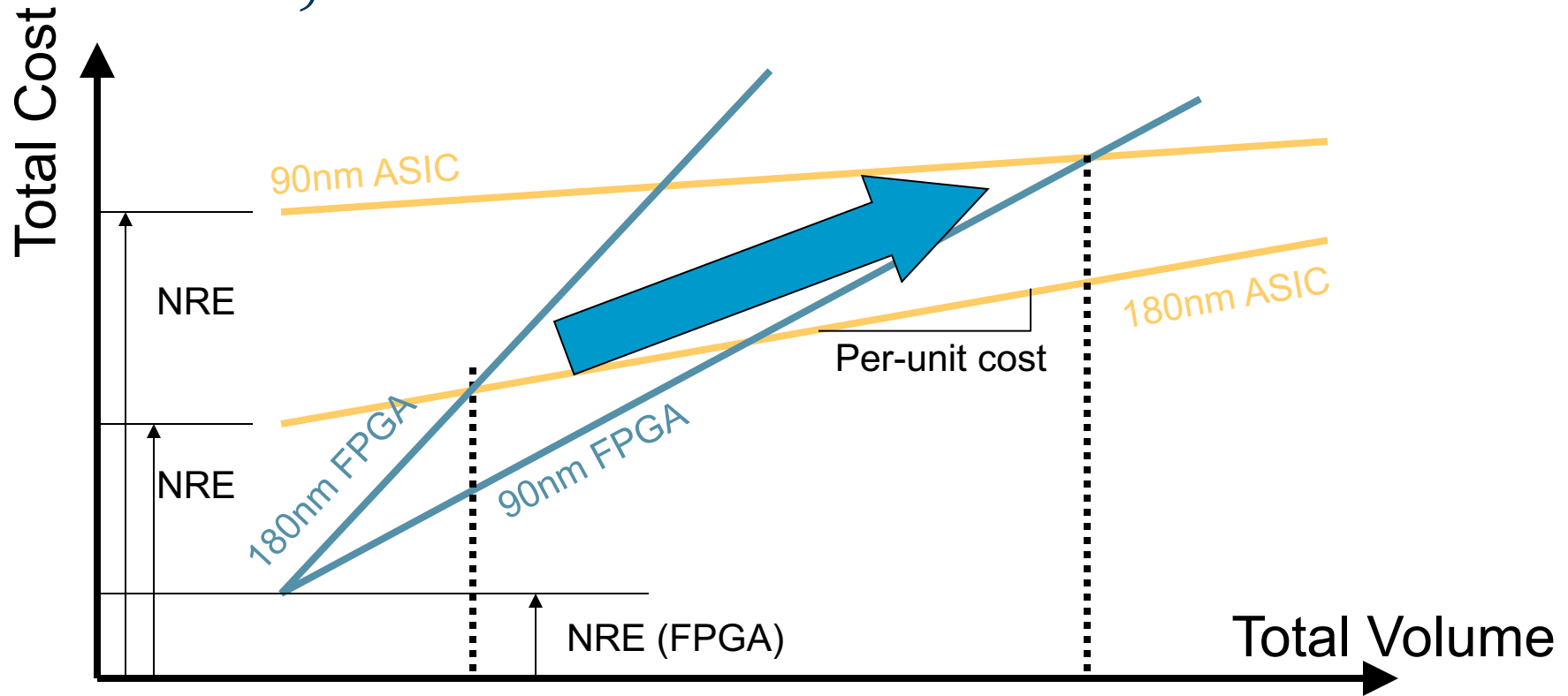

- Spartan-3E
 - 90nm
 - ~300 MHz


- Crossover point at ~250,000 units
- 1.2M system gates for under US\$9.00 (XC3S1200E*)

FPGA Design Flow

Traditional Design Flow


- With its root as an ASIC replacement, traditional FPGA design flow resembles closely that of an ASIC design.
- Start with schematics or high level hardware description languages, the design flow translate the input designs into low level entities
- FPGA's programmability make the low-level flow slightly different

FPGA design flow overview

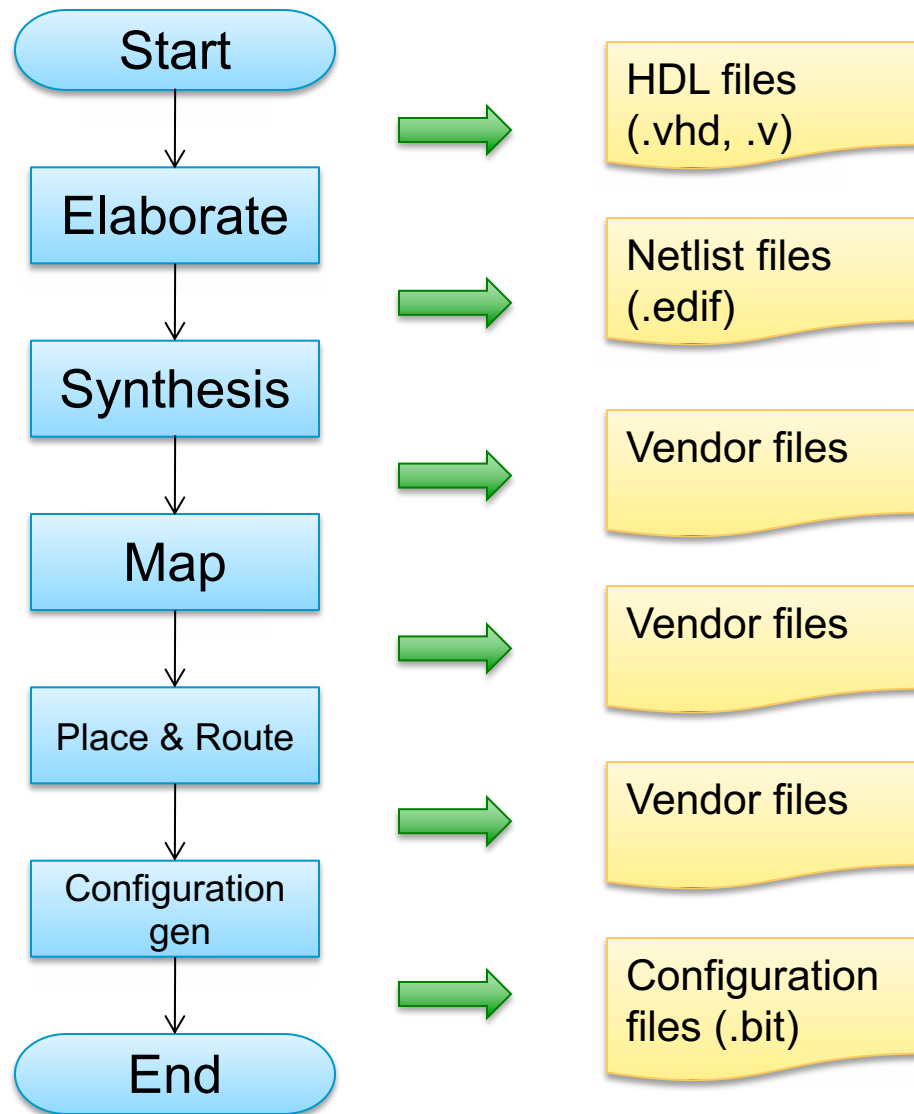

Elaborate

 - Assemble netlists from different sources
- Basic syntax check
- Basic inference
 - First step of real synthesis



Synthesis (Behavioral HDL)

- e.g.
if (d > e) then
 c <= a * b
else
 c <= a * e
end if
- Extract hardware structures from the code
- E.g. muxes, adders, multipliers, RAM, Flip-flops, etc
- Requires careful “writing styles” so that the synthesis tool can successfully extract the “correct” structure
- Many strange errors can be attributed to incorrect synthesis results.
- Synthesis tools *may* optimize for the target device

Synthesis (Structural HDL)

```
FA0: FULLADDER port map (a(0), b(0), Cin, sum(0), c(1));  
FA1: FULLADDER port map (a(1), b(1), C(1), sum(1), c(2));  
FA2: FULLADDER port map (a(2), b(2), C(2), sum(2), c(3));  
FA3: FULLADDER port map (a(3), b(3), C(3), sum(3), c(4));  
Cout <= c(4);
```

- Hardware structure is already presented in the code
- Synthesis tools simply translate and assemble the structures into a correct netlist
- Low-level blocks may be instantiated directly
 - But the code will no longer be “portable”

Map

- Convert netlist into LUTs, FFs, on-chip RAM, hardcore multipliers, DSP blocks, etc
- Generate the actual LUT equations
- May reorganize logics combine signals from different parts of the design into 1 LUT

Place and Route

- Place:
Select the site to where each LUT and FF should locate
- Route:
Select the optimal route to connect all LUTs and FFs
- Most time consuming
- Iterative process
 - Placement affects Route, and vice versa

Configuration Generation

- Generate final configuration for the device
- Download to the FPGA during run time
 - E.g. through JTAG