

# Lecture 16

## EE 421 / CS 425

# Digital System Design

Fall 2024

Shahid Masud

# Topics

- Examples: Booth / Radix 4 Multiplication
- Binary Divider Operation
- Binary Divider Circuit
- STG of Divider
- Floating Point Representation (if time permits)
- Floating Point Multiplier – design and operation

# Bit-Pair Encoding

## Modified Booth Encoding

## Radix-4 Encoding

$m_{i+1}$	$m_i$	$m_{i-1}$	Code	$BRC_{i+1}$	$BRC_i$	Value	Status	Multiply Actions
0	0	0	0	0	0	0	String of 0s	Shift by 2
0	0	1	1	0	1	+1	End of string of 1s	Add, Shift by 2
0	1	0	2	0	1	+1	Single 1	Add, Shift by 2
0	1	1	3	1	0	+2	End of string of 1s	Shift by 1, Add, Shift by 1
1	0	0	4	<u>1</u>	0	-2	Begin of string of 1s	Shift by 1, Subtract, Shift by 1
1	0	1	5	0	<u>1</u>	-1	Single 0	Subtract, Shift by 2
1	1	0	6	0	<u>1</u>	-1	Begin of string of 1s	Subtract, Shift by 2
1	1	1	7	0	0	0	Midstring of 1s	Shift by 2

# Bit-Pair / Radix-4 Recoding of $-65_{10}$

$-65_{10} =$




Imaginary '0' if LSB=1

2's Complement notation

$+65 = (01000001)$

2's Complement

$-65 = (10111111)$

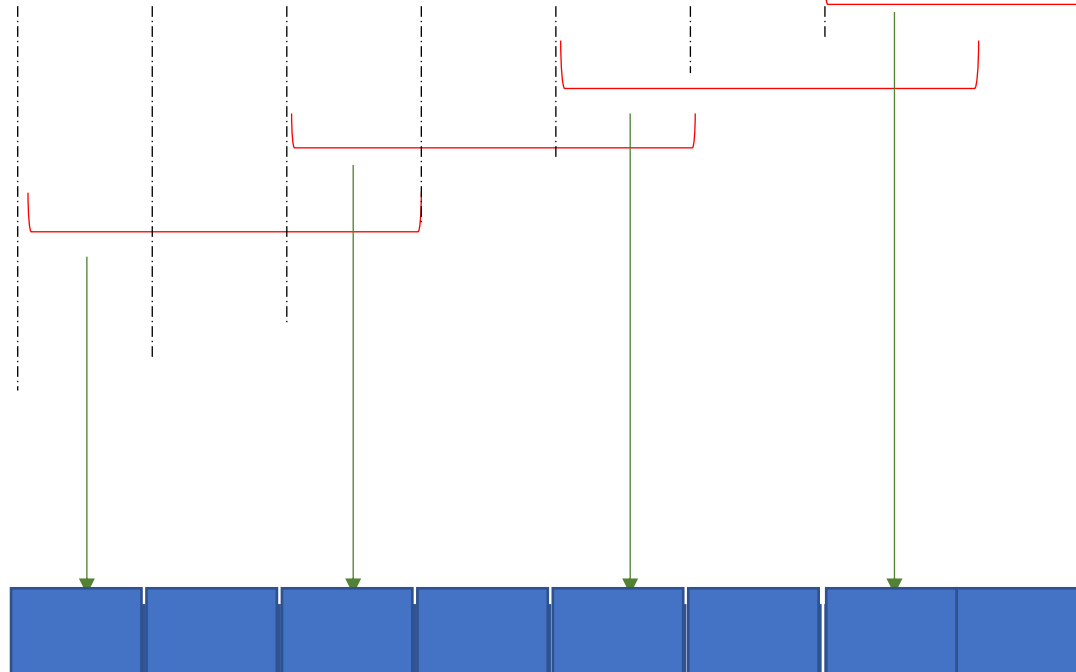

$-65_{10} =$



$m_{i+1}$	$m_i$	$m_{i-1}$	$BRC_{i+1}$	$BRC_i$	Value
0	0	0	0	0	0
0	0	1	0	1	+1
0	1	0	0	1	+1
0	1	1	1	0	+2
1	0	0	<u>1</u>	0	-2
1	0	1	0	<u>1</u>	-1
1	1	0	0	<u>1</u>	-1
1	1	1	0	0	0

Bit-Pair Recoded notation

# Question of Bit-Pair/Radix-4 Encoding

Express  $-75_{10}$  in Radix-4 Encoded format using 8 bits to express the given number

$m_{i+1}$	$m_i$	$m_{i-1}$	$BRC_{i+1}$	$BRC_i$	Value
0	0	0	0	0	0
0	0	1	0	1	+1
0	1	0	0	1	+1
0	1	1	1	0	+2
1	0	0	1	0	-2
1	0	1	0	1	-1
1	1	0	0	1	-1
1	1	1	0	0	0

$$+75_{10} = (64+8+2+1) = (0100\ 1011)_2$$

Thus 2's Complement  
 $= (1011\ 0101)_2 = -75$

1 0 1 1 0 1 0 1[0]

2; coded 01

2; coded 01

6; coded 0 -1

5; coded 0 -1

Radix 4 Encoded = 0 -1 0 -1 0 1 0 1


Radix 4 Encoded = 0 1 0 1 0 1

# Radix 4 Coding for Multiplication

$m_{i+1}$	$m_i$	$m_{i-1}$	Code	Multiply Actions
0	0	0	0	Shift Left by 2
0	0	1	1	Add Multiplicand, Shift Left by 2
0	1	0	2	Add Multiplicand, Shift Left by 2
0	1	1	3	Shift by 1, Add Multiplicand, Shift by 1
1	0	0	4	Shift by 1, Subtract Multiplicand, Shift by 1
1	0	1	5	Subtract Multiplicand, Shift Left by 2
1	1	0	6	Subtract Multiplicand, Shift Left by 2
1	1	1	7	Shift Left by 2


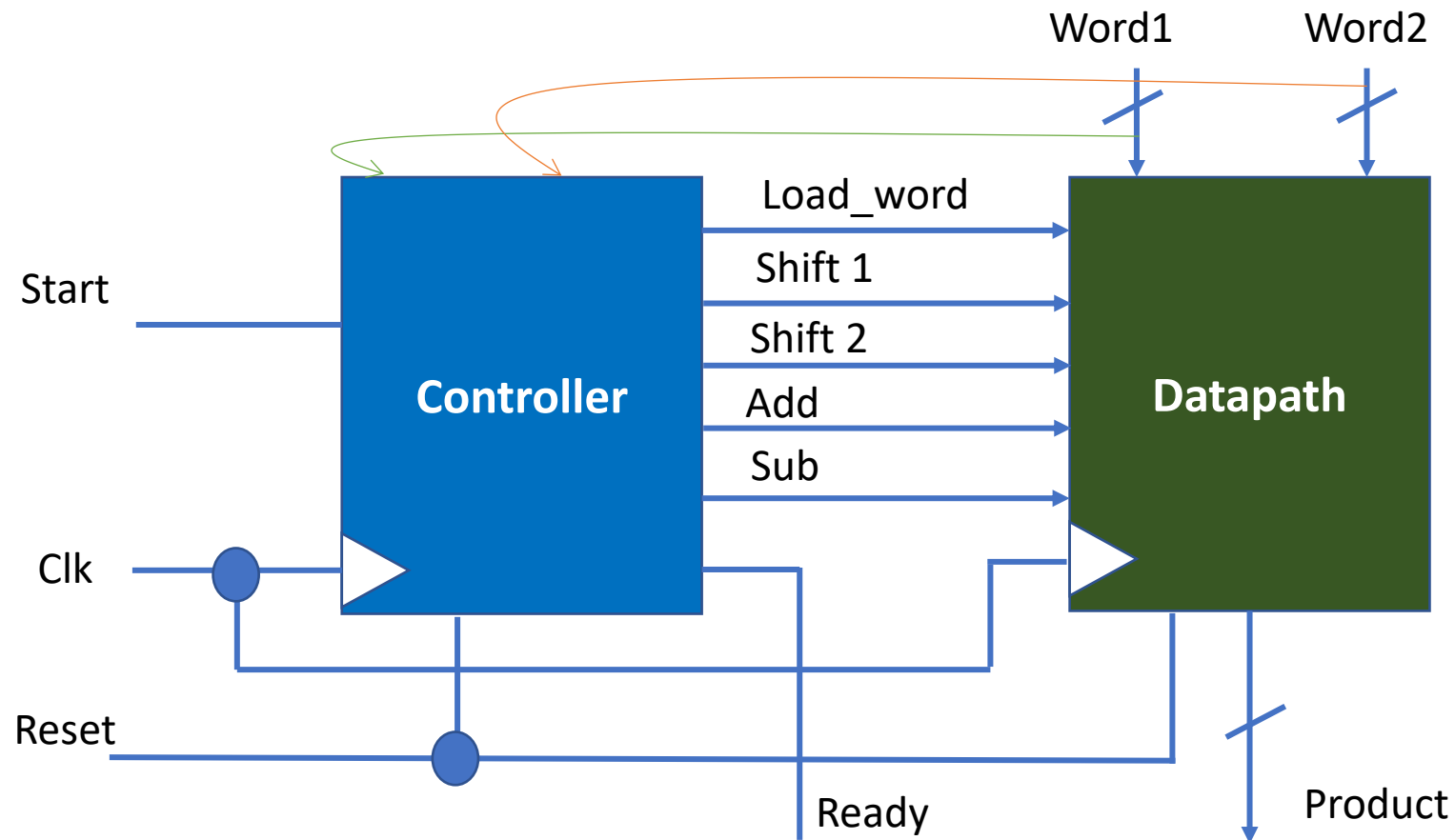
# Data Path Architecture of a Radix 4 Sequential Multiplier





# Radix 4 Multiplication – Example 1

Imagine Zero bit if LSB = 1

Show Radix 4 Encoded multiplication of 8 x 9, using 8 bits for both numbers

8 = 0000 1000

9 = 0000 1001

Convert 9 = 0000 1001 to Radix 4 Encoded bits

9 = 0 0 0 0 1 0 0 1 [0]

**RECODED**

010 → 01

100 → -1 0

001 → 01

000 → 00

8 = Multiplicand

X 9 = Recoded Multiplier

										0	0	0	0	1	0	0	0
										0	0	0	1	-1	0	0	1
0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
1	1	1	1	1	1	1	1	1	1	1	0	0	0	X	X	X	
0	0	0	0	0	0	0	0	0	1	0	0	0	X	X	X	X	
													X	X	X	X	
0	0	0	0	0	0	0	0	0	0	1	0	0	1	0	0	0	

0 1 = Add Multiplicand, Shl2

-1 0 = Shl 1, Sub, Shl1

0 1 = Add, Shl2

0 0 = Only Shl2, No op

Answer = (0100 1000) = +(64 + 8) = +72<sub>10</sub>

# Radix 4 Multiplication – Example 2

Show Radix 4 Encoded multiplication of **68 x -19**, using 8 bits for both numbers

68 = 0100 0100  
And 2's Compl is  
-68 = 1011 1100

19 = 0001 0011  
And 2's Compl is  
-19 = 1110 1101

Convert -19 = 1110 1101 to Radix 4 Encoded bits

-19 = 1 1 1 0 1 1 0 1 [0]

Imagine Zero

**RECODED**  
010 → 01  
110 → 0-1  
110 → 0-1  
111 → 00

68 = Multiplicand

X -19 = **Recoded** Multiplier

Result

										0	1	0	0	0	1	0	0
										0	0	0	-1	0	-1	0	1
	0	0	0	0	0	0	0	0	0	0	1	0	0	0	1	0	0
1	1	1	1	1	1	1	1	0	1	1	1	1	0	0	X	X	
1	1	1	1	1	1	0	1	1	1	1	0	0	X	X	X	X	
													X	X	X	X	
1	1	1	1	1	1	0	1	0	1	1	1	1	0	1	0	0	

0 1 = Add Multiplicand, Shl2

0 -1 = Sub, Shl2

0 -1 = Sub, Shl2

0 0 = Only Shl2, No op

Take 2's Complement of Result = -(0101 0000 1100) = -(50C) Hex = -(1292)<sub>10</sub>

# Radix 4 Multiplication – Example 3

Show Radix 4 Encoded multiplication of **76 x 55**, using 8 bits for both numbers

76 = 0100 1100  
And 2's Compl is  
-76 = 1011 0100

55 = 0011 0111  
And 2's Compl is  
-55 = 1100 1001

Convert 55 = 0011 0111 to Radix 4 Encoded bits

55 = 0 0 1 1 0 1 1 1 [0]

Imagine Zero

**RECODED**  
110 → 0-1  
011 → 10  
110 → 0-1  
001 → 01

76 = Multiplicand

X 55 = Recoded Multiplier

Partial Sum

Partial Sum

Result

										0	1	0	0	1	1	0	0
										0	1	0	-1	1	0	0	-1
	1	1	1	1	1	1	1	1	1	0	1	1	0	1	0	0	
	0	0	0	0	0	0	0	1	0	0	1	1	0	0	X	X	X
Partial Sum	0	0	0	0	0	0	0	1	0	0	0	0	1	0	1	0	0
	1	1	1	1	1	1	0	1	1	0	1	0	0	X	X	X	X
Partial Sum	1	1	1	1	1	1	1	0	1	0	1	0	1	0	1	0	0
	0	0	0	0	1	0	0	1	1	0	0	X	X	X	X	X	X
Result	0	0	0	0	1	0	0	0	0	0	1	0	1	0	1	0	0

0 -1 = Sub, Shl2

1 0 = Shl1, Add, Shl1

0 -1 = Sub, Shl2

0 1 = Add, Shl2

**Answer = 0001 0000 0101 0100 = (4+16+64+4096) = (4180)<sub>10</sub>**

# Question?

Perform the following multiplication using Radix 4 Encoding.

Multiplicand = 38, Multiplier = 23 (bits allocated?)

How many Adds and Shifts are required in this multiplication?

How does this compare to a simple binary array multiplier?

# Division Operation in Decimal Numbers

Division of  $274 \div 13$

				2	1	Quotient
Divisor	1	3	2	7	4	Dividend
		-	-2	6		
				1	4	
			-	1	3	
		Remainder		1	Rem	

# Division Operation in Decimal Numbers

Division of  $299 \div 15$

			1	9	Quotient	
Divisor	1	5	2	9	9	Dividend
		-	2	8	5	
		Remainder	1	4	Rem	

# Decimal Division – another example

		1	0	0	4	Quotient
Divisor	8	8	0	3	5	Dividend
	-	8				
		0	0	3	5	
		-		3	2	
	Remainder				3	

### Division of $274 \div 13$

			2	1	
1	3	2	7	4	
	-	-2	6		
			1	4	
		-	1	3	
				1	Rem

## Divisor

Divisor					1	0	1	0	1				
1	1	0	1		1	0	0	0	1	0	0	1	0
		-			0	1	1	0	1				
						1	0	0	0	0			
		-					1	1	0	1			
						0	0	0	1	1	1	0	
							-		1	1	0	1	
									0	0	0	1	Re

## Remainder



# Division Operation in Binary – Example 2

Division of  $299 \div 15$


			1	9	
1	5	2	9	9	
	-	2	8	5	
			1	4	Rem

Divisor														Quotient			
				1	0	0	1	0	1	0	1	1					
1	1	1	1	1	0	0	1	0	1	0	1	1	Dividend				
			-		1	1	1	1									
					0	0	1	1	1	0	1						
			-		0	0	1	1	1	1	1						
					0	0	1	1	1	0	1						
									1	1	1	1					
									1	1	1	0					
						</											

## Division Operation in Binary – Example 3

								1 1 0 1 Quotient					
Divisor	1	0	1	1	1	0	0	1	0	0	1	1	Dividend
			-		1	0	1	1					
					0	1	1	1	0				
			-			1	0	1	1				
						0	0	1	1	1	1		
					-			1	0	1	1		
								0	1	0	0	Re	
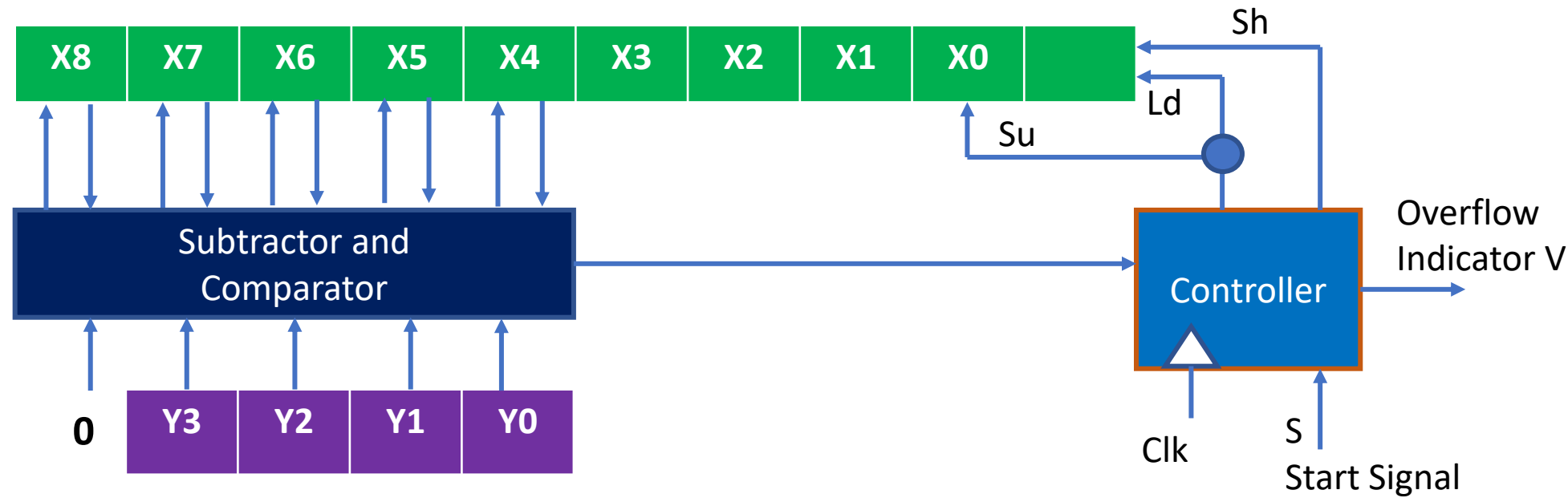
# Block Diagram of Sequential Binary Divider



Dividend Register

0	1	0	0	0	0	1	1	1
---	---	---	---	---	---	---	---	---

Divisor Register


1	1	0	1
---	---	---	---

Overflow V = As a result of a division operation, if the quotient requires more bits than are available for storing quotient

# Operation of Sequential Binary Divider

Show binary division

135 ÷ 13

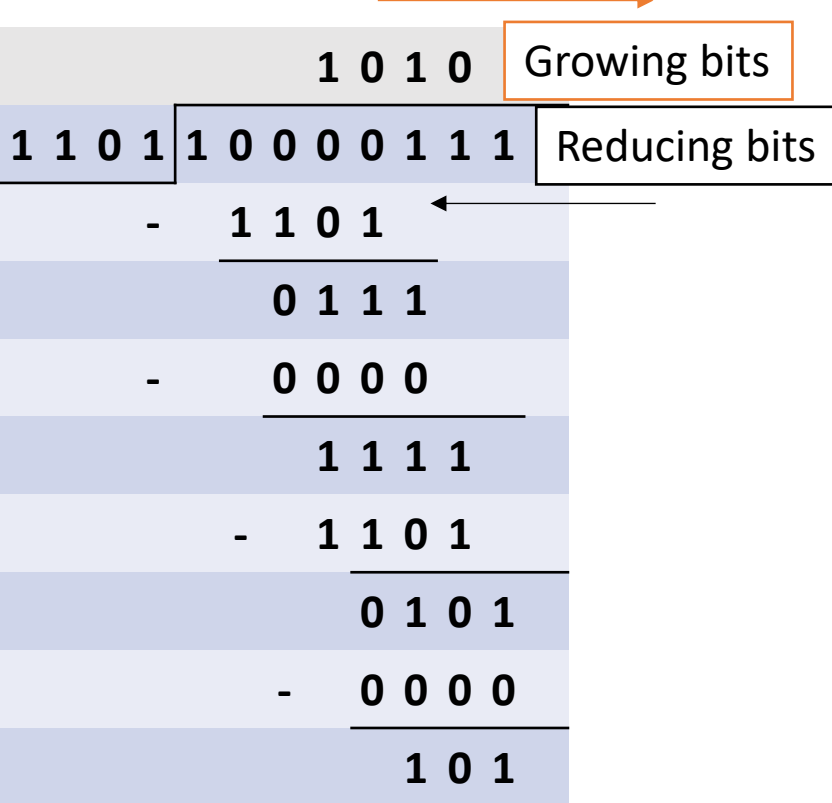

Dividend



Dividing line between Dividend and Quotient

After the shift, the right most position in dividend register is 'empty'

Subtraction is now carried out. The first quotient digit of 1 is stored in the unused portion of the dividend register



First quotient digit

Next we shift the dividend one place to the left



Since subtraction yields negative result so we shift dividend to the left again, and the second quotient bit remains 0



Subtraction is now carried out, the third quotient digit of 1 is stored in the unused portion of the dividend register



Third quotient digit


A final shift is done and fourth quotient bit is set to 0



Quotient

Remainder

# STG of a Binary Divider

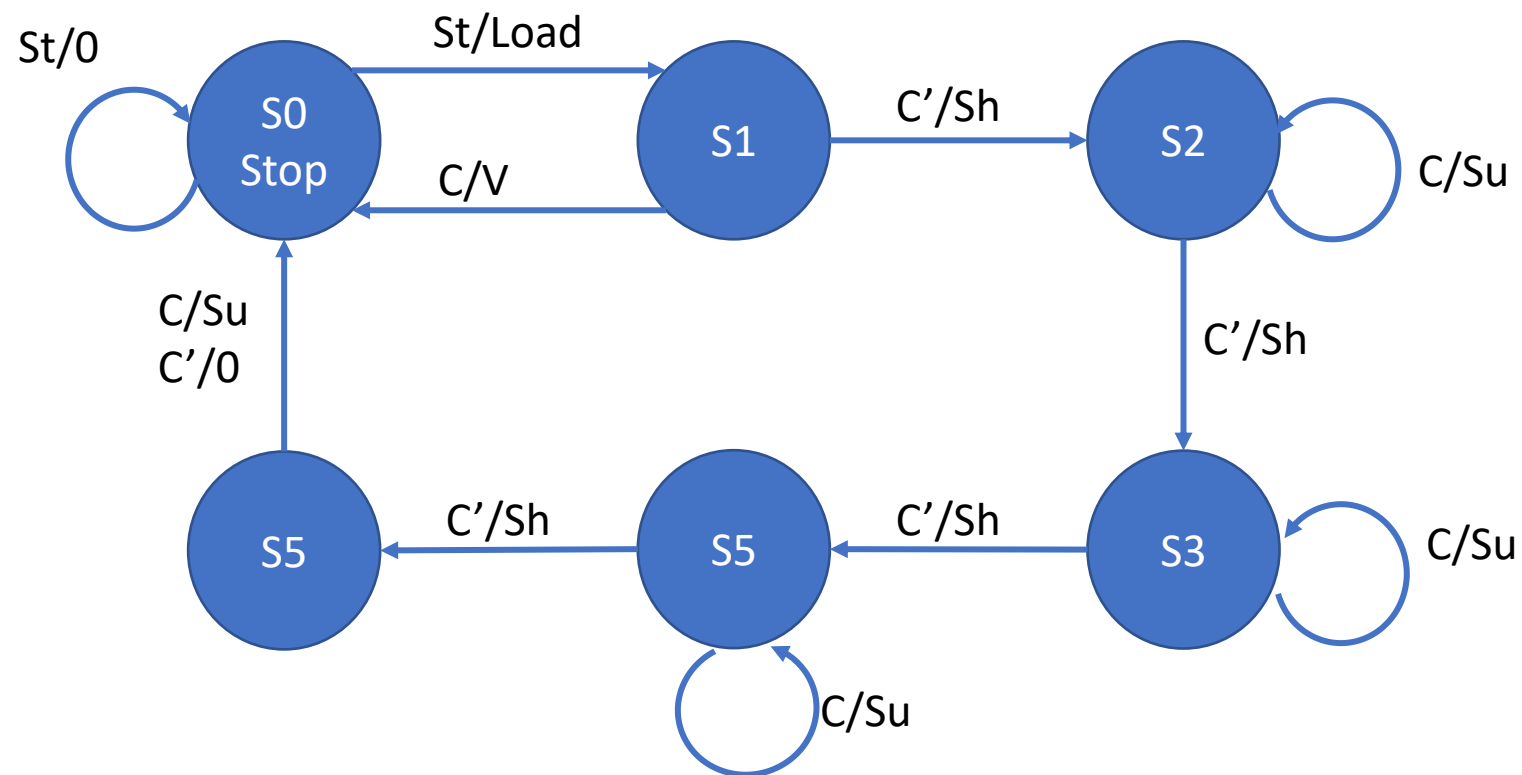

**Su = Subtract Signal**

**C = Comparator Output**

**If divisor is greater than 5 leftmost dividend bits (as per given number),  
then C=0; otherwise C=1**

**Whenever C=1, then subtract signal is generated and quotient bit is set to 1**

**Whenever C=0, then subtraction cannot occur without a negative result so a  
Shift signal Sh is generated**

# Division Examples

- Try using 2's Complement Add instead of Sub in Division operations